

Channel capacity :- Max. data rate. Independent of latency and modulation.


AWGN channels :- Capacity \propto B.W

$$C = BW \log_2 (SNR + 1)$$

→ If $SNR \times 4$, we could use 4 levels,
⇒ 2 extra bits ... hence the log.


Basic concepts

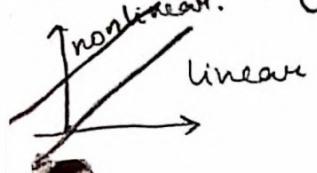① Linearity :- linear combination of inputs produces the same linear combination at the outputs.
 Graphically:- Straight line through the origin.



② Time invariance :- Response does not change with time.

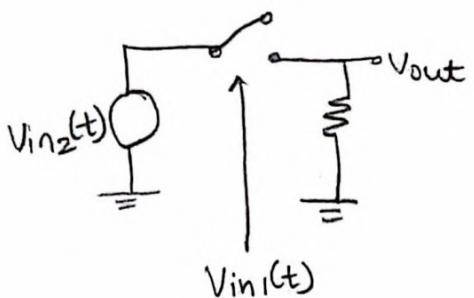
→ Linear \Rightarrow may change the frequency content of input
 LTI \Rightarrow Don't. Although magnitudes of each freq. component may vary.



→ V_{in_1} to V_{out} is nonlinear, V_{in_2} to V_{out} is linear.
 → Both are time variant.
 → In circuits with switches, the system must be well defined to draw conclusions.

③ Memory / memoryless :- Output depends only on current input \Rightarrow Memoryless
 L, C networks have memory.

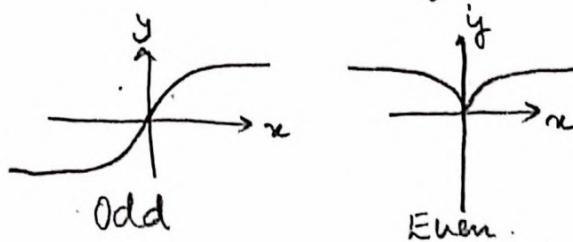④ Symmetry :- Odd \Rightarrow w.r.t origin : $x(t) \rightarrow y(t) = y - x(t) \rightarrow -y(t)$
 Even \Rightarrow w.r.t y-axis : $x(t) \rightarrow y(t) \Rightarrow -x(t) \rightarrow y(t)$



LTI: $y(t) = x(t) * h(t)$

LTV: $y(t) = x(t) * h(t, \tau)$

Nonlinear: Approximated using the Volterra series.

Units in RF

① power $\left|_{\text{dBm}}\right. = 10 \log (\text{power in mW})$

$$0 \text{ dB} = 1 \text{ mW}$$

$$30 \text{ dB} = 2 \text{ mW}$$

$$-3 \text{ dB} = 0.5 \text{ mW}$$

What $V_{\text{pp-pk}}$ is necessary to deliver 1mW (0dBm) to a 50Ω load? $V_{\text{pp}} = 632 \text{ mV}$

$$\Rightarrow [0 \text{ dBm} \leftrightarrow 1 \text{ mW} \leftrightarrow 632 \text{ mV} @ 50\Omega]$$

② Ratios $\left|_{\text{dB}}\right. \frac{V}{V} = 20 \log \frac{V_1}{V_2} ; \frac{P}{P} = 10 \log \frac{P_1}{P_2}$

$\frac{V}{V}$	dB
1	0
2	6
3.1	10
4	12
10	20

Nonlinearity Effects

$$x(t) \rightarrow \boxed{\quad} \rightarrow y(t)$$

$$y(t) = \alpha_1 x(t) + \alpha_2 x^2(t) + \alpha_3 x^3(t) \rightarrow 3^{\text{rd}} \text{ degree of nonlinearity}$$

① Harmonic generation \rightarrow Assuming alphas are constant \Rightarrow Not so nonlinear

If $x(t) = A \cos \omega t$

$$y(t) = \alpha_1 A \cos \omega t + \alpha_2 A^2 \cos^2 \omega t + \alpha_3 A^3 \cos^3 \omega t$$

$$= \underbrace{\frac{\alpha_2 A^2}{2}}_{0^{\text{th}}} + \underbrace{\left(\alpha_1 A + \frac{3\alpha_3 A^3}{4} \right) \cos \omega t}_{\text{fundamental}} + \underbrace{\frac{\alpha_2 A^2}{2} \cos 2\omega t + \frac{\alpha_3 A^3}{4} \cos 3\omega t}_{\text{higher order harmonics}}$$

Observations

① Differential pair (or any diff treatment) gets rid of the even harmonics including 0 since they are even functions!


② Amplitude of n^{th} harmonic has A^n and above terms.

$\Rightarrow n^{\text{th}}$ harmonic $\approx \propto A^n$ when $A \ll 1$ also $\alpha_1 \gg \alpha_2 \alpha_3 \rightarrow$ Not so nonlinear

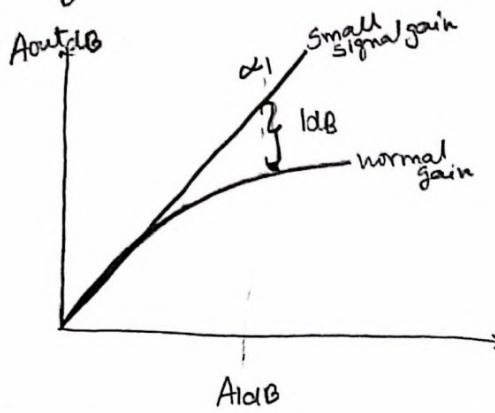(II) Gain compression

→ Small signal gain = α_1 since $A \ll 1$

• Regular gain @ fundamental = $\alpha_1 + \frac{3}{4} \alpha_3 A^2$ where α_3 is usually negative
 \Rightarrow as $A \uparrow$, gain @ fundamental drops.



\Rightarrow gain is a function of A_{in} .
 $\rightarrow A_{1dB}$ is the input value for which gain falls by 1dB.
 $\rightarrow 20 \log |\alpha_1 + \frac{3}{4} \alpha_3 A_{1dB}^2| = 20 \log |\alpha_1| - 1dB$

$$\Rightarrow A_{1dB} = \sqrt{0.145 \left| \frac{\alpha_1}{\alpha_3} \right|}$$

(III) Blocking / Desensitization

→ ^{strong} A tone at some frequency (ω_2) can lower the signal amplitude of interest @ ω_1 .

$$x(t) = A_1 \cos \omega_1 t + A_2 \cos \omega_2 t$$


$$y(t) \approx \left(\alpha_1 + \frac{3}{2} \alpha_3 A_2^2 \right) A_1 \cos \omega_1 t \quad \text{when } A_2 \gg A_1$$

\Rightarrow gain α_1 is desensitized by A_2

Blocking \Rightarrow gain is 0.

→ Can ω_1 and ω_2 be arbitrary? No since the receiver itself has a B.W.

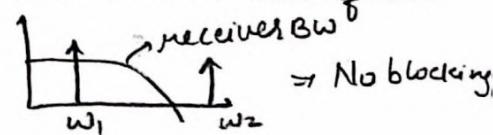In this case alphas are ~~fun~~ of frequency and are not constant.



(IV) Cross modulation

→ If there is an interfering signal A_2 which is modulated. Its modulation leaks into our desired signal A_1 .

$$\text{If } A_2 \xrightarrow{AM} A_2 (1+m \cos \omega_m t) \cos \omega_2 t$$

$$\Rightarrow y(t) = \left[\alpha_1 A_1 + \frac{3}{2} \alpha_3 A_2^2 A_1 \left(1 + \frac{m^2}{2} + \frac{m^2}{2} \cos 2\omega_m t + 2m \cos \omega_m t \right) \right] \cos \omega_1 t$$

→ Now the signal is amplitude modulated at ω_m and $2\omega_m$.

(IV) Intermodulation

→ 2 input signals at ω_1 and ω_2 produce outputs at frequencies other than the harmonics of ω_1 and ω_2 .

$$x(t) = A_1 \cos \omega_1 t + A_2 \cos \omega_2 t$$

⇒ $y(t)$ has the following terms (ignored DC and higher harmonics)

$$\text{at } \omega = \omega_1 \pm \omega_2 : \alpha_2 A_1 A_2 \cos(\omega_1 + \omega_2)t + \alpha_2 A_1 A_2 \cos(\omega_1 - \omega_2)t$$

nd order { at $\omega = 2\omega_1 \pm \omega_2$: $\frac{3\alpha_3 A_1^2 A_2}{4} \cos(2\omega_1 + \omega_2)t + \frac{3\alpha_3 A_1^2 A_2}{4} \cos(2\omega_1 - \omega_2)t$
 at $\omega = \omega_1 \pm 2\omega_2$: $\frac{3\alpha_3 A_1 A_2^2}{4} \cos(2\omega_2 + \omega_1)t + \frac{3\alpha_3 A_1 A_2^2}{4} \cos(2\omega_2 - \omega_1)t$


$$\text{at } \omega = \omega_1, \omega_2 : (\alpha_1 A_1 + \frac{3}{4} \alpha_3 A_1^3 + \frac{3}{2} \alpha_3 A_1 A_2^2) \cos \omega_1 t \xrightarrow{\text{is the gain of signal 1 ie } \alpha_1 + 3\alpha_3 (\frac{A_1^2}{4} + \frac{A_2^2}{2})}$$

$$(\alpha_1 A_2 + \frac{3}{4} \alpha_3 A_2^3 + \frac{3}{2} \alpha_3 A_2 A_1^2) \cos \omega_2 t \xrightarrow{\text{is the gain of 2nd signal.}}$$

→ The signals we care about are at $2\omega_1 - \omega_2$ and $2\omega_2 - \omega_1$ because they are too close to ω_1 and ω_2 to filter them out.

How do we characterize it? Two tone test!

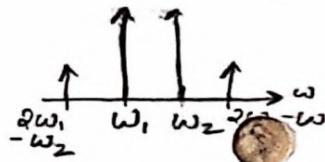Use $A_1 = A_2 = A$, The ratio of the op 3rd order products ($2\omega_1 - \omega_2$ & $2\omega_2 - \omega_1$) to $\alpha_1 A$ (small signal gain) gives the IM distortion.




→ This affects only the amplitude of our signal of interest. So can we just use phase modulation? No, because it affects the zero crossing points (and hence the stability of the system).

→ Third intercept point (IP₃)

When A is small gain is $\approx \alpha_1$. When $A \uparrow$, gain $\uparrow \propto A$ (ignoring gain compression)
 Whereas third order IM terms $\propto A^3$

→ IP₃ :- Input amplitude where the fundamental freq. amplitude (to the first order approximation) is equal to the 3rd order IM terms ($2\omega_1 - \omega_2 + 2\omega_2 - \omega_1$) is called IP₃.

$$|g_1| A_{IP_3} = \frac{3}{4} |\alpha_3| A^3 \Rightarrow A_{IP_3} = \sqrt{\frac{4}{3} \left| \frac{\alpha_1}{\alpha_3} \right|}$$

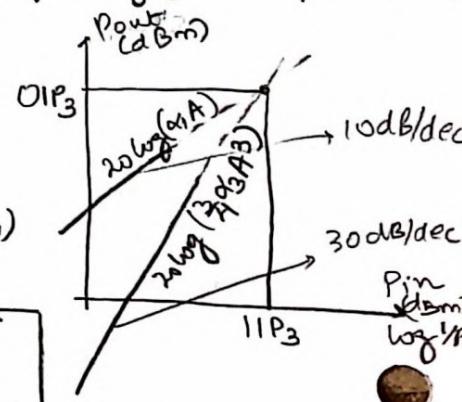


→ In reality gain compression sets in much before IP₃. So extrapolate linearly from small signal gain on a log-log plot.

How do we measure IIP_3 on a circuit?


$$\frac{A_{W_1, W_2}}{A_{IM_3}} = \frac{\frac{1}{3} |\alpha_1| A_{in}}{\frac{3}{4} |\alpha_3| A_{in}^3} = \frac{\frac{4}{3} |\alpha_1|}{|\alpha_3|} \cdot \frac{1}{A_{in}^2} = \frac{A_{IP_3}^2}{A_{in}^2}$$

$$\Rightarrow \frac{IIP_3}{dB} = \frac{1}{2} (20 \log A_{W_1, W_2} - 20 \log A_{IM_3}) + 20 \log A_{in}$$
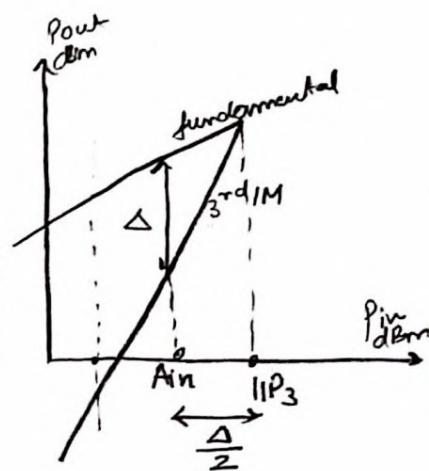
$$\Rightarrow \boxed{\frac{IIP_3}{dB} = \frac{1}{2} (\text{Diff. of fundamental } \pm IM_3) + \text{Input } (A_{in})_{dB}}$$



VII Cascaded nonlinear stages

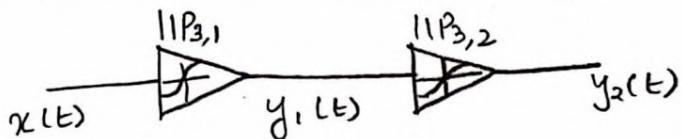

$$\left\{ \begin{array}{l} y_1(t) = \alpha_1 x(t) + \alpha_2 x^2(t) + \alpha_3 x^3(t) \\ y_2(t) = \beta_1 y_1(t) + \beta_2 y_1^2(t) + \beta_3 y_1^3(t) \end{array} \right.$$

Solve for $y_2(t)$ in terms of $x(t)$, and
use two tone test $x(t) = A \cos \omega_1 t + A \cos \omega_2 t$

y_{out} get,

$$y(t) = \alpha_1 \beta_1 A (\cos \omega_1 t + \cos \omega_2 t) + (\alpha_3 \beta_1 + 2\alpha_1 \alpha_2 \beta_2 + \alpha_1^3 \beta_3) \left(\frac{3}{4} A^3 \right) (\cos(2\omega_1 - \omega_2)t + \cos(2\omega_2 - \omega_1)t) + \dots$$

$$\Rightarrow A_{IP_3} = \sqrt{\frac{4}{3} \left| \frac{\alpha_1 \beta_1}{\alpha_3 \beta_1 + 2\alpha_1 \alpha_2 \beta_2 + \alpha_1^3 \beta_3} \right|} \xrightarrow{\text{rewriting}} \frac{1}{A_{IP_3}^2} = \underbrace{\frac{1}{A_{IP_3,1}^2}}_{\text{Stage ①}} + \underbrace{\frac{3\alpha_2 \beta_2}{2\beta_1}}_{\text{Stage ②}} + \underbrace{\frac{\alpha_1^2}{A_{IP_3,2}^2}}_{\text{Stage ③}}$$

→ Notice, $A_{IP_3,2}$ is scaled down by gain of stage ① so we want $A_{IP_3,2}$ to be high to begin with. Intuitively, outputs of stage ① are 'large signals' so we want $A_{IP_3,2}$ to be large so that it can handle them.

→ The term $\frac{3\alpha_2 \beta_2}{2\beta_1}$ comes from $\omega_1 - \omega_2, 2\omega_1, 2\omega_2$ generated by stage ①. It can be filtered so we are left with $\frac{1}{A_{IP_3}^2} = \frac{1}{A_{IP_3,1}^2} + \frac{\alpha_1^2}{A_{IP_3,2}^2}$

→ Generalizing,

$$\frac{1}{A_{IP_3}^2} = \frac{1}{A_{IP_3,1}^2} + \frac{\alpha_1^2}{A_{IP_3,2}^2} + \frac{\alpha_1^2 \beta_1^2}{A_{IP_3,3}^2} + \frac{\alpha_1^2 \beta_1^2 \gamma_1^2}{A_{IP_3,4}^2} + \dots$$


→ Later stages should be more linear!

RF System parameters

Receiver specifications

- ① Noise \approx Sensitivity (Also depends on modulation and BER)
- ② Quality factor (Image rejection)
- ③ Linearity (max ip signal) \rightarrow Set by breakdown voltage.
- ④ P_{dc} - dc power consumption
- ⑤ Gain

Dynamic Range

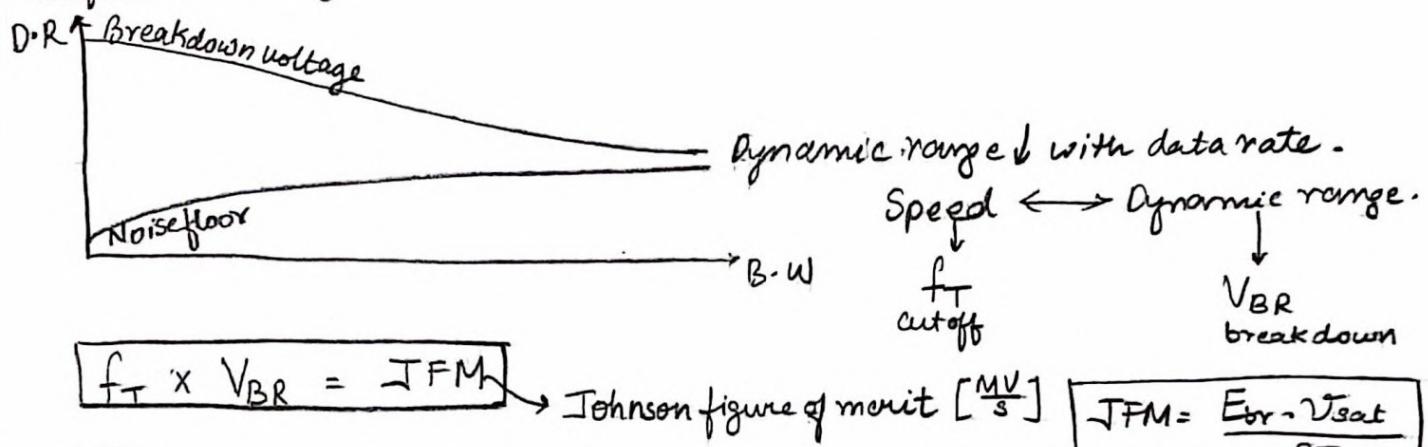

$JFM_{Si} = 1 \rightarrow$ normalised to Si

$JFM_{GaAs} = 2.7$

$JFM_{SiC} = 20$

$JFM_{GaN} = 24.5$ (Costly)

E_{BR} : Breakdown field

V_{sat} : - saturation velocity.

Transmitter specifications


- ① $P_{dc} \rightarrow$ DC power consumption \rightarrow keep low
- ② $P_{out} \rightarrow$ Transmitted power \rightarrow keep high.
- ③ Power spectral density mask
- ④ Noise (Want to send pure signal)
- ⑤ Error vector magnitude.

Passive Structures


- can handle higher frequencies
- higher efficiency at high frequencies.

AC Circuits

(I) Parallel

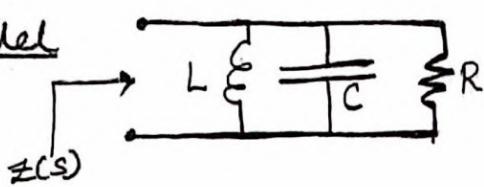
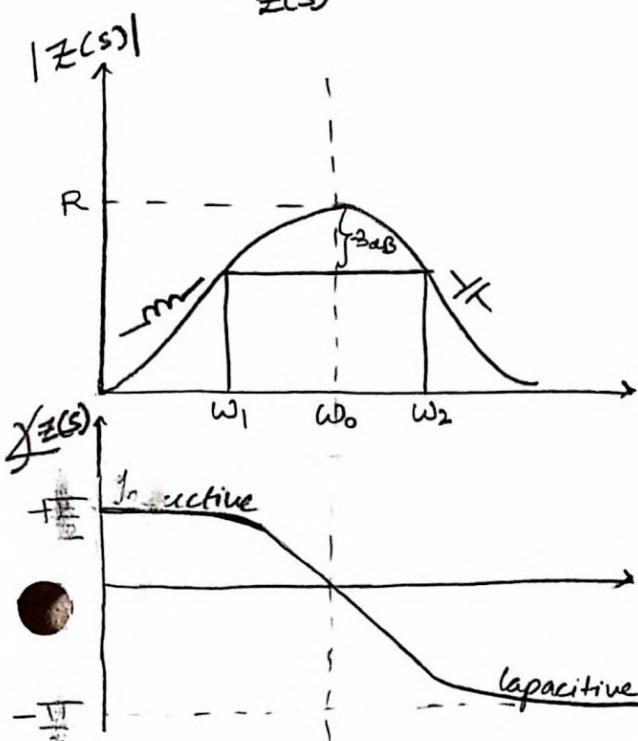
$$Z(s) = \frac{1}{C} \circ \frac{s}{s^2 + \frac{1}{RC}s + \frac{1}{LC}} \frac{\omega_0}{\omega_0^2}$$



$$BW_{-3dB} = \omega_2 - \omega_1 \quad |Z| = R - 3dB \rightarrow \text{Solve for } 2 \text{ root} \\ \text{to find } \omega_1, \omega_2$$

$$\Rightarrow BW = \frac{\omega_0}{Q} \quad \text{At a given } \omega_0, Q \uparrow \Rightarrow BW \downarrow$$

$$\chi Z = \frac{\pi}{2} - \tan^{-1} \left(\frac{\omega \omega_0}{Q} \right) \Rightarrow \frac{d\chi Z}{d\omega} = \frac{2Q}{\omega_0^2} \text{ at } \omega = \omega_0$$

$$Q = \frac{\omega_0}{2} \cdot \left| \frac{d\chi Z(j\omega_0)}{d\omega} \right| \quad \text{High } Q \Rightarrow \text{Steep Slope in phase!}$$


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q = \frac{R}{\omega_0 L} = \omega_0 R C = \frac{R}{\sqrt{LC}}$$

large R \Rightarrow Ideal LC \Rightarrow Q↑

- large C \Rightarrow low X \Rightarrow current flows more easily \Rightarrow high Q. ω₀ occurs early for both C↑ & L↑
- large L \Rightarrow high X \Rightarrow opposes currents \Rightarrow low Q. More current through R

(II) Series

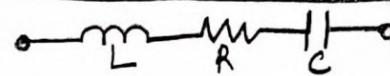

$$Z(s) = \frac{1}{s} (s^2 + \frac{R}{L}s + \frac{1}{LC}) \frac{\omega_0}{\omega_0^2}$$


$$\omega_0 = \frac{1}{\sqrt{LC}} ; \quad BW = \frac{\omega_0}{Q} ; \quad Q = \frac{\omega_0}{2} \left| \frac{d\chi Z(j\omega)}{d\omega} \right|$$

$$Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 R C} = \frac{\sqrt{L/C}}{R}$$

C↑ \Rightarrow Xc↓ \Rightarrow I↑ \Rightarrow more dissipation through R.


L↑ \Rightarrow XL↑ \Rightarrow I↓ \Rightarrow less dissipation through R

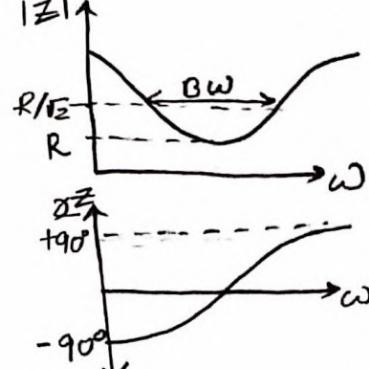R→0 \Rightarrow Ideal LC \Rightarrow Q→∞.



Essence of ω_0 and β

ω_0 Take

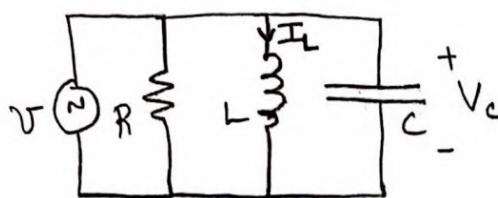


$$\text{let } V = V_0 \cos \omega_0 t$$

$$E_C(t) = \frac{1}{2} C V^2 = \frac{1}{2} C V_0^2 \cos^2 \omega_0 t$$

$$E_L(t) = \frac{1}{2} L I^2 = \frac{1}{2} L \left[\frac{V_0 \sin \omega_0 t}{L \omega_0} \right]^2 = \frac{1}{2} C V_0^2 \sin^2 \omega_0 t$$


$$\Rightarrow [E_C(t) + E_L(t)] = \frac{1}{2} C V_0^2 \Rightarrow \text{Total energy in LC is a constant!}$$

The energies are out of phase

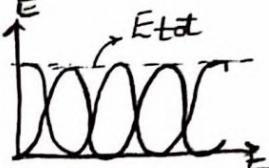

→ Only when $\omega = \omega_0$. Therefore, ω_0 is the frequency at which the total energy in LC is constant and oscillates between "total & E_{total} "

Let's take

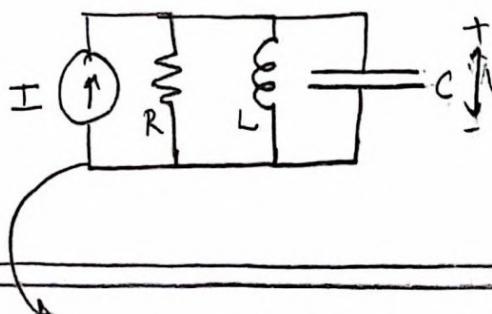

$$\text{let } I = I_0 \cos \omega_0 t$$

$$|Z_L| = |Z_C| \Rightarrow |I_L| = |I_C| = \frac{R I}{L \omega_0} = \frac{R I_0}{L \omega_0}$$

$$\Rightarrow |I_L| = |I_C| = I \beta \quad \text{could destroy components at high } \beta$$

β

$$V = R I \Rightarrow V_0 = R I_0 \Rightarrow E_{\text{tot stored}} = \frac{1}{2} C V_0^2 = \frac{1}{2} C (R I_0)^2, \text{ Here } V_0 \text{ is peak value!}$$

$$E_{\text{tot dissipated}} = \frac{1}{2} R I^2 T = \frac{1}{2} \frac{V^2}{R} T$$

$$\Rightarrow \frac{E_{\text{tot stored}}}{E_{\text{tot dissipated}} \text{ in one } T} = \frac{R C}{T} = \frac{R C \cdot \omega_0}{2 \pi} = \frac{\beta}{2 \pi}$$

$$\Rightarrow \beta = 2 \pi \frac{E_{\text{total stored in one period}}}{E_{\text{dissipated in one period}}} = \omega_0 \cdot \frac{\text{Stored energy}}{\text{Dissipated power}}$$

This is the fundamental definition of β applicable at all frequencies!

→ Impulse response $V(t) \propto e^{-t/\tau_{RC}} \propto e^{(-t/T_0)(\frac{T_0}{\beta})}$ → At each period amplitude drops by $e^{-\pi/\beta}$ → High β → Sustain longer!

→ A system could have multiple ω_0 s & β s.


→ β is defined for any frequency.

→ In H & 1 pF $\Rightarrow f_0 \approx 5 \text{ GHz}$

→ β is roughly the no. of cycles of ringing.


$$\begin{aligned} \beta &= \omega_0 \frac{E_{\text{tot}}}{P_{\text{avg}}} \\ \beta &= \frac{\omega_0}{B_W} = \frac{\omega_0}{2} \left| \frac{d\phi}{d\omega} \right| \\ \beta &= \frac{\text{Im}(Z(\omega))}{\text{Re}(Z(\omega))} \end{aligned}$$

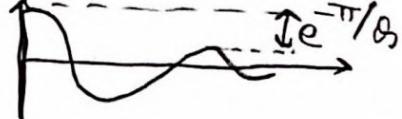Ex:- Piano \Rightarrow High β
Violin \Rightarrow Low β



General Theorem for RLC

L7

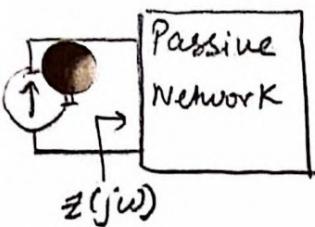

$$z(j\omega) = R(j\omega) + jX(j\omega)$$


$$= \frac{2P_{\text{dissipated}} + 4j\omega [E_M(\omega) - E_E(\omega)]}{|I|^2}$$

① ω_0 :- $E_M(\omega) = E_E(\omega)$

$$\Rightarrow X(j\omega) = 0$$

$E_M(\omega), E_E(\omega)$
are avg stored
M & E energies -

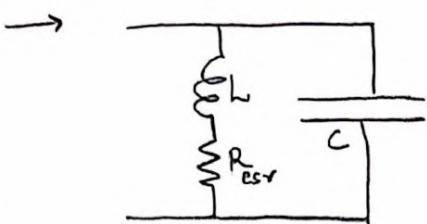For θ_s :- $\theta_s := \frac{\text{Im}\{z\}}{\text{Re}\{z\}}$ {Under certain conditions}



$$\omega_r = \sqrt{\frac{1}{LC} - \left(\frac{R}{L}\right)^2}$$

$$z(j\omega_r) = R(j\omega_r) = \frac{L}{RC} = \frac{\left(\frac{L}{C}\right)^2}{R} = \frac{(L\omega_0)^2}{R} = \frac{1}{R(C\omega_0)^2}$$


where, $\omega_0 = \frac{1}{\sqrt{LC}}$
 $= (\text{no. } R!)$

→ At resonance the circuit behaves as a resistor

$$R_p = \frac{\left(\frac{L}{C}\right)^2}{R} \quad \text{if } R \text{ is small} \Rightarrow R \ll \omega L$$

$$\theta_s = \frac{\omega_0 L}{R}$$

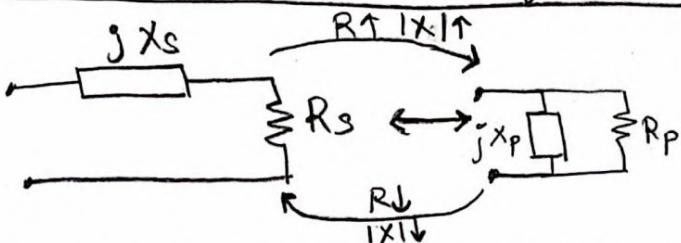→ Series \leftrightarrow Parallel transformations.



$$R_p = \frac{R_s^2 + X_s^2}{R_s}$$

$$X_p = \frac{R_s}{\frac{R_s^2 + X_s^2}{X_s}}$$

$$R_s = R_p \cdot \frac{X_p^2}{R_p^2 + X_p^2}$$

$$X_s = X_p \cdot \frac{R_p^2}{R_p^2 + X_p^2}$$


→ These equations are true at all frequencies however, R, X could become function of frequency.

→ The signs of X_p, X_s remain same \Rightarrow caps remain caps & inductors remain inductors

$$\rightarrow \text{Also, } R_p = R_s(1 + \theta_s^2); L_p = L_s(1 + \frac{1}{\theta_s^2});$$

$$C_s = C_p \left[1 + \frac{1}{\theta_s^2} \right]; R_s = R_p \left[\frac{1}{1 + \theta_s^2} \right]$$

Maximum Power Transfer.

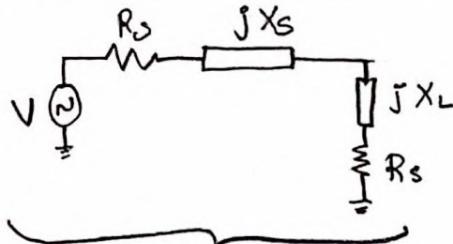

For maximum power

$$Z_L = Z_s^*$$

$$P_{RL} = \text{power delivered to the load} = \frac{V_{RL}^2}{R_L}$$

$$P_{RL} = \frac{V^2}{2} \cdot \frac{R_L}{(R_L + R_s)^2 + (X_s + X_L)^2}$$

To maximize $P_{RL} \Rightarrow \frac{dP_{RL}}{dR_L} = 0 \Rightarrow R_s = R_L \text{ & } \frac{dP_{RL}}{dX_L} = 0 \Rightarrow X_s = -X_L$

$$P_s = \text{power at source}$$


$$P_s = \frac{V^2}{4R_s}$$

$P_{RL\max}$ = max. power available at load

$$P_{RL\max} = \frac{V^2}{8R_s}$$

Matching.

→ Transformers :-

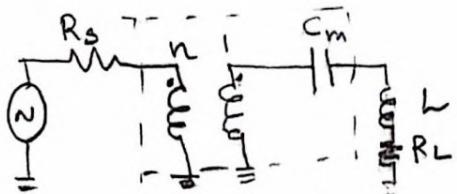

→ C_m resonates with L at operating frequency

$$n^2 = \frac{R_s}{R_L}$$


→ Transformers are lossy, large & have poor coupling ($K < 1$).

Z-match

→ We can transform the impedance looking at load using an LC network that is also not lossy.

- ① → Find the δ that gives the desired R_p, R_s based on $R_p = R_s(1+\delta^2)$.
- ② → Change δ by adding an inductor or capacitor to the desired δ .
- ③ → Find L/C to resonate with X_L .

Downconverter ($R_s < R_L$)

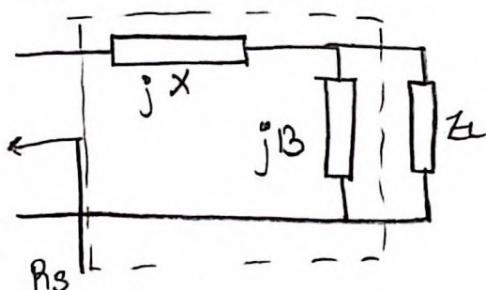

$$\delta = \frac{X_L \pm \sqrt{\frac{R_L}{R_s} \sqrt{R_L^2 + X_L^2} - R_L R_s}}{R_L^2 + X_L^2}$$

$$X = \frac{1}{\delta} + \frac{X_L R_s}{R_L} - \frac{R_s}{\delta R_L}$$

$$X = \omega L \text{ or } -\frac{1}{\omega C}$$

$$\delta = -\frac{1}{\omega L} \text{ or } \omega C$$

$X \Rightarrow +ve \Rightarrow$ inductor.

$\delta \Rightarrow +ve \Rightarrow$ capacitor.


$X, \delta \Rightarrow +ve \Rightarrow$ low pass.

$X, \delta \Rightarrow -ve \Rightarrow$ High pass.

→ Prefer lowpass! It is easier to make inductors b/w 2 nodes & caps b/w a node & ground. Also these give higher δ .


→ Also choose based on DC bias.

Upconverter ($R_s > R_L$)

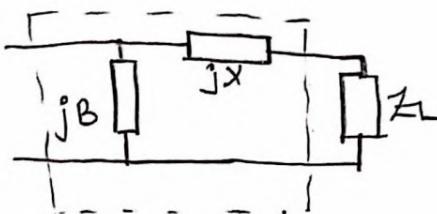

$$X = \pm \sqrt{R_L(R_s - R_L)} - X_L$$
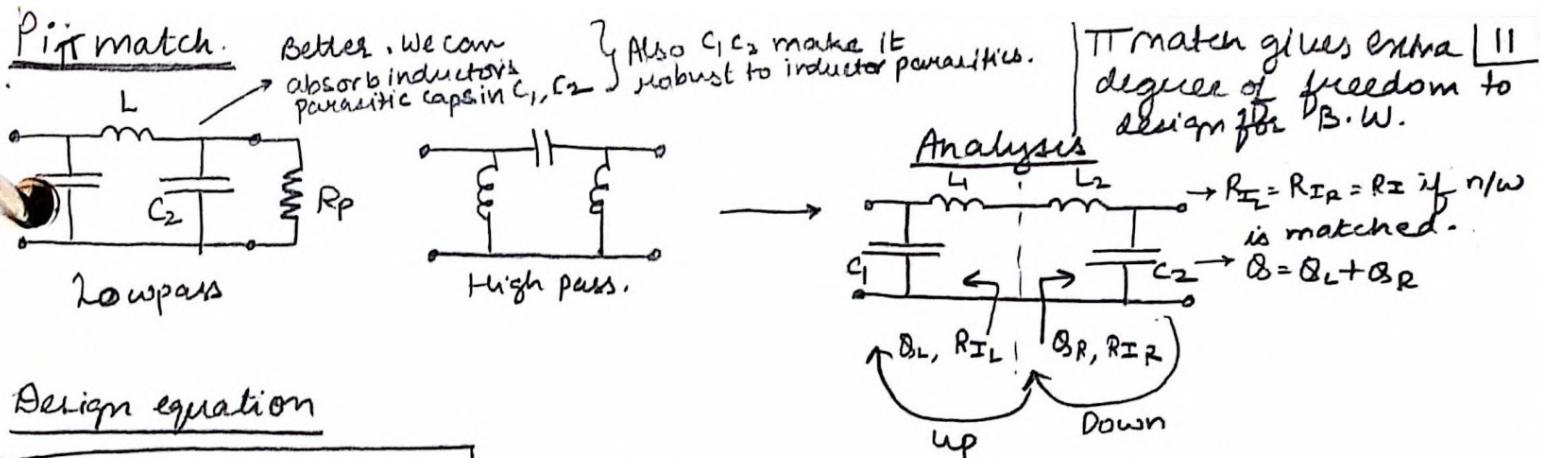
$$\delta = \pm \sqrt{\frac{R_s - R_L}{R_s}}$$



Design equation

$$Q = \sqrt{\frac{R_{in}}{R_I}} - 1 + \sqrt{\frac{R_P}{R_I}} - 1$$

$$\rightarrow Q_R \sqrt{\frac{R_P}{R_I}} = \frac{\omega_0 L_2}{R_I}$$


$$Q_L = \sqrt{\frac{R_{in}}{R_I}} - 1$$

Design RHS, LHS as 2 L-matches w.r.t R_I .

A more approximate approach

$$R_I = \left(\frac{\sqrt{R_{in}} + \sqrt{R_P}}{Q^2} \right)^2; \quad C_1 = \frac{Q_L}{\omega_0 R_{in}}; \quad C_2 = \frac{Q_R}{\omega_0 R_P}; \quad L = \frac{Q R_I}{\omega_0}$$

T-match

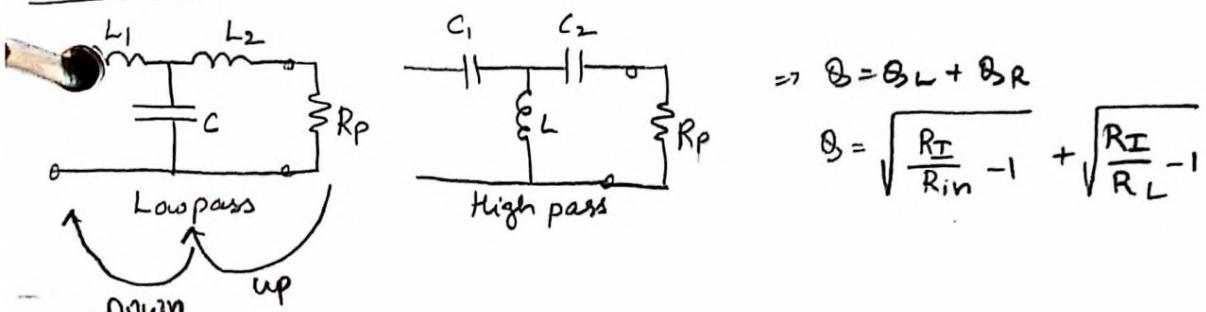


→ For lossless matching networks, matching from one side guarantees matching from other side.

→ How well can we design the matching network?




$$T = \frac{Z_{in} - R_s}{Z_{in} + R_s} \quad |T| = 0 \Rightarrow \text{perfect match}$$

Reflection coeff. $|T| = 1 \Rightarrow \text{perfect mismatch.}$

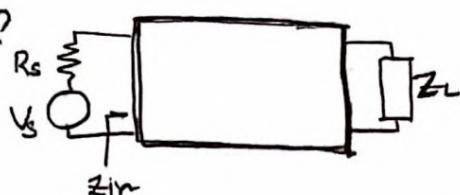


→ We could match at one frequency but how much Bandwidth could we get?

→ It is limited by the Bode-Fano limit. $\int_0^\infty \ln \frac{1}{|T(j\omega)|} d\omega < \frac{\pi}{RC}$ for parallel RC

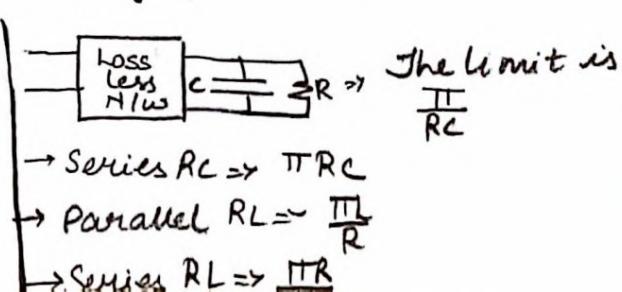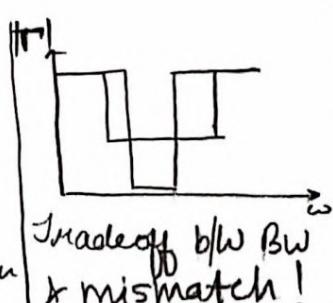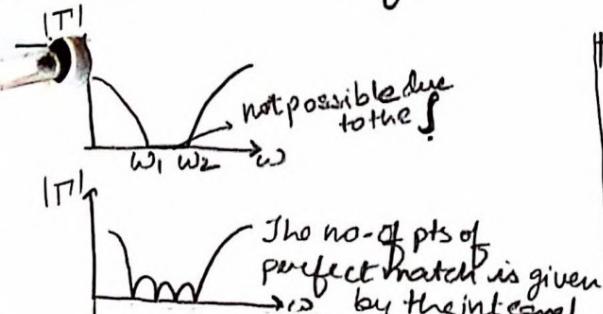

Integrated Passives on CMOS

→ CMOS has 5-12 metal layers

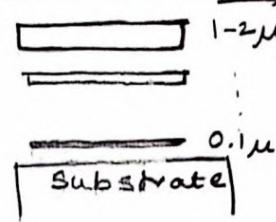

passivation (SiO_2)

- Metals:
 - Al → low ρ
→ Easy manufacture
→ ↑ Adherence to SiO_2
 - Cu → Better conductivity
→ Hard manufacture
→ Better electro-migration.

Electromigration: How much current a metal can carry per unit width. Very strong E fields move ions & change the lattice structure forming holes which ↑ E fields → positive feedback!

Effect ① Penetration of E-fields.:

Wave equation inside a dielectric: $\nabla^2 E = j\omega\mu(\sigma + j\omega\epsilon)E$. $\frac{\sigma}{\omega\epsilon} \rightarrow$ loss tangent

Assuming $\sigma \gg \omega\epsilon \Rightarrow$ loss is very small $\Rightarrow \nabla^2 E = j\omega\mu(\sigma E)$ { $E = E_Z$ }

How does E field change with x ? $\frac{d^2 E}{dx^2} = j\omega\mu\sigma E_Z = T^2 E_Z \Rightarrow E_Z = E_0 e^{-Tx} + c/e^{+Tx}$
since $E_Z \rightarrow 0$

$E_Z(x=0) = E_0$
 $\Rightarrow E_Z = E_0 e^{-Tx} \Rightarrow$ Exponential decay inside the metal.

$$T = \sqrt{j\omega\mu\sigma} = \frac{1+j}{8}$$

$$\delta = \sqrt{\frac{1}{\pi f \mu \sigma}}$$


Skin depth: Depth at which E_0 drops by e .

Function of material and frequency!

→ At high frequencies thick metals are pretty useless.

Effect ② Current flows where M field is stronger.

Proximity effects:- Two adjacent wires!

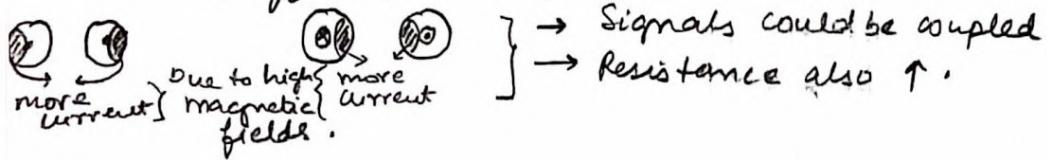

f	Cu	Al
1GHz	2μ	2.6μ
10G	0.65μ	0.82μ
100G	0.2μ	0.26μ

{ values! }

Capacitors: ① Lateral field caps are better: Better control & tolerance, ↓ substrate coupling.
② Fractal caps for ↑ area but very hard to simulate/model.
③ MIM cap: High ϵ insulator, low breakdown voltage, Cap. density is high $\approx \frac{1fF}{\mu\text{m}^2}$
④ Lateral field vertical bars:- Highest density!



Inductors $\rightarrow L \propto \frac{1}{\sqrt{w}}$ \Rightarrow Thinner \Rightarrow $L \propto T$; $0.2\text{nH} \leq \frac{L_{\text{on chip}}}{L_{\text{spiral}}} \leq 20\text{nH}$; $\frac{\geq 20\text{nH}}{\leq 0.2\text{nH}} \Rightarrow$ Bondwire vs Tx. lines.

→ How spirals since inner loops have ↓ φ flux & high loss.

→ Rule of Thumb:



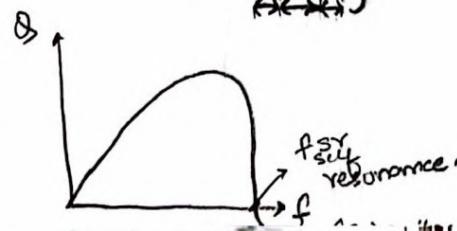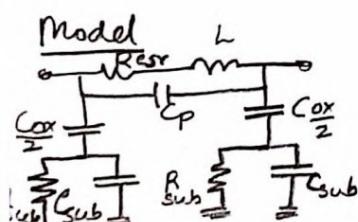
Keep these three distances same for good Q & L




- Shield patterns are used to prevent substrate coupling and break early currents in the shield. Also ↑ Q.
- Floating shields are better but harder to model.

Smith Charts

L10

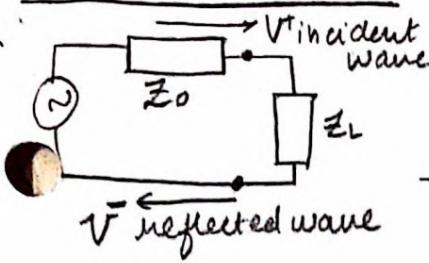
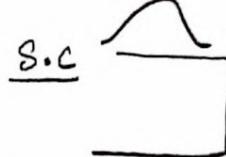
$$T = \frac{V^-}{V^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$$




180° phase shift
since boundary condition is $V=0$.

$$\rightarrow Z_L = Z_0 \Rightarrow T = 0 \\ \text{matched}$$

$$\rightarrow Z_L = 0 \Rightarrow T = -1$$
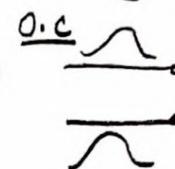
$$\rightarrow Z_L = \infty \Rightarrow T = +1$$





0° phase shift since $I=0$

$$T = \frac{Z_L - 1}{\frac{Z_0}{Z_L} + 1} = \frac{\gamma_L - 1}{\gamma_L + 1}$$



Smith chart is a graphical representation of this bilinear transform.


$$T = T_r + j T_i \quad , \quad Z_L = \gamma_L + j \chi_L \Rightarrow T_r = \frac{\gamma_L^2 + \chi_L^2 - 1}{(\gamma_L + 1)^2 + \chi_L^2} \quad \gamma_L = \frac{1 - T_r^2 - T_i^2}{(1 - T_r)^2 - T_i^2} \\ T_i = \frac{2 \chi_L}{(\gamma_L + 1)^2 + \chi_L^2} \quad \chi_L = \frac{2 T_i}{(1 - T_r)^2 - T_i^2}$$

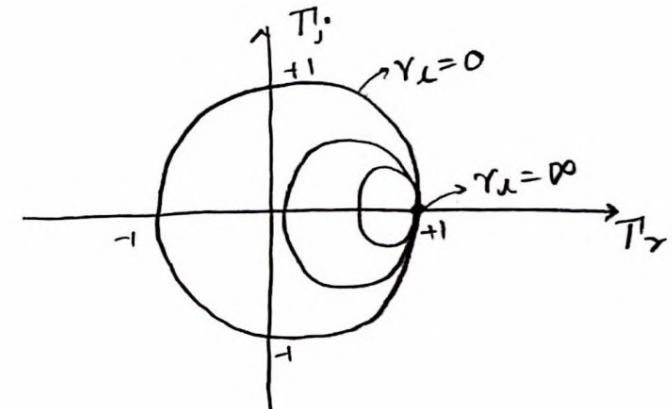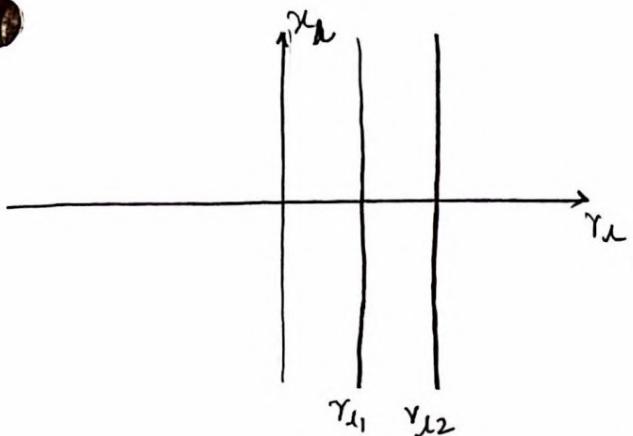→ Constant γ_L & eliminate $\chi_L \Rightarrow \left(T_r - \frac{\gamma_L}{1 + \gamma_L}\right)^2 + T_i^2 = \left(\frac{1}{1 + \gamma_L}\right)^2 \rightarrow \text{circle.}$



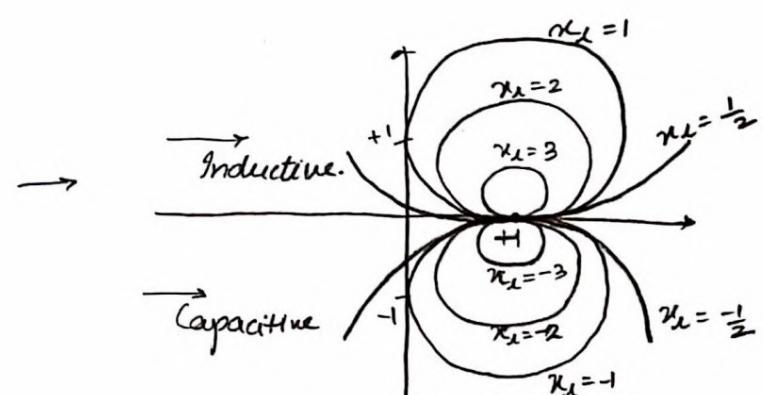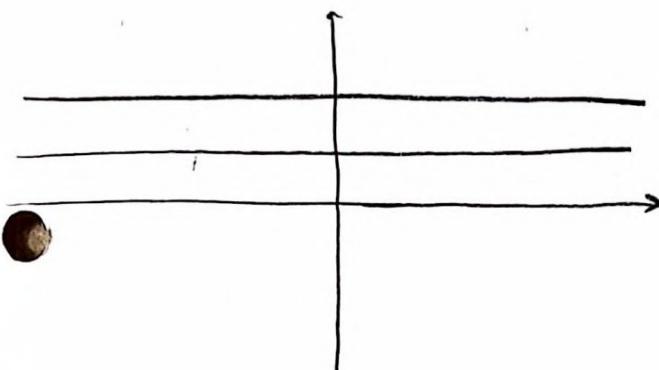→ Constant χ_L & eliminate $\gamma_L \Rightarrow (T_r - 1)^2 + (T_i - \frac{1}{\chi_L})^2 = (\frac{1}{\chi_L})^2$



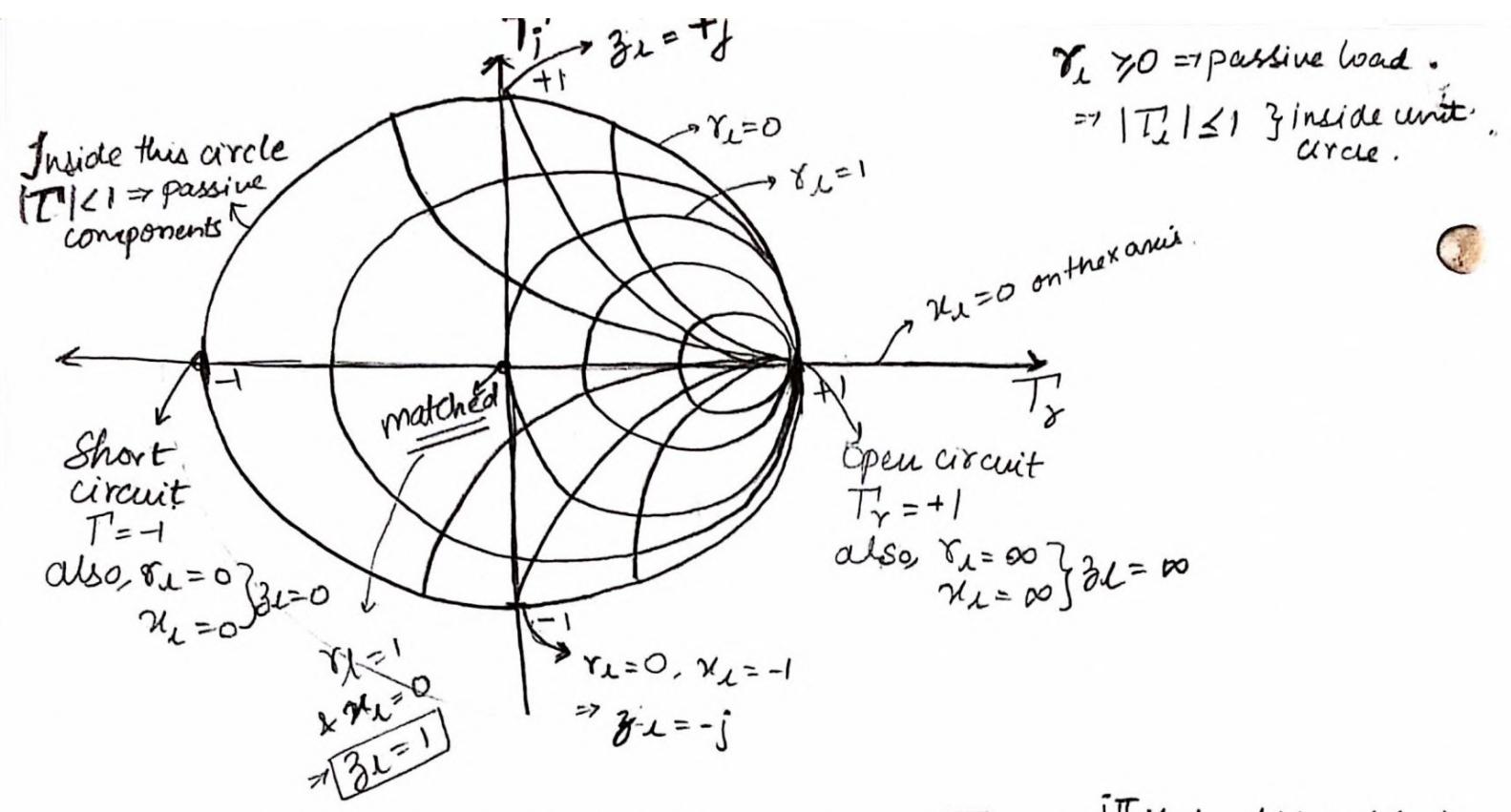


$r_L \geq 0 \Rightarrow$ passive load.

$\Rightarrow |T_x| \leq 1$ if inside unit circle.

- Smith chart for admittance $y = \frac{1}{Z}$: $T = e^{j\pi y - 1} \frac{y+1}{y-1}$ flipped & mirror w.r.t origin.
- To find admittance find impedance and mirror w.r.t origin.
- $x_L \uparrow \Rightarrow$ ~~series~~ in parallel (with value $\frac{wL}{Z_0}$)
- $x_L \downarrow \Rightarrow$ ~~parallel~~ in series ($\frac{-1}{wCZ_0}$)
- $b_L \uparrow \Rightarrow$ ~~parallel~~ in parallel ($\frac{-Z_0}{\omega L}$)
- $b_L \downarrow \Rightarrow$ ~~parallel~~ in series ($\frac{1}{\omega C Z_0}$)
- Impedance Smith chart → normalize !!
- Admittance Smith chart
- Find where Z_L is on the chart & move to the centre by moving on constant r_L lines and getting to the $r_L = 1$ circle.
- $Z_L = r_L + j x_L$
- $y_L = g_L + j b_L$
- $x_L = jwL$ (or) $\frac{-j}{\omega C}$
- $b_L = jwC$ (or) $\frac{j}{\omega L}$
- $r_L + \text{ve} \Rightarrow$ inductor in series ; $r_L - \text{ve} \Rightarrow$ capacitor in series.
- $b_L + \text{ve} \Rightarrow$ capacitor in parallel ; $b_L - \text{ve} \Rightarrow$ inductor in parallel.
- $C_{\text{parallel}} = \frac{b}{2\pi f Z_0}$
- $C_{\text{series}} = \frac{-1}{2\pi f Z_0 x}$
- $L_{\text{parallel}} = \frac{-Z_0}{2\pi f b}$
- $L_{\text{series}} = \frac{x Z_0}{2\pi f}$

S - Parameters

Transmission lines

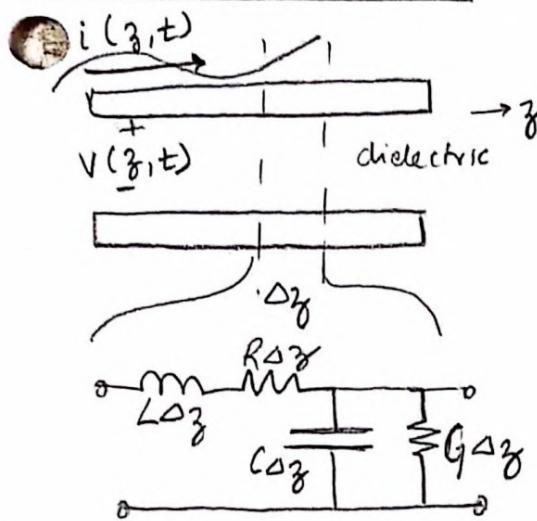

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$


$$I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{+\gamma z}$$

$$\gamma = \sqrt{(R+j\omega L)(G+j\omega C)}$$

$$\frac{V_0^+}{I_0^+} = -\frac{V_0^-}{I_0^-} = Z_0 = \frac{R+j\omega L}{\gamma}$$

↑ characteristic impedance.

Scattering parameters

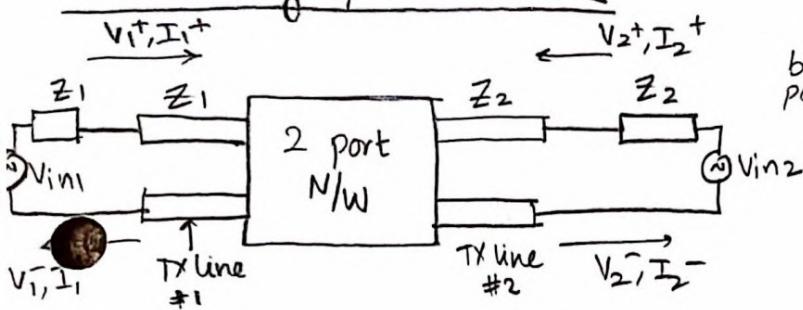

$$\frac{V_1^-}{\sqrt{Z_1}} = S_{11} \frac{V_1^+}{\sqrt{Z_1}} + S_{12} \frac{V_2^+}{\sqrt{Z_2}}$$

$$\frac{V_2^-}{\sqrt{Z_2}} = S_{21} \frac{V_1^+}{\sqrt{Z_1}} + S_{22} \frac{V_2^+}{\sqrt{Z_2}}$$

$$S = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix}$$

Oftenly used notation: $a_1 \triangleq \frac{V_1^+}{\sqrt{Z_1}}$; $b_1 \triangleq \frac{V_1^-}{\sqrt{Z_1}}$

$$a_2 \triangleq \frac{V_2^+}{\sqrt{Z_2}}; b_2 \triangleq \frac{V_2^-}{\sqrt{Z_2}}$$

$$\rightarrow S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{\substack{V_2^+ = 0 \\ (V_{in2} = 0)}} = T_{L1}$$

V_2^- may be $\neq 0$.

$\rightarrow S_{11}$ is a measure of λp mismatch.

$$\rightarrow S_{21} = \left. \sqrt{\frac{Z_1}{Z_2}} \frac{V_2^-}{V_1^+} \right|_{\substack{V_2^+ = 0 \\ V_{in2} = 0}}$$

$\rightarrow S_{21}$ is a measure of gain from P1 to P2

$$\rightarrow S_{22} = \left. \frac{V_2^-}{V_2^+} \right|_{\substack{V_1^+ = 0 \\ V_{in1} = 0}} = T_{L2}$$

$$\rightarrow S_{12} = \left. \sqrt{\frac{Z_2}{Z_1}} \frac{V_1^-}{V_2^+} \right|_{\substack{V_1^+ = 0 \\ V_{in1} = 0}}$$

Eg 0 - Amplifier that is matched!



$$S = \begin{bmatrix} 0 & \text{Small} \\ 3.16/\sqrt{0} & 0 \end{bmatrix}$$


due to delay, some phase is added.

→ How can we measure from value of sources?

$$\left. \begin{array}{l} V_1 = V_{1+} + V_{1-} \\ I_1 = I_{1+} + I_{1-} = \frac{1}{Z_1} (V_{1+} - V_{1-}) \end{array} \right\} \text{Tr-L equations} \Rightarrow \begin{aligned} V_{1+} &= \frac{1}{2} (V_1 + Z I_1) \\ \Rightarrow V_{1+} &= \frac{1}{2} V_{in1} \end{aligned}$$

$$\Rightarrow S_{21} = 2 \sqrt{\frac{Z_1}{Z_2}} \cdot \frac{V_{2-}}{V_{in1}} \quad \left| \begin{array}{l} V_{2+} = 0 \\ (V_{in2} = 0) \end{array} \right.$$

$$S_{12} = 2 \sqrt{\frac{Z_2}{Z_1}} \cdot \frac{V_{1-}}{V_{in2}} \quad \left| \begin{array}{l} V_{1+} = 0 \\ (V_{in1} = 0) \end{array} \right.$$

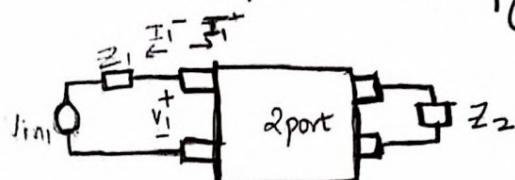

But what is the physical meaning of S parameters?

Available source power: $P_{av} = \frac{|V_{in1}|^2}{4Z_1} = |a_{11}|^2$ since $a_{11} \equiv \frac{V_{1+}}{Z_1} = \frac{V_{in1}}{2\sqrt{Z_1}}$


Average power delivered to P1: $P \equiv \frac{1}{2} \operatorname{Re} \{ V_1 I_1 \} \Rightarrow P_1 = \frac{1}{2} \operatorname{Re} \{ |a_{11}|^2 - |b_{11}|^2 + (a_{11} b_{11} - a_{11} b_{11}^*) \}$

$$\Rightarrow P_1 = \frac{1}{2} |a_{11}|^2 - \frac{1}{2} |b_{11}|^2 \Rightarrow \boxed{\frac{1}{2} |b_{11}|^2 = \frac{P_{av} - P_1}{2}} \quad \begin{array}{l} \text{Power that is actually delivered} \\ \downarrow \text{Reflected power} \quad \downarrow \text{max. power} \\ \text{delivered to load} \\ \text{when matched} \end{array}$$

$$\Rightarrow S_{11}^2 = \frac{|b_{11}|^2}{|a_{11}|^2} = \frac{\text{Reflected power at } P_1}{\text{Max. available source power that can be delivered to a matched load at } P_1}$$

$$S_{21} = \frac{b_2}{a_1} \quad \left| \begin{array}{l} a_2 = 0 \\ V_{2+} = 0 \end{array} \right. \Rightarrow \boxed{\frac{V_2}{\sqrt{Z_2}}} \quad \left| \begin{array}{l} V_{2-} \\ \Rightarrow |S_{21}| = \frac{|V_2|^2}{2 Z_2} \\ \frac{V_{in1}}{2\sqrt{Z_1}} \quad a_2 = 0 \\ V_{2+} = 0 \end{array} \right. \quad \frac{1}{2} \frac{|V_{in1}|^2}{4Z_1}$$

$$\Rightarrow |S_{21}|^2 = \frac{\text{power delivered to load at } P_2}{\text{Max. available power at the source that can be delivered to a matched load}}$$

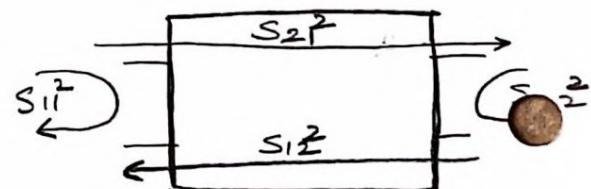

→ S_{22}, S_{12} are vice versa.

Properties of S parameters

(1) P_i = Total power delivered to port i .

$P_i = \frac{1}{2} (a_i^* a_i - b_i^* b_i)$

power incident power reflected

Total power delivered to n port network

$$\sum_{i=1}^n P_i = \sum_{i=1}^n \frac{1}{2} (a_i^* a_i - b_i^* b_i)$$


$$P_{\text{total}} = \frac{1}{2} [a]^T [a]^* - \frac{1}{2} [b]^T [b]^* \quad \text{where } [a] = \begin{bmatrix} a_1 \\ a_2 \\ \vdots \\ a_n \end{bmatrix}; [b] = \begin{bmatrix} b_1 \\ b_2 \\ \vdots \\ b_n \end{bmatrix}$$

We know $[b] = [s] [a]$

$$\Rightarrow P_{\text{tot}} = \frac{1}{2} [a]^T [a]^* - \frac{1}{2} [a]^T [s]^T [s]^* [a]^* = \frac{1}{2} [a]^T \underbrace{[U]}_{n \times n}_{\text{unit matrix}} - [s]^T [s]^* [a]^*$$

\Rightarrow If network is lossless $P_{\text{tot}} = 0$

$\Rightarrow [s]^T [s]^* = [U]$

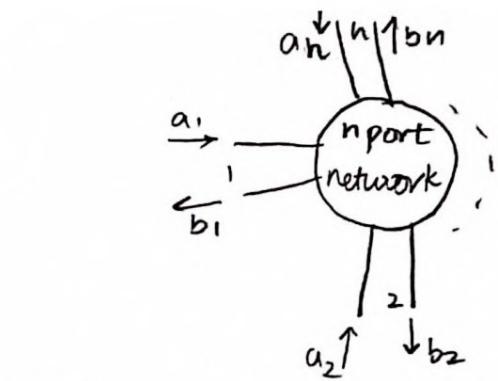

For lossless networks, S is a unitary matrix.

In two port:

$$\left. \begin{array}{l} |S_{11}|^2 + |S_{21}|^2 = 1 \\ |S_{21}|^2 + |S_{22}|^2 = 1 \\ S_{11} S_{12}^* + S_{21} S_{22}^* = 0 \end{array} \right\} \begin{array}{l} \text{all power goes from } P_1 \text{ to } P_2 \\ \text{All 3 conditions} \\ \text{must be} \\ \text{satisfied} \end{array}$$

$\xrightarrow{\text{all power goes from } P_1 \text{ to } P_2}$

② For a reciprocal network: $[S]^T = [S] \Rightarrow S_{12} = S_{21}$ $\boxed{\Rightarrow}$

③ For a matched network $S_{11} = 0 \Rightarrow \boxed{\begin{bmatrix} 0 & * \\ * & 0 \end{bmatrix}}$

Note:- A 3 port network cannot be matched, lossless & reciprocal at once.

Useful trig identities.

$$\cos A \cos B = \frac{1}{2} [\cos(A-B) + \cos(A+B)] \quad \left| \quad \sin A \cos B = \frac{1}{2} (\sin(A+B) + \sin(A-B)) \right.$$

$$\sin A \sin B = \frac{1}{2} [\cos(A-B) - \cos(A+B)]$$

$$\cos^3 A = \frac{3}{4} \cos A + \frac{1}{4} \cos 3A$$

$$\cos^2 A = \frac{1 + \cos 2A}{2}$$

$$\sin A + \sin B = 2 \sin\left(\frac{A+B}{2}\right) \cos\left(\frac{A-B}{2}\right)$$

$$\sin^3 A = \frac{3}{4} \sin A - \frac{\sin 3A}{4}$$

Noise

Math problems

① $\bar{x} = E\{x\} = \int_{-\infty}^{\infty} x \cdot f_x(x) dx = \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} x(t) dt$

$\bar{x^2} = E\{x^2\} = \int_{-\infty}^{\infty} x^2 \cdot f_x(x) dx = \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} x^2(t) dt$

Variance


$$\sigma_x^2 = E\{(x - \bar{x})^2\} = \bar{x^2} - \bar{x}^2$$

Stationary :- Statistical properties do not change with time

Ergodic :- Ensemble average = Time average.

Autocorrelation

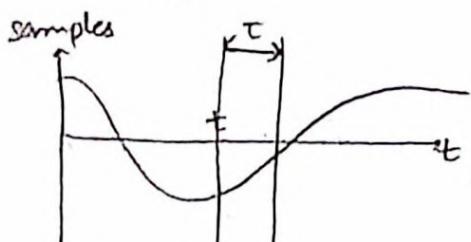② $R(\tau) = \int_{-\infty}^{\infty} x^*(t) x(t+\tau) dt$




→ move this borders from \rightarrow to \leftarrow or small size. Then simulate the two points are.

→ For a stationary R.P it is only a function of τ


For a random variable or stationary R.P

→ $R(\tau) = E\{x^*(t) x(t+\tau)\}$

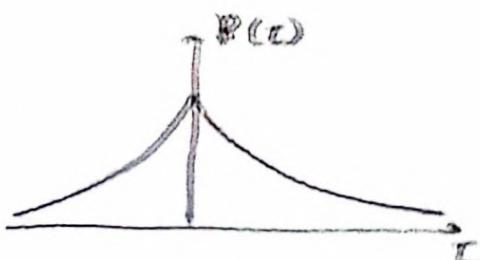

→ Wideband R.V \Rightarrow narrow R(τ) since it quickly becomes dissimilar as τ increases.

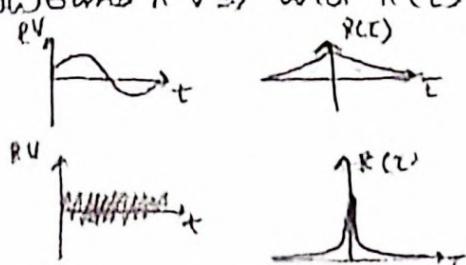→ III Narrowband R.V \Rightarrow wide R(τ)



Power Spectral Density.

$$S_x(f) = F.T \left\{ R_x(\tau) \right\} \rightarrow \frac{\overline{V^2}}{\Delta f} \propto \frac{1}{\Delta f}$$

→ $\int_{-\infty}^{\infty} S_x(f) df$ gives total power. Note $\int_{f_1}^{f_2} S_x(f) df$ gives total power in band f_1 to f_2 .
 for $f < 0$ freq counts

→ For LTI Systems

$$S_y(f) = S_x(f) |H(j\omega)|^2$$

From fluctuation dissipation & Equipartition theorems:

$$S_v(f) = 4kT R \quad \text{- Thermal noise of a resistor}$$

Noise correlation

Correlation factor

$$\rho_{xy} = \frac{E\{xy^*\}}{\sqrt{E\{x^2\} E\{y^2\}}} \stackrel{\text{cross correlation}}{=} \frac{E\{xy^*\}}{|x| |y|} \quad \therefore \sqrt{E\{|x^2(t)|}} = |x(t)|_{\text{rms}}$$

$$0 \leq \rho \leq 1 \quad \left. \begin{array}{l} \text{uncorrelated} \\ \text{fully correlated} \end{array} \right\} \quad \text{If } \rho_{xy}=0 \Rightarrow P_{\text{tot}} = P_x + P_y = \frac{V_x^2}{R} + \frac{V_y^2}{R}$$

$$\text{If } \rho_{xy}=1 \Rightarrow P_{\text{tot}} \neq P_x + P_y$$

$$\begin{aligned} V_{\text{tot}} &= \frac{V_x + V_y}{\sqrt{\frac{(V_x + V_y)^2}{R}}} \\ \Rightarrow P_{\text{tot}} &= \frac{(V_x + V_y)^2}{R} \end{aligned}$$

Noise Types

I Thermal Noise

$$R \xrightarrow{\text{noise}} \xrightarrow{\text{noise}} R \xrightarrow{\frac{V_n^2}{\Delta f} = \frac{4kT}{R}}$$

$$\xrightarrow{\text{noise}} R \xrightarrow{\frac{V_n^2}{\Delta f} = 4kTR}$$


Example ① Available noise power

$$\xrightarrow{\frac{V_n^2}{\Delta f}} R \parallel R \Rightarrow P = \frac{V_n^2}{4R} = \frac{4kTR}{4R} = \underline{\underline{KT}}$$

$$= \underline{\underline{4\pi \times 10^{-29} \frac{600}{1000}}}$$

$$P_{\text{answ}} = -174 \text{ dBm}$$

Example ②

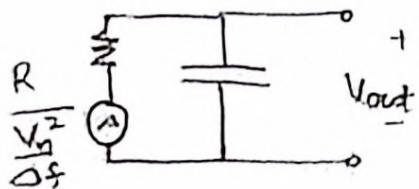

$$V_{\text{out}} = V_n \frac{1}{RSC + j\omega}$$

$$\frac{V_{\text{out}}^2}{\Delta f} = \frac{V_n^2}{\Delta f} \left| \frac{1}{RSC + j\omega} \right|^2$$

$$\frac{V_n^2}{\Delta f} = \left[\frac{1}{1 + \frac{R^2 C^2 \omega^2}{1}} \right]$$

$$\frac{V_{\text{out}}^2}{\Delta f} = \frac{4kTR}{1 + R^2 C^2 \omega^2}$$

$$\frac{V_{\text{out}}^2}{\Delta f} = \frac{4kTR}{1 + R^2 C^2 \omega^2} = \frac{\frac{kT}{C}}{1 + \frac{R^2 C^2 \omega^2}{1}}$$

Independent of R

Solution ①

Equipartition theorem.

$$\frac{1}{2} kT = \frac{1}{2} C V_{\text{out}}^2$$

$$\Rightarrow \frac{V_{\text{out}}^2}{\Delta f} = \frac{kT}{C}$$

Avg charge on capacitor


$$Q_0 = \sqrt{\frac{kT}{C}} \cdot C = \sqrt{kTC}$$

→ Lowpass \Rightarrow As R, BWF = power is constant

$$\boxed{\frac{V_{\text{out}}^2}{\Delta f}}$$

→ In reality thermal noise is white upto $f \leq \frac{kT}{h}$. Beyond we need to use the Bose-Einstein distribution

Noise in 2 port

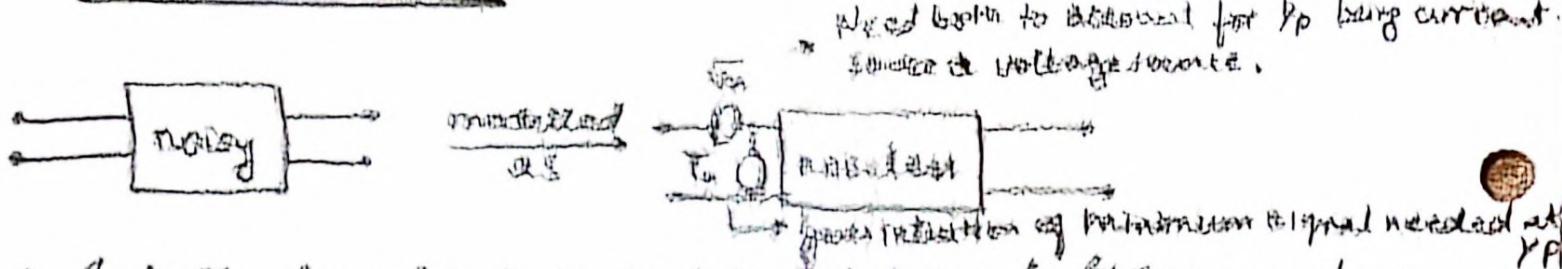


> To fully characterize noise in circuit we need 4 parameters here.

$|V_{nl}|$, $|I_{nl}|$ and R_c for port of P_{in} .

> Let $\bar{I}_n = \bar{I}_x + \bar{I}_o \rightarrow$ fully correlated
uncorrelated

$$\bar{I}_n + \bar{V}_n$$

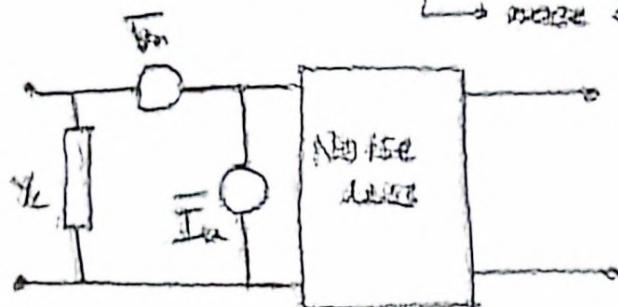↳ noise correlation extensiveness (Averaging linearity)



$$P_{n,in} = \frac{\bar{I}_n \bar{V}_n}{|\bar{I}_n| |\bar{V}_n|}$$

$$V_c = \frac{\bar{I}_n \bar{V}_n}{|\bar{V}_n|^2}$$

$$\therefore \bar{I}_n \bar{V}_n = \bar{I}_n \bar{V}_n^* \\ \text{or } V_c = \frac{\bar{I}_n \bar{V}_n^*}{|\bar{V}_n|^2} \cdot V_c$$

$$Y_c = P_{n,in} \frac{|\bar{I}_n|}{|\bar{V}_n|}$$

Noise Factor (F) → How much noise is circuit adding.

$$F = \frac{SNR_{xp}}{ENR_{xp}} = \frac{S/N}{G_S / G_{N3+da}} \quad 1 + \frac{Na}{ENR} \gg 1 \quad \text{--- (1)}$$

$$F = \frac{\text{noise power out at } \omega_p \text{ (total)}}{\text{noise power out at } \omega_p \text{ due to input}}$$

$$= F_1 + \frac{F_2 - 1}{G_1} + \dots + \frac{F_{n-1}}{G_1 G_2 \dots G_{n-1}}$$

for cascaded stages.

$$= [F_1, G_1] \parallel [F_2, G_2] \parallel \dots \parallel [F_n, G_n] =$$

G is power gain

i.e. first stage should be LNA

Noise Figure (NF)

$$NF = 10 \log F \approx 0dB$$

Noise temperature (T_e)

→ N_a (noise of amplifier) is modelled as a resistor at temperature T_e

$$N_a = (K T_e \Delta f) G.$$

$$\Rightarrow T_e = \frac{N_a}{k G \Delta f} \quad \text{--- (2)}$$

From (1) and (2) $F = 1 + \frac{T_e}{T}$

$$(F-1)T = T_e$$


↑
actual temp. ↑
Equivalent noise temp.

Noise measure (Noise v/s. gain)

low \Rightarrow good. $M = \frac{F-1}{1 - \frac{1}{G}}$


* Noise matching

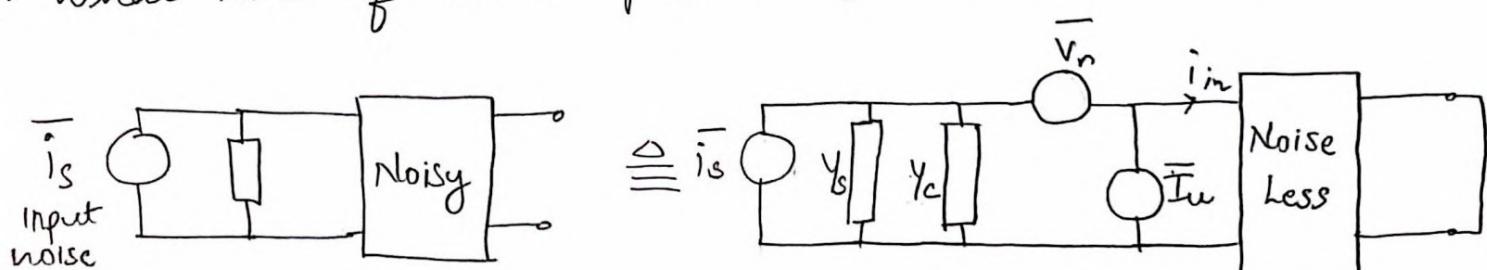→ What kind of source impedance gives minimum noise at O/P.



→ Short o/p since noise is independent of Z_{out}

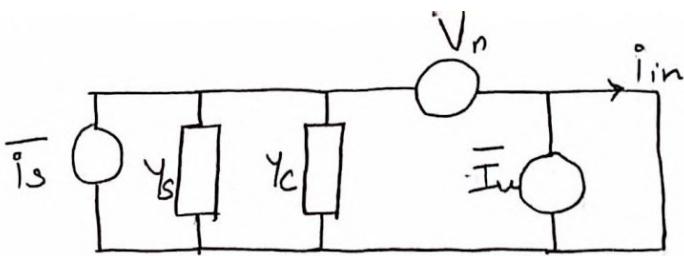→ Circuit is noisier so we can ignore it for our noise analysis



$$F = \frac{\overline{I_{in}^2}_{total}}{\overline{I_{in}^2} Y_p} = \frac{|I_s + I_u + (Y_c + Y_s)V_n|^2}{\overline{I_s^2}}$$

$$= \frac{i_s^2 + I_u^2 + (Y_c + Y_s)^2 V_n^2 + 0 + 0 + 0}{\overline{I_s^2}}$$

$$F = 1 + \frac{\overline{I_u^2} + |Y_s + Y_c|^2 \overline{V_n^2}}{\overline{I_s^2}}$$

Equivalent noise impedances

$$\overline{V_n^2} = 4kT R_n \Delta f \quad \text{defined as a source for } V_n$$

$$\overline{I_u^2} = 4kT G_u \Delta f \quad \text{source for } I_u$$

$$\overline{I_s^2} = 4kT G_s \Delta f \quad \text{real part of } Y_s = G_s + jB_s$$

$$Y_s = G_s + jB_s$$

$$Y_c = G_c + jB_c$$

$$\Rightarrow F = 1 + \frac{G_u + |Y_c + Y_s|^2 R_n}{G_s}$$

$$F = 1 + \frac{G_u + [(G_c + G_s)^2 + (B_c + B_s)^2] R_n}{G_s}$$

→ Find Y_s optimum to minimize F .


Set, $\frac{dF}{dB_s} = 0$ & $\frac{dF}{dG_s} = 0$ and solve.

$$\Rightarrow B_s = -B_c = B_{\text{opt}}$$

$$G_s = \sqrt{\frac{G_u}{R_n} + G_c^2} = G_{\text{opt}}$$

$$F_{\text{min}} = 1 + 2 R_n (G_{\text{opt}} + G_c) \quad \boxed{= 1 + 2 \sqrt{R_n G_u}}$$
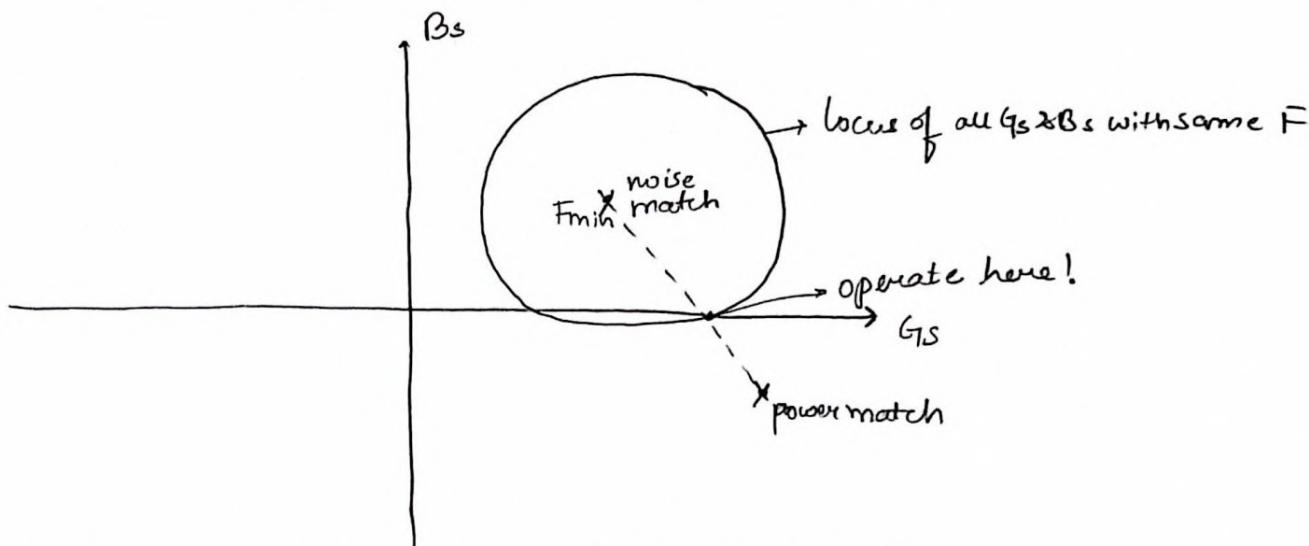
$$F = F_{\text{min}} + \frac{R_n}{G_s} \left[(G_s - G_{\text{opt}})^2 + (B_s - B_{\text{opt}})^2 \right]$$




→ Tradeoff between noise match and power match.

→ There is an optimum input Y_s admittance to get best noise factor!

$$R_n = \frac{V_n^2 / \Delta f}{4kT}$$

$$G_u = \frac{I_u^2 / \Delta f}{4kT}$$

Note on transformer matching

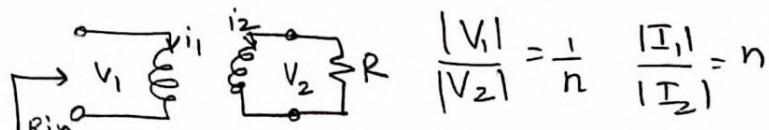

$$\Rightarrow R_{\text{in}} = \frac{R}{n^2}$$

Noise sources in MOSFET


1) Thermal noise of channel :

$$\boxed{\overline{i_{nd}^2} = 4kT \gamma g_{do} \Delta f}$$

at the drain

$$g_{do} = \frac{\partial I_d}{\partial V_{gs}} \Big|_{V_{ds}=0} = \mu_n C_o x \frac{W}{L} (V_{gs} - V_{th})$$

conductance
of channel

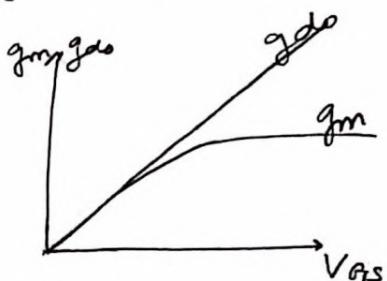

$g_{do} = g_m$ for long channel devices.

$$g_{do} = \frac{g_m}{\alpha} \text{ for short channel where } \alpha \leq 1$$

→ g_m & g_{do} are fundamentally different.


→ γ models variation due to CLM

$\gamma = 1$ ($V_{ds} = 0$) channel is flat.

$\gamma = \frac{2}{3}$ (saturation & long channel)

$\gamma = 2-6$ (saturation & short channel) since charge moves in a discrete lattice & tunneling occurs.

2) Gate noise :

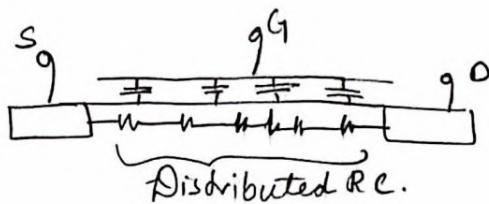

$$g_g = \frac{\omega^2 C_{gs}^2}{5g_{do}}$$

$$\Rightarrow \boxed{\overline{i_{hg}^2} = 4kT \delta g_g \Delta f} \quad \delta = 2\gamma$$


→ g_g & g_{do} are correlated ⇒ correlation factor 'c'

$$c = \frac{\overline{i_{hg} i_{hd}^*}}{|\overline{i_{hg}}| |\overline{i_{hd}}|} \approx -j 0.395$$

⇒ Flicker noise (not much in BJT) (24)

$$\overline{i_{nd}^2} = \frac{k}{f} \cdot \frac{q_m^2}{WL C_{ox}^2} \Delta f \quad \text{not white}$$

↳ Empirical model

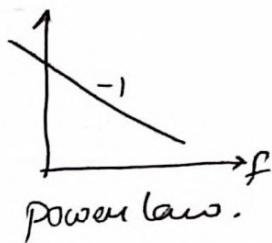

4) Shot noise (more in BJT not MOSFET)


→ Discrete transitions across barrier when current flows.

→ It is a poisson R.V


$$\begin{aligned} S_i(0) &= \lambda \xrightarrow{\text{rate of events}} |(\psi(0)|^2 \xrightarrow{\text{weight of one event}} \\ &= 2 \left(\frac{I}{q} \right) q^2 \\ &= 2 I q \end{aligned}$$

$$\Rightarrow \boxed{\overline{i_n^2} = 2qI\Delta f}$$

Noise model of MOSFET


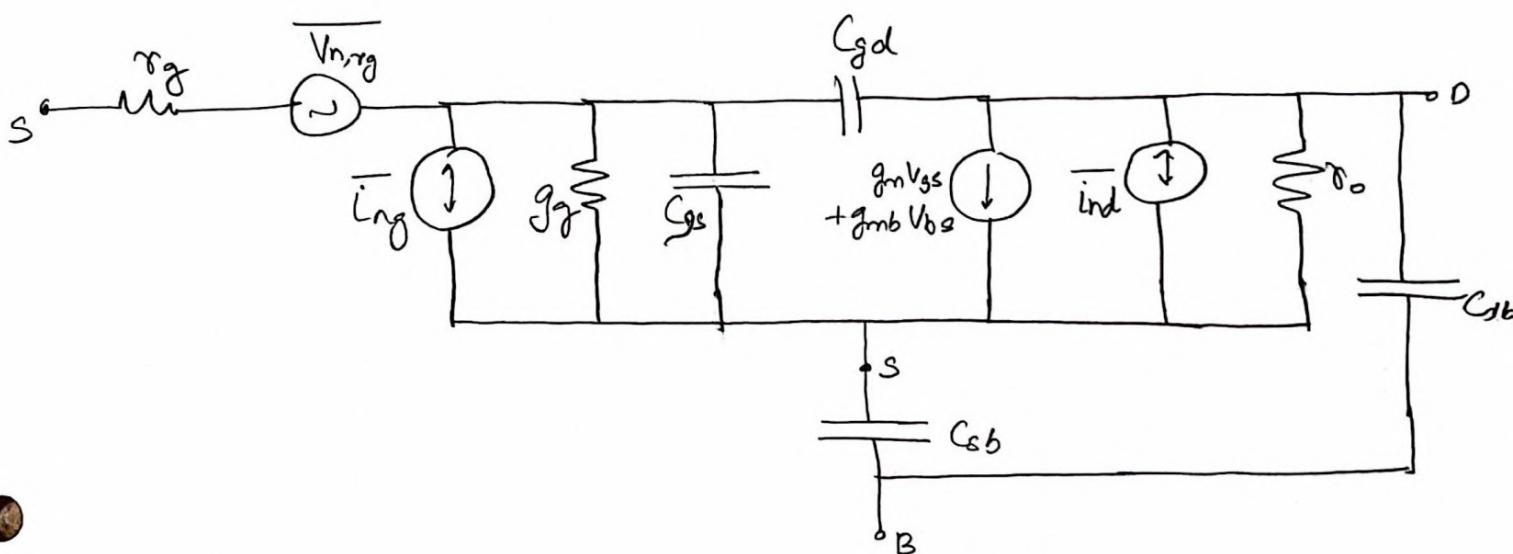


Noise example

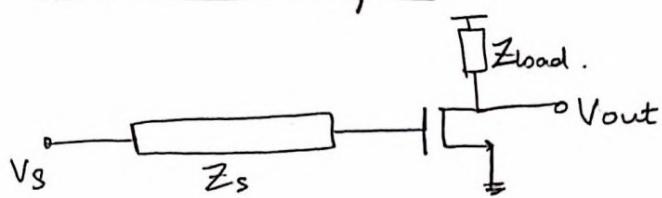

Find: $\bar{V}_n, \bar{I}_n, Y_c$

Solution: Ignoring G_{dL}, r_o, Z_L, g_g

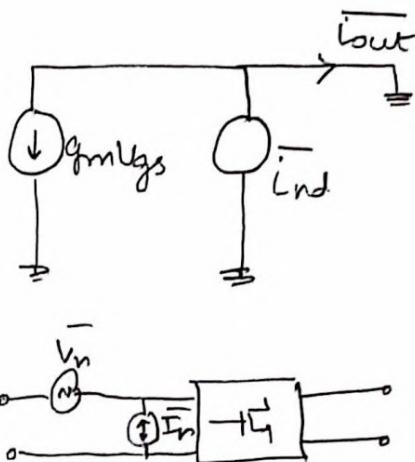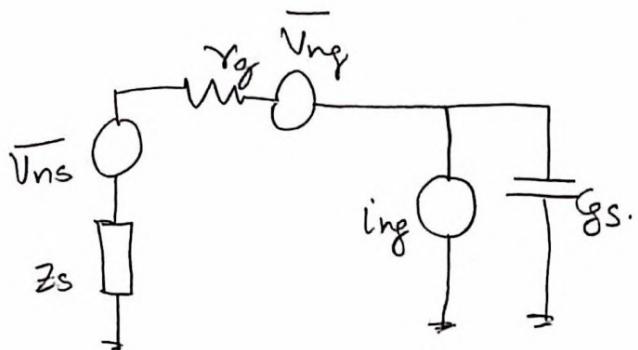


To find \bar{V}_n : Short input

To find \bar{I}_n : Open input

$\bar{V}_n = ?$

$$i_{out} = \bar{I}_n + g_m V_{gs} = \bar{I}_n + g_m \bar{I}_{ng} \cdot \frac{\gamma_g}{\gamma_g G_{sS} + 1} + g_m \bar{V}_{ng} \cdot \frac{1}{\gamma_g G_{sS} + 1} \quad \text{---(1)}$$

Replace all noise sources by \bar{V}_n

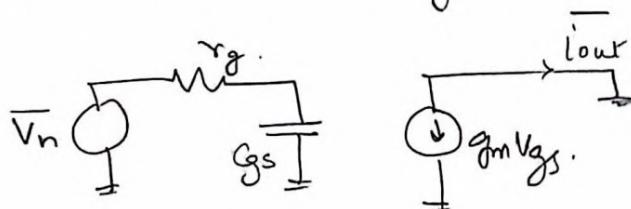

$$i_{out} = g_m V_{gs} = g_m \bar{V}_n \cdot \frac{1}{\gamma_g G_{sS} + 1} \quad \text{---(2)}$$

$$\underline{(1) = (2)} \Rightarrow$$

$$\Rightarrow \bar{V}_n = \frac{\gamma_g G_{sS} + 1}{g_m} + \bar{I}_n + \gamma_g \bar{I}_{ng} + \bar{V}_{ng}$$

$$\text{Hence } \bar{I}_n = \bar{I}_{ng} + \frac{S G_s}{g_m} \bar{I}_{nd}$$

Note: While finding \bar{V}_n, \bar{I}_n use mean values of noise sources. For noise factor use 2nd moment (power)

But, \bar{V}_n , \bar{I}_n are correlated

$$\bar{I}_n = \bar{I}_{in} + Y_C \bar{V}_n$$

$$\overline{\bar{I}_n \cdot V_n^*} = 0 + Y_C |\bar{V}_n|^2$$

$$\Rightarrow Y_C = \frac{\overline{\bar{I}_n \bar{V}_n^*}}{|\bar{V}_n|^2}$$

Assume $\gamma_g = 0$ (make it easier)

$$\bar{V}_n^* = \frac{1}{g_m} \bar{I}_{ind}^* \quad \left\{ \text{since } \overline{V_n V_n^*} = |V_n|^2 = \frac{1}{g_m^2} |\bar{I}_{ind}|^2 \right. \\ \Rightarrow \bar{V}_n = \frac{1}{g_m} \bar{I}_{ind}$$

$$\bar{I}_n = \frac{S_{GS}}{g_m} \bar{I}_{ind} + \bar{I}_{ing}$$

$$\Rightarrow \overline{\bar{I}_n V_n^*} = \left(\frac{S_{GS}}{g_m} \bar{I}_{ind} + \bar{I}_{ing} \right) \left(\frac{1}{g_m} \bar{I}_{ind}^* \right)$$

$$= \frac{S_{GS}}{g_m^2} \overline{|\bar{I}_{ind}|^2} + \frac{1}{g_m} \overline{\bar{I}_{ing} \bar{I}_{ind}^*}$$

$$Y_C = \frac{\overline{\bar{I}_n V_n^*}}{|\bar{V}_n|^2} = \frac{\frac{S_{GS}}{g_m^2} \overline{|\bar{I}_{ind}|^2} + \frac{1}{g_m} \overline{\bar{I}_{ing} \bar{I}_{ind}^*}}{\frac{1}{g_m^2} \cdot \overline{|\bar{I}_{ind}|^2}}$$

$$= S_{GS} + g_m \frac{\overline{\bar{I}_{ing} \bar{I}_{ind}^*}}{\overline{|\bar{I}_{ind}|^2}}$$


$$= Sg_{ds} + g_m \frac{\frac{i_{ng}}{i_{nd}} \frac{i_{nd}}{i_{nd}}} {\sqrt{i_{nd}^2} \sqrt{i_{nd}^2}} \cdot \sqrt{\frac{i_{ng}^2}{i_{nd}^2}}$$

$$= Sg_{ds} + g_m \cdot C \cdot \sqrt{\frac{i_{ng}^2}{i_{nd}^2}} \quad \text{where } C = \frac{\frac{i_{ng}}{i_{nd}} \frac{i_{nd}}{i_{nd}}}{\frac{i_{ng}}{i_{nd}} \frac{i_{nd}}{i_{nd}}}$$

$$\Rightarrow Y_c = Sg_{ds} + g_m \cdot c \sqrt{\frac{\delta g_g}{\delta g_{d0}}}$$

$$Y_c = j\omega g_{ds} \left[1 - \frac{g_m}{g_{d0}} |C| \sqrt{\frac{\delta}{5\delta}} \right]$$

Example :

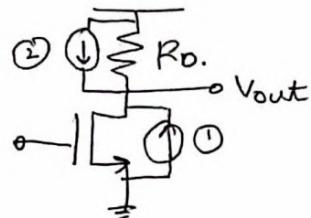

$$\begin{aligned} Y &= \frac{2}{3} \\ i_{ng} &= 0 \\ g_g &= 0 \\ g_m - g_{d0} &= 0 \end{aligned}$$

Find $\overline{V_n^2}$? Method ①

$$\frac{\overline{V_{nout}^2}}{\Delta f} = \left(4KT \cdot \frac{2}{3} g_m + \frac{k}{C_{ox}WL} \frac{1}{f} g_m^2 + \frac{4KT}{R_d} \right)$$

$$\frac{\overline{V_{nin}^2}}{\Delta f} = \frac{\overline{V_{nout}^2}}{\Delta f} = \frac{\overline{V_{n,out}^2}}{\Delta f (g_m R_d)^2}$$


$$\frac{\overline{V_{nin}^2}}{\Delta f} = 4KT \frac{2}{3} g_m + \frac{k}{C_{ox}WL} \cdot \frac{1}{f} + \frac{4KT}{g_m^2 R_d}$$

Method ② From previous example.

$$\overline{V_n^2} = \frac{1}{g_m^2} \overline{i_{nd}^2} = \frac{1}{g_m^2} \cdot 4KT \cdot \frac{2}{3} g_m + \frac{k}{C_{ox}WL} \frac{1}{f} g_m^2 + \frac{4KT}{R_d}$$

(Assuming $g_m = g_{d0}$)


$$\overline{V_n^2} = \frac{4KT \cdot 2}{3g_m} + \frac{k}{C_{ox}WL} \frac{1}{f} + \frac{4KT}{g_m^2 R_d}$$

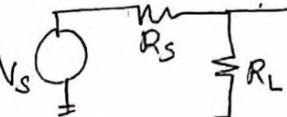Example : 

$$\overline{V_{n,tot}^2} = \overline{V_{n_{R_s}}^2} \left(\frac{R_L}{R_L + R_s} \right)^2 + \overline{V_{n_{R_L}}^2} \left(\frac{R_s}{R_s + R_L} \right)^2 + \overline{V_{n_{out}}^2} (\gamma_p) = \overline{V_{n_{R_s}}^2} \left(\frac{R_L}{R_L + R_s} \right)^2$$

$$\Rightarrow F = 1 + \frac{R_s}{R_L}$$

Example:

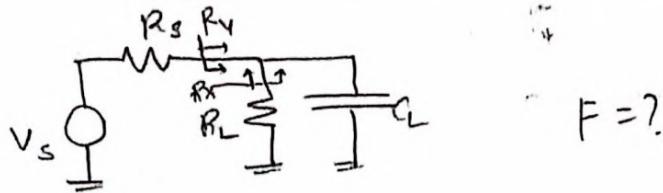

$$F = ?$$

$$R_x = R_s \parallel \frac{1}{sC_L} = \frac{R_s}{1 + R_s s C_L}$$

$$R_y = \frac{R_L}{1 + s R_L C_L}$$

$$\overline{\frac{V_{out}^2}{df}}_1 = \left| \frac{R_x}{R_x + R_L} \right|^2 \overline{V_{nL}^2} \quad \text{--- (1)}$$

$$\overline{\frac{V_{out}^2}{df}}_2 = \left| \frac{R_y}{R_y + R_s} \right|^2 \overline{V_{ns}^2}$$

From (1) :

$$\frac{R_x}{R_L + R_x} = \frac{\frac{R_s}{1 + s R_s C_L}}{\frac{R_s}{1 + s R_s C_L} + R_L} = \frac{R_s}{(R_s + R_L) + s R_L R_s C_L}$$

$$\Rightarrow \left| \frac{R_x}{R_L + R_x} \right|^2 = \left(\frac{R_s}{R_s + R_L} \right)^2 \left| \frac{1}{1 + s \frac{R_L R_s C_L}{R_s + R_L}} \right|^2 = \left(\frac{R_s}{R_s + R_L} \right)^2 \left\{ \frac{1}{1 + \omega^2 \frac{R_s R_L C_L}{R_s + R_L}} \right\}$$

$$\Rightarrow \overline{\frac{V_{out}^2}{df}}_1 = \left(\frac{R_s}{R_s + R_L} \right)^2 \left\{ \frac{1}{1 + f^2 \left(\frac{2\pi R_s R_L C_L}{R_s + R_L} \right)^2} \right\} 4kT R_L$$

$$\int \frac{1}{1 + \alpha^2 x^2} dx = \tan^{-1} \alpha x$$

$$\Rightarrow \overline{\frac{V_{out}^2}{df}}_1 = 4kT R_L \cdot \left(\frac{R_s}{R_s + R_L} \right)^2 \int_0^\infty \left\{ \frac{1}{1 + f^2 \left(\frac{2\pi R_s R_L C_L}{R_s + R_L} \right)^2} \right\} df$$

$$= 4kT R_L \cdot \left(\frac{R_s}{R_s + R_L} \right)^2 \cdot \frac{R_s + R_L}{2\pi R_s R_L C_L} \cdot \frac{\pi}{2}$$


$$\overline{\frac{V_{out}^2}{(load)}} = \frac{kT}{C_L} \left[\frac{R_s}{R_s + R_L} \right]$$

$$\left\{ NF = \frac{\frac{kT}{R_L}}{\frac{kT}{C_L} \left[\frac{R_L}{R_s + R_L} \right]} = \boxed{1 + \frac{R_s}{R_L}}$$

Same as before


$$\overline{\frac{V_{out}^2}{df}}_2 = \frac{kT}{C_L} \left[\frac{R_L}{R_s + R_L} \right]$$

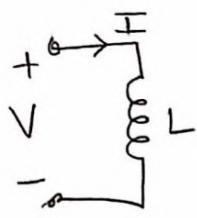Quick note of passive (inductors) for midterm



$$\phi = LI$$

$$V = SLI$$

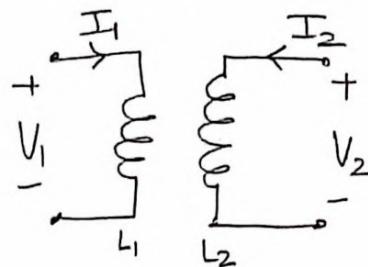

$$\phi_1 = L_1 I_1 + M I_2$$

$$\phi_2 = M I_1 + L_2 I_2$$

$$\Rightarrow [\phi] = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} [I]$$

$$V_1 = SL_1 I_1 + SM I_2$$

$$V_2 = SMI_1 + SL_2 I_2$$

$$\text{Coupling factor} = \frac{M}{\sqrt{L_1 L_2}} = K$$

$= 1 \Rightarrow$ perfect coupling.

$$\Rightarrow \begin{bmatrix} \phi_1 \\ \phi_2 \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = S \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

How to find NF?

Step ① Small signal model.

Step ② Draw out all noise current sources.

Step ③ Short the output since NF is independent of load (It is a ratio)


Step ④ Find contribution of each independent noise source
(null all other independent sources)

$$\frac{I_{tot+Zload}^2}{I_{pp+Zload}^2}$$

Step ⑤ Add powers to find $\overline{I_{out,tot}^2}$ & add amplitudes if correlated.

Step ⑥ $NF = \frac{\overline{I_{out,tot}^2}}{\overline{I^2}}$.

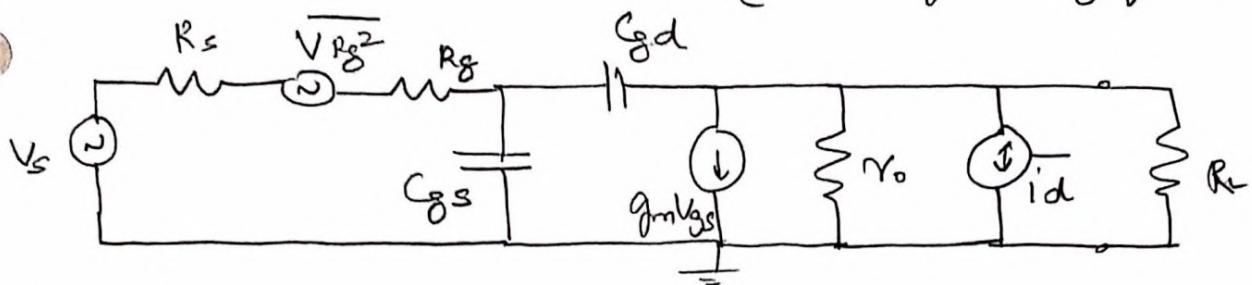FET Noise Factor (using a different style)



$$R_S: \overline{V_S^2} = 4KT R_S \Delta f$$

$$R_S: \overline{V_g^2} = 4KT R_S \Delta f$$

$$R_{ch}: \overline{i_d^2} = 4KT \gamma g_{ds} \Delta f$$

$$R_L: \overline{i_L^2} = 4KT G_L \Delta f$$

Input noise is drawn as voltages since we can just multiply them by g_m and they would show up at 0% at low frequencies since C_{gs} would be open.

At low freq :- C_{gs} is open $\Rightarrow \overline{V_S} \times \overline{V_g}$ show up as ($\times g_m$) at $\overline{i_{out}}$.

$$\Rightarrow \overline{i_o^2} = \overline{i_d^2} + \overline{i_L^2} + (\overline{V_g^2} + \overline{V_S^2}) g_m^2$$

$$\Rightarrow F = 1 + \frac{\overline{V_g^2}}{\overline{V_S^2}} + \frac{\overline{i_d^2} + \overline{i_L^2}}{g_m^2 \overline{V_S^2}}$$

$$F = 1 + \frac{R_S}{R_S} + \frac{g_{ds} \gamma + G_L}{R_S g_m^2}$$

$g_m = g_{ds}$ (long channel)

$$\Rightarrow F = 1 + \frac{R_S}{R_S} + \frac{\gamma}{g_m R_S} + \frac{G_L G_S}{g_m^2}$$

Higher frequencies: We know, $g_m = \frac{i_{out}}{V_{gs}}$ (since i_d shunts directly at i_{out} since source is g_m)

$$\text{Let } G_m = \frac{V_{gs}}{V_s}$$

$$\Rightarrow \frac{i_{out}}{V_s} = \frac{i_{out}}{V_{gs}} \times G_m = g_m \cdot G_m.$$

\Rightarrow To refer the input noise sources directly to output current scale g_m by G_m which is just a voltage divider!

$$G_m = \frac{\frac{1}{j\omega g_s}}{\frac{1}{j\omega g_s + R_s + R_g}} = \frac{1}{1 + j\omega g_s (R_s + R_g)}$$

$$\Rightarrow |G_m|^{-2} = 1 + \omega^2 g_s^2 (R_s + R_g)^2$$

$$\text{From earlier, } F = 1 + \frac{R_g}{R_s} + \frac{g_{do} \gamma + G_L}{R_s g_m^2} \xrightarrow{\text{scale this.}}$$

$$F = 1 + \frac{R_g}{R_s} + \frac{g_{do} \gamma + G_L}{R_s g_m^2} [|G_m|^{-2}]$$

$$\Rightarrow F = 1 + \frac{R_g}{R_s} + \frac{g_{do} \gamma + G_L}{R_s g_m^2} (1 + \omega^2 g_s^2 (R_s + R_g)^2).$$

Assume $G_L \rightarrow 0$ and $1 + \omega^2 g_s^2 (R_s + R_g)^2 \rightarrow \omega^2 g_s^2 (R_s + R_g)^2$
 $\Rightarrow (R_s \text{ is large})$

$$F = 1 + \frac{R_g}{R_s} + \frac{\gamma}{\omega^2 g_m^2 R_s} \cdot (\omega^2 g_s^2 (R_s + R_g)^2) \quad (\because \frac{g_m}{g_{do}} = \omega)$$

$$\text{Assume } R_s \gg R_g \Rightarrow F = 1 + \frac{\gamma}{\omega^2 g_m^2 R_s} \left\{ \omega^2 g_s^2 R_s^2 \right\}$$

$$\Rightarrow F = 1 + \frac{\gamma}{\omega^2} \left(\frac{1}{g_m^2 R_s} \right)$$

$$\omega_T^2 = \frac{g_m^2}{g_s^2}$$

MOSFET NOISE - REVIEW/SUMMARY

$$Y_C = G_C + jB_C$$

$$\alpha = \frac{g_{fm}}{g_{ds}} = 1 \text{ (for long channel)}$$

$$Y_S = G_S + jB_S$$

$$\bar{I}_n = \bar{I}_u + Y_C \bar{V_n}$$

$\xrightarrow{*} G_C \approx 0$

$\xrightarrow{*} B_C = \omega C_{GS} \left[1 - \alpha |C| \sqrt{\frac{8}{5\gamma}} \right]$ from Y_C

$\xrightarrow{*} R_n = \frac{\gamma}{\alpha} \cdot \frac{1}{g_{fm}} \rightarrow \left\{ \begin{array}{l} \text{Equivalent noise impedance } R_n = \frac{\bar{V_n}^2 / \Delta f}{4kT} \\ R_n = \frac{1}{g_{fm}^2} \cdot \frac{4kT \gamma g_{do}}{4kT} \\ = \frac{\gamma g_{do}}{g_{fm}^2} = \frac{\gamma}{g_{fm} \alpha} \end{array} \right.$

$\xrightarrow{*} G_u = \frac{\delta \omega^2 C_{GS}^2 (1 - |C|^2)}{5 g_{do}}$

$\left\{ \begin{array}{l} \bar{I}_{ng}^2 = \overline{(I_{ngc} + I_{ngu})^2} \\ = 4kT \delta g_{gg} |C|^2 \Delta f \\ + 4kT \delta g_{gg} (1 - |C|^2) \Delta f \\ \Rightarrow \bar{I}_{ngu}^2 = 4kT \delta g_{gg} (1 - |C|^2) \Delta f \end{array} \right.$

Derivation -

$$G_u = \frac{\bar{I}_{ngu}^2}{4kT \Delta f} = \delta g_{gg} (1 - |C|^2)$$

We know, $g_g = \frac{\omega^2 C_{GS}^2}{15 g_{do}}$

$$\Rightarrow G_u = \frac{\delta \omega^2 C_{GS}^2 (1 - |C|^2)}{5 g_{do}}$$

\Rightarrow Optimum source admittance Y_s can be calculated.

Minimum NF

We Know, $B_{opt} = -B_C$

$$\Rightarrow B_{opt} = -\omega G_S \left(1 - \alpha |C| \sqrt{\frac{\delta}{5\gamma}} \right) \quad \left\{ \begin{array}{l} C = j\sqrt{\frac{5}{32}} \text{ for} \\ (\text{long channel}) \end{array} \right\}$$

$$G_{opt} = \sqrt{\frac{g_u}{R_n} + G_C^2} = \alpha \omega G_S \sqrt{\frac{\delta}{5\gamma} (1 - |C|^2)} \quad \begin{array}{l} B_{opt} \text{ is -ve.} \\ \Rightarrow (\text{inductive}) \end{array}$$

$$F_{min} = 1 + 2 R_n (G_{opt} + G_C)$$

$$F_{min} = 1 + \frac{2}{\sqrt{5}} \cdot \frac{\omega}{\omega_T} \sqrt{\delta \gamma (1 - |C|^2)}$$

$$\omega_T = \frac{g_m}{G_S + G_D} \approx \frac{g_m}{G_S}$$

$\Rightarrow \omega_T \uparrow \Rightarrow F_{min} \downarrow$


$\Rightarrow \delta = 0 \Rightarrow F_{min} = 0 \text{ dB}$ (If gate noise was zero).

\Rightarrow If correlation is high b/w gate & drain noise $F_{min} \downarrow$.

\Rightarrow Higher frequency $\Rightarrow F_{min}$ degrades.

LNA Design

Receiver

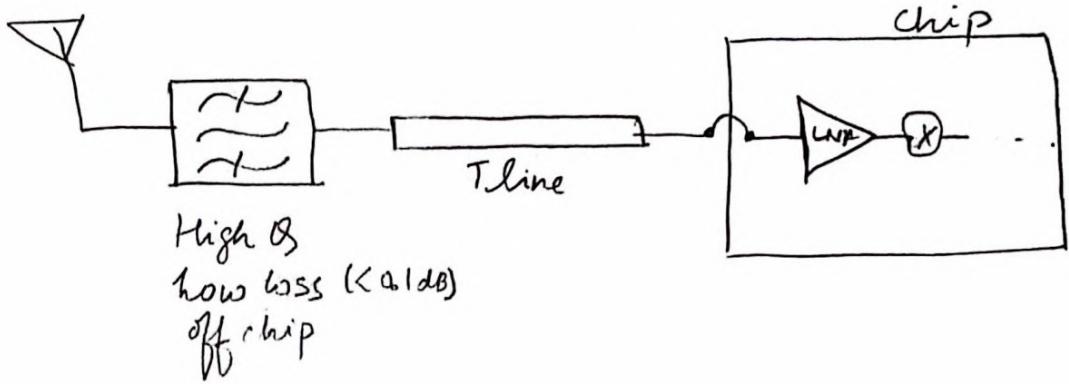


Requirements of LNA

- 1) low NF. (sets the sensitivity)
- 2) High Power gain (Noise of later stages does not matter)
- 3) Linearity (Not so important since signal is small)
- 4) Power consumption
- 5) Area.
- 6) Bandwidth (Not larger than necessary - tradeoffs)
- 7) Dynamic range (Not so important since signal is small)
- 8) Reverse isolation (Protect antenna & don't transmit power back).
- 9) Matching (Power match \otimes Noise match).

→ Obviously we need noise match since it is an LNA (low NF)
But why do we need Power match?

Reason ① :- Input of LNA should match filter (filter is finely tuned).

But there is a more important reason.

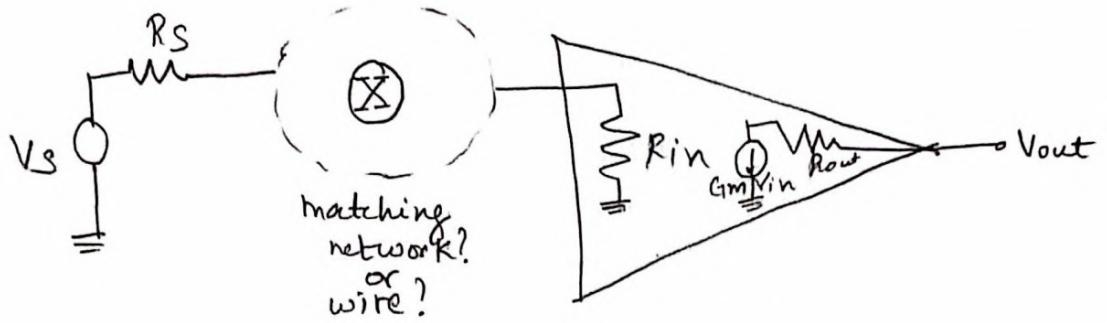

Ideally: $R_{out} = 0$ & $R_{in} = \infty$ to get maximum voltage gain.

Case ①
→ To get maximum voltage gain: X should be short & R_{in} should be high! $\Rightarrow V_{in} = V_s$.

Case ②
→ If we use a power match for X $\Rightarrow P_{in} = \frac{1}{2} P_s$.


So, it looks like case ① is the best approach for voltage gain.

But No.

→ Recall that if we use a matching network the voltage across the reactive components is $\Omega \times V_s$. So using a power match gives higher V_{in} ($V_{in} = \Omega V_s$) ($\Omega = \sqrt{\frac{R_{in}}{R_s}}$).
(proof below) (Across V_{gs} in MOSFET)

→ Also notice $P_{in} = \frac{V_{in}^2}{R_{in}}$ so for maximum V_{in} we need max P_{in} which also suggest power match is best. Current goes down by a factor of Ω (Since power must be conserved) but we care about voltage gain so it's OK.

Proof

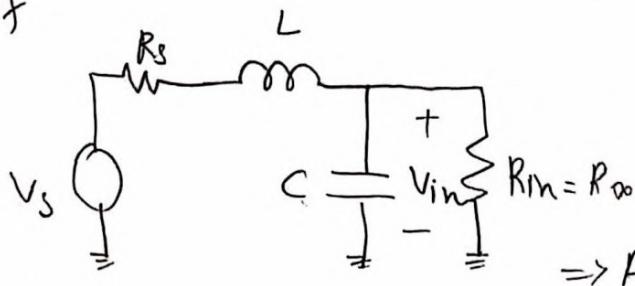

Notice here $V_{in} = \Omega V_s$.


If $R_{in} = \infty$ $\Rightarrow V_{in} = \infty$!

\Rightarrow A power match also gives maximum voltage gain.

Noise match

→ (For a more rigorous treatment notice 'B_{opt} needs to be 137' from inductor so we need L to give best NF) → Calculate L from B_{opt}.

> What Z_s gives best NF?

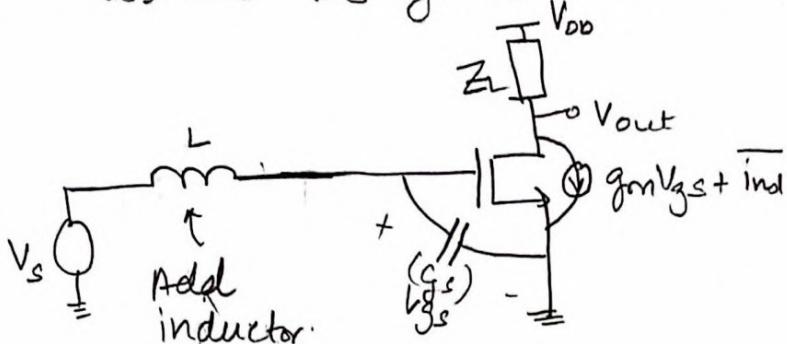

If h_s & g_s resonate,

$$V_{gs} \rightarrow \infty \quad \{R_{gs} = \infty\}$$

$$\Rightarrow g_m V_{gs} \rightarrow \infty$$


⇒ Ind does not matter.

$$\Rightarrow NF = 1, \text{ But } BW = 0.$$

→ ∴ Need something (—m) to resonate with g_s for best NF.

→ In reality we have an R_s.
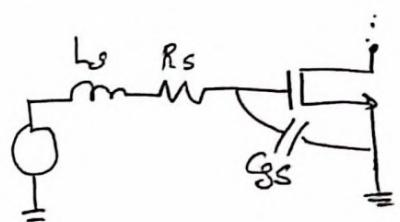
$$\Rightarrow \theta \text{ is finite} \& V_{gs} = \theta V_s.$$



h_s & g_s resonate

$$V_{gs} = \frac{1}{\omega g_s} \cdot \theta = \frac{V_s}{\omega g_s R_s} = \frac{\theta V_s}{\omega g_s R_s} \Rightarrow V_{gs} = \theta V_s.$$

(Derivation on page 31.1)

$$F = 1 + \frac{g_m R_s \theta}{\omega \left(\frac{w_T}{w} \right)^2}$$

Same as CS noise with h_s & g_s since they don't change NF.


Power match

> Simplest approach:

$$R_m = R_s = R.$$

$$\overline{i_{in}^2} = Q_p \text{ noise due to } j_p.$$
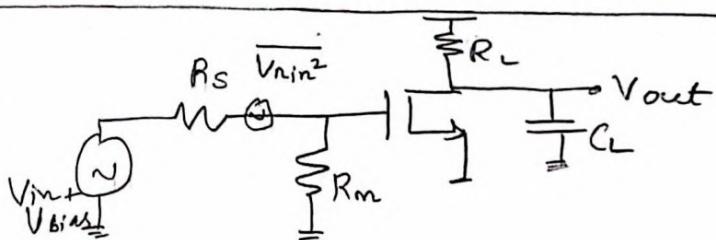
$$= g_m^2 V_{gs}^2 = g_m^2 \left(\frac{1}{2} \overline{V_{in, in}^2} \right) = kT g_m^2 R \Delta f$$




$$\overline{i_{in}^2} = \text{Same due to } R_m = kT g_m^2 R_m \Delta f$$

$$\Rightarrow \overline{i_{in}^2} = 2 kT g_m^2 R \Delta f + 4 kT \delta g_{ds} \Delta f$$


$$\Rightarrow F = 2 + \frac{4\gamma}{\alpha} \frac{1}{g_m R_L} \rightarrow \text{Pretty high } \left\{ \begin{array}{l} \text{Problem is } R_m \\ \text{Even to gain gives } F=2 \end{array} \right.$$

- \Rightarrow Power match with just R_m is bad for noise!
 But we need power match!
 \Rightarrow Before we fix this let's see if common gate can help.

Common Gate

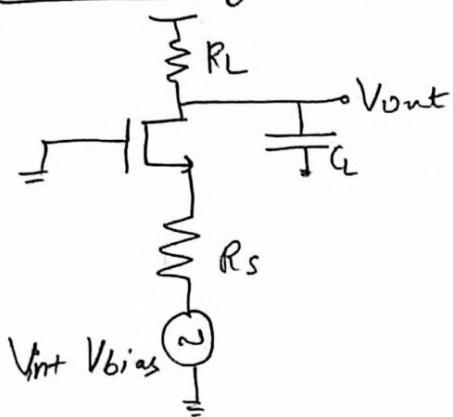
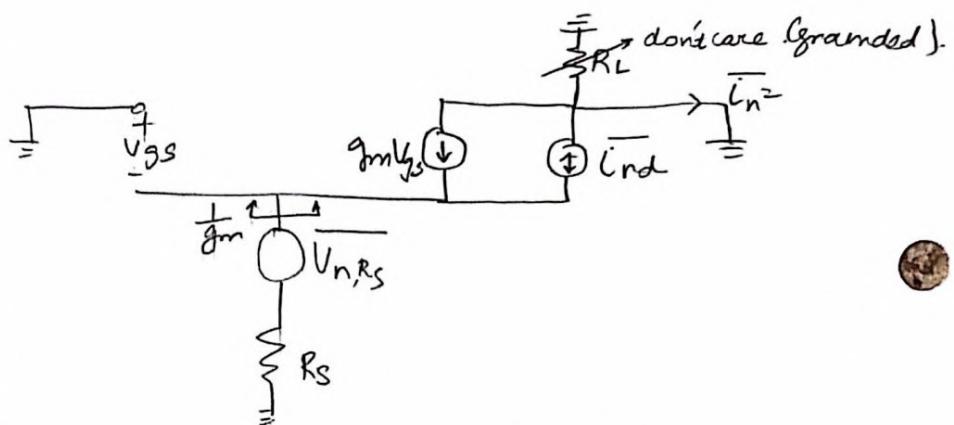
$$\frac{1}{g_m} = R_s \text{ for power match} \Rightarrow g_m R_s = 1$$



Noise due to input R_s :- $\overline{i_{nd}^2}_{sp} = g_m^2 V_{gs}^2 = \frac{g_m^2 \left(\frac{1}{g_m} \right)^2}{\left(R_s + \frac{1}{g_m} \right)} \cdot 4kT R_s \Delta f \underbrace{\overline{V_{n,Rs}^2} \cdot L}_{①}$

$\overline{i_{nd}}$ does not show up directly at O/p due to R_s (since $V_{gs} = 0$).

> What is $\overline{i_n^2}$? Null $\overline{V_{n,Rs}}$:- $V_{gs} = -R_s(g_m V_{gs} + \overline{i_{nd}})$.

$$\overline{i_n} = \overline{i_{nd}} + g_m V_{gs} \text{ where } \overline{i_{nd}^2} = 4kT \gamma g_m R_s \Delta f$$

$$\Rightarrow \overline{i_n^2} = \frac{1}{(1+g_m R_s)^2} \cdot 4kT \gamma g_m R_s \Delta f \quad ②$$


From ① & ② $\Rightarrow F = 1 + \frac{\gamma}{\alpha} \cdot \frac{1}{g_m R_s}$ But $g_m R_s = 1$ (power match)

$$F = 1 + \frac{\gamma}{\alpha} \rightarrow \text{Pretty high } \left\{ \begin{array}{l} \text{Problem is that } g_m R_s = 1 \end{array} \right.$$

Let's go back to CS and see if we can match power¹³⁹ with R_m and still have that noise match.

- > To get best noise match we needed on Ls to resonate with Gs. So we cannot change the circuit there.
 - > To get power match we need to change resistance looking into the gate without changing the noise match circuit that is already there. Is it possible?

Let's look at an example

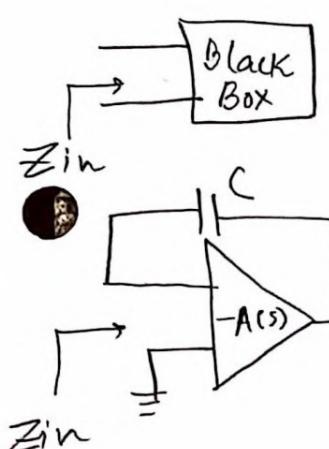

$$Z_{in} = |Z_{in}| e^{j \frac{\pi}{2} \ln} \rightarrow = 0 \text{ to get a resistor.}$$


$$Z_{in} = \frac{1}{1 + A(s)} \quad \text{where } A(s) = A_0 e^{-js\tau} \xrightarrow{\text{due to delay}} \text{-ve phase}$$

$$\Rightarrow Y_{in} = j\omega C (1 + A_0 e^{-j\phi})$$


$$= j\omega C (1 + A_0 \cos \phi) + \underbrace{A_0 \omega C \sin \phi}_{\text{resistor}}.$$


\Rightarrow A delay in the amplifier gives a resistive part to Z_{in} . We can control this resistor by controlling delay.


> Going back to our amplifier.

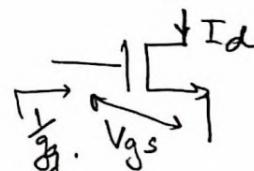


In vectors.

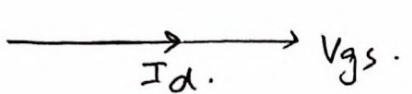 V_{gs} . g_m is real. (Only C_{gs} exists) at low frequencies.

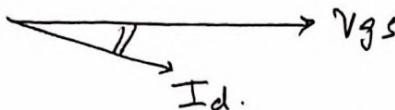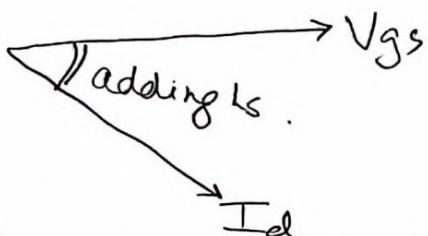 g_m is complex. (Both g_g & C_{gs} exist) at high freq. $g_g = \frac{w^2 C_{gs}^2}{5 g_{ds}}$.



Draw small signals & derive Z_{in}

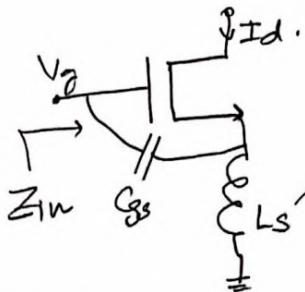


L_s gives feedback if added at source. like the feedback we saw with . This is probably why we don't use I_d .

$$Z_{in} = \frac{g_m L_s}{C_{gs}} + \frac{1}{s C_{gs}} + s L_s.$$

Resistive! $R_{in} = w_T L_s$ if $C_{gs} \gg C_d$

→ Putting it all together.

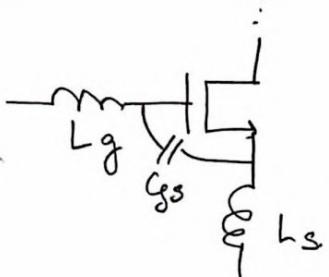

> $L_s + L_g$ resonate with C_{gs} .


> L_s & L_g are both needed since we need two degrees of freedom to get both noise match and power match.

→ C_d ? 1) lowers reverse isolation (large due to Miller).
2) changes phase relationship of input & output.

→ How to get rid of C_d ? Cascode! It also helps with stability and prevents oscillations.

Final LNA

44

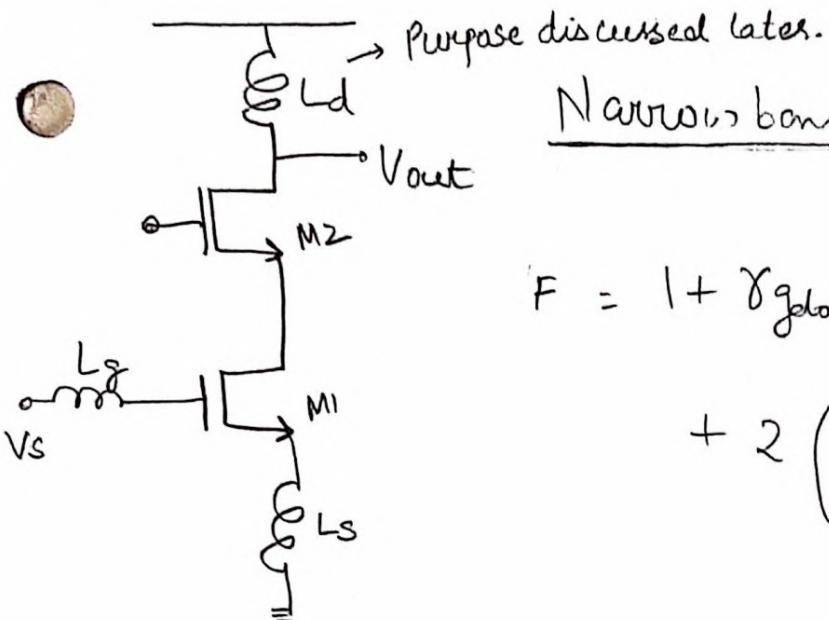

Narrowband LNA

$$F = 1 + \gamma g_{ds} R_s' \left(\frac{\omega C_{gs}}{g_m} \right)^2 + \left[1 + \frac{1}{(\omega C_{gs} R_s')^2} \right] g_{ds} R_s'$$

$$+ 2 \left(\frac{\omega C_{gs}}{g_m} \right)^2 g_m R_s' |c| \sqrt{\frac{\delta s}{5}}$$

where, $R_s' = \frac{g_m L_s}{C_{gs}}$


If $\overline{i_{in}^2} = 0$,

$$F = 1 + \gamma g_{ds} R_s' \left(\frac{\omega}{\omega_T} \right)^2$$


$$\omega_T = \frac{g_m}{C_{gs}}$$

We care about ω_T
Higher \Rightarrow Better
(assuming γ is same)

Derivation (ignoring G_d , & M_2)

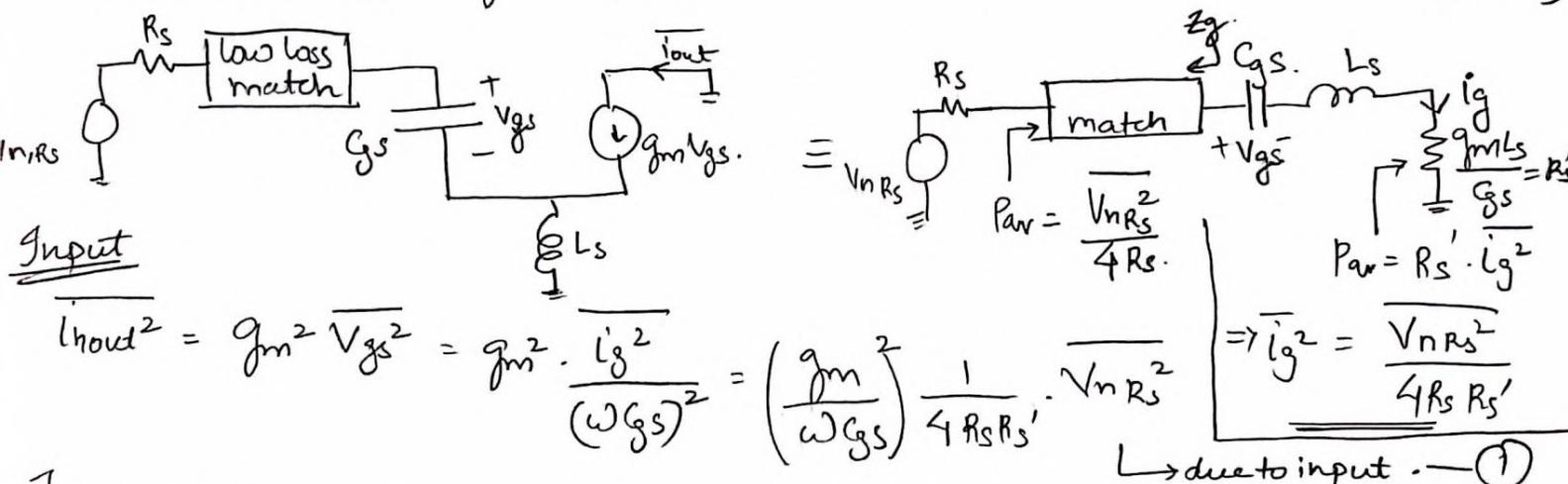

Transistor

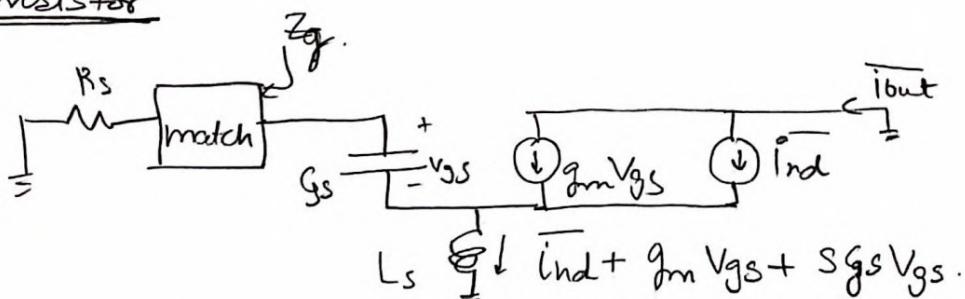

$$KVL \Rightarrow S L_s [(g_m + S C_{gs}) V_{gs} + i_{nd}] + V_{gs} + Z_d [S C_{gs} V_{gs}] = 0$$

$$\Rightarrow V_{gs} = - \frac{SL_s}{1 + sG_s Z_g + SL_s (g_m + sG_s)} \bar{i}_{ind}$$


$$\bar{i}_{out} = g_m V_{gs} + \bar{i}_{ind} = \frac{Z_g + \frac{1}{sG_s} + SL_s}{Z_g + \frac{1}{sG_s} + SL_s + \frac{g_m L_s}{C_s}} \cdot \bar{i}_{ind}$$

$$\text{But for matching we need, } Z_g + \underbrace{\frac{1}{sG_s} + SL_s}_{\text{These two would cancel}} = R_s'$$

cancel & $Z_g = R_s'$

$$\Rightarrow \bar{i}_{out} = \frac{R_s'}{R_s' + R_s} \bar{i}_{ind} = \frac{\bar{i}_{ind}}{2} \rightarrow \text{noise due to } \bar{i}_{ind}$$

Noise due to \bar{i}_{ng} ?

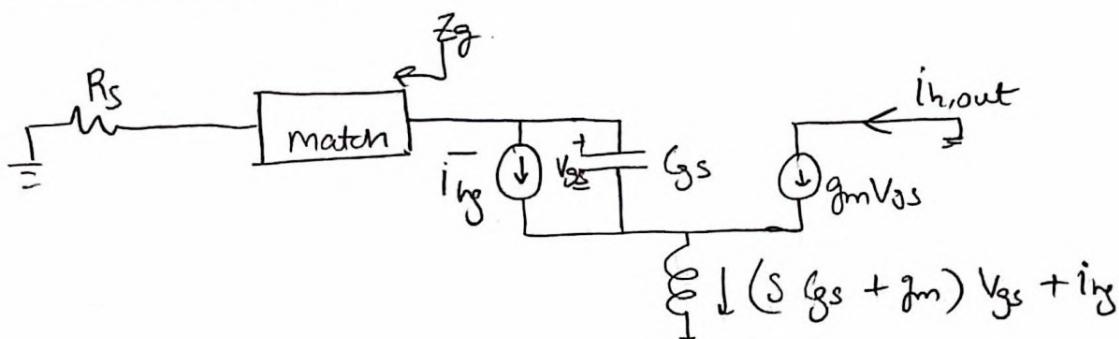

$$\text{KVL: } SL_s [(sG_s + g_m) V_{gs} + i_{ng}] + V_{gs} + Z_g (i_{ng} + sG_s V_{gs}) = 0.$$

$$\Rightarrow V_{gs} = - \frac{SL_s + Z_g \cdot \bar{i}_{ng}}{1 + sG_s Z_g + SL_s (sG_s + g_m)} \cdot \bar{i}_{ng}$$

$$i_{out} = g_m V_{gs} = \left[-\frac{g_m}{sG_s} \times \frac{1}{2} \times \left(1 - \frac{1}{sG_s R_s'} \right) \bar{i}_{ng} \right] \bar{i}_{ng} \quad \text{since } R_s' = Z_g + \frac{1}{sG_s} + SL_s$$

$$\Rightarrow \bar{i}_{out} = \bar{i}_{tot} = \bar{i}_{(V_n R_s)} + \bar{i}_{(i_{ind})} + \bar{i}_{(i_{ng})}$$

But what about correlation.

V_{n, R_s} & i_{ind} \rightarrow Uncorrelated.

V_{n, R_s} & i_{ng} \rightarrow Uncorrelated.
i.e. i_{ng} \rightarrow Correl. i_{ind}

$$\begin{aligned}
 \Rightarrow \frac{i_{\text{out}}}{i_{\text{tot}}} &= \frac{i_{\text{out}} \times i_{\text{out}}^*}{i_{\text{tot}} \times i_{\text{tot}}^*} \\
 &= \frac{i_{\text{out}}^2}{(V_{\text{ps}})} + \frac{i_{\text{out}}^2}{(i_{\text{nd}})} + \frac{i_{\text{out}}^2}{(i_{\text{ng}})} + \frac{i_{\text{out}} \times i_{\text{out}}^*}{(i_{\text{nd}})(i_{\text{ng}})} \\
 &\quad + \frac{i_{\text{out}} \cdot i_{\text{out}}^*}{(i_{\text{ng}})(i_{\text{nd}})} \quad A + A^* = 2 \operatorname{Re}(A) \\
 \frac{i_{\text{out}}}{i_{\text{nd}}} \cdot \frac{i_{\text{out}}^*}{i_{\text{ng}}} + \frac{i_{\text{out}}^*}{i_{\text{nd}}} \frac{i_{\text{out}}}{i_{\text{ng}}} &= 2 \operatorname{Re} \left\{ \frac{i_{\text{out}}^* \cdot i_{\text{out}}}{i_{\text{nd}} \cdot i_{\text{ng}}} \right\} \\
 &= 2 \operatorname{Re} \left\{ \frac{-g_m}{4sG_{\text{gs}}} \left(1 - \frac{1}{sG_{\text{gs}}R_s'} \right) \frac{i_{\text{out}}^* i_{\text{ng}}}{i_{\text{nd}}} \right\} \quad \therefore C = -j|C| \\
 &= 2 \operatorname{Re} \left\{ \frac{\pm g_m}{4\omega G_{\text{gs}}} + \frac{j g_m}{4\omega^2 G_{\text{gs}}^2 R_s'} \right\} |C| \sqrt{i_{\text{nd}}^2 \cdot i_{\text{ng}}^2} \\
 &= \frac{2 g_m}{4\omega G_{\text{gs}}} \cdot |C| \sqrt{\gamma_{\text{gdo}} \gamma_{\text{gg}} \cdot 4K_T \Delta f} \quad j\gamma_{\text{gdo}} \gamma_{\text{gg}} = \frac{\omega^2 G_{\text{gs}}^2}{5} \\
 &= \frac{g_m}{2} |C| \sqrt{\frac{8\delta}{5}} \cdot 4K_T \Delta f.
 \end{aligned}$$

$$\boxed{NF = 1 + \gamma_{\text{gdo}} R_s' \left(\frac{\omega G_{\text{gs}}}{g_m} \right)^2 + \left[1 + \frac{1}{(\omega G_{\text{gs}} R_s')^2} \right] \gamma_{\text{gdo}} \gamma_{\text{gg}} R_s' + 2 \left(\frac{\omega G_{\text{gs}}}{g_m} \right)^2 g_m R_s' |C| \sqrt{\frac{\delta \gamma}{5}}}$$

$$\begin{aligned}
 \omega_T &= \frac{g_m}{G_{\text{gs}}} \\
 R_s' &= \frac{g_m}{g_m L_S}
 \end{aligned}$$

$$\boxed{\overline{i_{\text{ng}}^2} = 0} \Rightarrow \boxed{NF = 1 + \gamma_{\text{gdo}} R_s' \left(\frac{\omega}{\omega_T} \right)^2}$$

LNA Design example

$$f_0 = 1.8 \text{ GHz}$$

$$R_s = R_s' = 50 \Omega$$

$$\gamma = 2$$

$$BW = 180 \text{ MHz}$$

In velocity saturation.

$$g_m = \frac{MnC_{ox}}{2} \cdot E_c W$$

$$\Rightarrow g_m \propto W$$

$$C_{gs} = \frac{2}{3} WL C_{ox} = \frac{2}{3} C_{ox} \left(\frac{L}{t_{ox}} \right) W \quad \text{constant with process.}$$

$$\Rightarrow C_{gs} \propto W$$

Process = $0.25 \mu\text{m CMOS}$


$$C_{gs} = (1.5 - 2.5 f_F) W$$

$$g_m = (0.3 - 0.4 \frac{mA}{V}) W$$

$$\omega_T = \frac{g_m}{C_{gs}} \approx 25 \text{ GHz}$$

$$R_s' = \omega_T L_s \Rightarrow L_s = \frac{R_s'}{\omega_T} = \frac{50 \Omega}{25 \text{ GHz} \times 2\pi} = 0.3 \text{ nH}$$

$$\Rightarrow L_s = 0.3 \text{ nH}$$

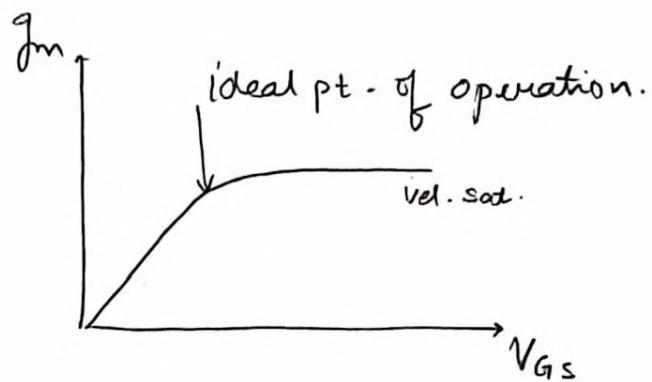


Device size?

$$\begin{array}{l} \xrightarrow{\quad} C_{gs} \rightarrow L_g \\ \xrightarrow{\quad} Q \rightarrow BW \end{array}$$

Bias?

$$\xrightarrow{\quad} g_m \& g_{do}.$$

Input circuit

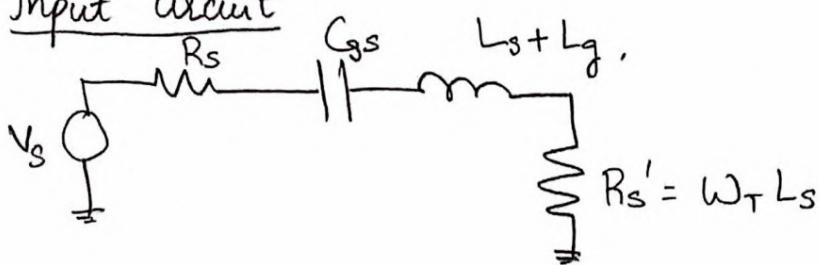

$$Q = \frac{1}{(R_s + R_s') C_{gs} \omega_0}, \quad BW = \frac{\omega_0}{Q}.$$

Tradeoffs on W

$$W \downarrow \Rightarrow C_{gs} \downarrow \Rightarrow$$

$$\left\{ \begin{array}{l} Q \uparrow \Rightarrow BW \downarrow \\ L_g \uparrow \Rightarrow \text{Size} \uparrow \Rightarrow \text{Tr}_g \Rightarrow \uparrow \text{Loss} \Rightarrow \uparrow \text{NF} \\ \Rightarrow \text{Loss at } 1/\rho \text{ is bad!} \end{array} \right.$$

$$W \downarrow \Rightarrow g_m \downarrow \Rightarrow g_{do} \downarrow \Rightarrow NF \downarrow$$

$\Rightarrow f_f \ g_m \uparrow = NF \uparrow$ but input suffered noise $\bar{V_n^2} \downarrow$ since gain \uparrow
 \Rightarrow Tradeoff $\bar{V_n^2} \propto NF$.

$\downarrow NF \rightarrow$ in narrowband \Rightarrow lower g_m .

$\downarrow \bar{V_n^2} \rightarrow$ in broadband \Rightarrow increase g_m .

$$W \downarrow \Rightarrow I_d \downarrow \Rightarrow P_{dc} \downarrow$$

$$BW = 180 \text{ MHz} \Rightarrow Q_{yp} = 10$$

$$= \frac{1}{2 R_s C_{gs} \omega_0}$$

$$\Rightarrow C_{gs} = 88 \text{ fF}$$

$$\text{But } C_{gs} = 2f_F \times \omega$$

$$\Rightarrow \boxed{\omega = 44 \mu\text{rad}} \quad \text{Huge! But let's see!}$$

$\Rightarrow L_s + L_g$ should resonate with C_{gs} .

$$\Rightarrow (L_s + L_g) C_{gs} \omega_0^2 = 1$$


$$\Rightarrow \boxed{L_g = 88 \text{ nH}} \rightarrow \text{not possible to integrate.}$$

Assume Q of L_g is 15 (Wishful thinking)

$$\Rightarrow \gamma_g = \frac{\omega L_g}{Q} = 66 \Omega \Rightarrow \frac{88 \text{ nH}}{Q = 15} \Rightarrow 88 \text{ nH} \parallel 66 \Omega$$

$$NF_{\text{tot}} = 1 + \frac{R_f}{R_s} \gamma_{gd} R_s' \left(\frac{\omega}{\omega_T} \right)^2$$

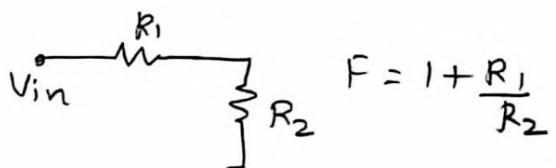$\rightarrow \gamma_p$ is very sensitive to R_g .



$\Rightarrow 66 \Omega$ at γ_p is too high since we don't want to add another matching network to down convert it. Cannot down convert it with $R_s' = \omega_T L_s$ & current matching network.

Reminder: $\omega \downarrow \Rightarrow C_{gs} \downarrow \Rightarrow L_g \uparrow \Rightarrow \gamma_g \uparrow \Rightarrow NF \uparrow$

Solution: Lower $V_p \Rightarrow C_{GS} \uparrow \Rightarrow L_g \downarrow \Rightarrow r_g \downarrow$.
 ↴ But $W \uparrow$.

$$\frac{V_s}{V_p} = 1 \Rightarrow C_{GS} = 880 \text{ fF} \Rightarrow W = 440 \quad [\text{LNA drivers are huge}]$$

$$\Rightarrow L_g \approx 8.5 \text{ nH.}$$

If θ of L_g is 15 $\Rightarrow r_g = 6.4 \Omega$ (much better).

Current? Remember we bias b/w square law & velocity saturation

$$\Rightarrow g_m = \frac{\mu_n C_{ox}}{2} E_c W$$

$$\Rightarrow V_{GS} - V_{TH} = \frac{E_c L}{2} \Rightarrow I_D = \frac{\mu_n C_{ox}}{2} \cdot \frac{W}{L} \cdot \frac{(V_{GS} - V_{TH})^2}{1 + \frac{1}{E_c L} (V_{GS} - V_{TH})}$$

$$\Rightarrow I_D = \left(\frac{1}{12} \mu_n \left(\frac{C_{ox}}{L} \right) L \cdot E_c^2 \right) W$$

$$= (0.1 \text{ mA}) W \quad \text{from simulation.}$$

comes from
 $M = \frac{M_0}{1 + \frac{E}{E_c}}$

where $E = \frac{V_{GS} - V_{TH}}{L}$

$$\text{For } W = 440 \Rightarrow I_D = 44 \text{ mA}$$

$$\Rightarrow g_m = \omega_T C_{GS} = 140 \text{ mA/V} \Rightarrow g_{d0} = g_m,$$


$$F = 1 + \gamma g_{d0} R_s' \left(\frac{\omega}{\omega_T} \right)^2 = 1.07$$

$$\Rightarrow \boxed{NF = 0.3 \text{ dB}}$$

$$\text{With } r_g = 6.4 \Omega \Rightarrow F = 1.2$$

$$\Rightarrow \boxed{NF = 0.8 \text{ dB}}$$

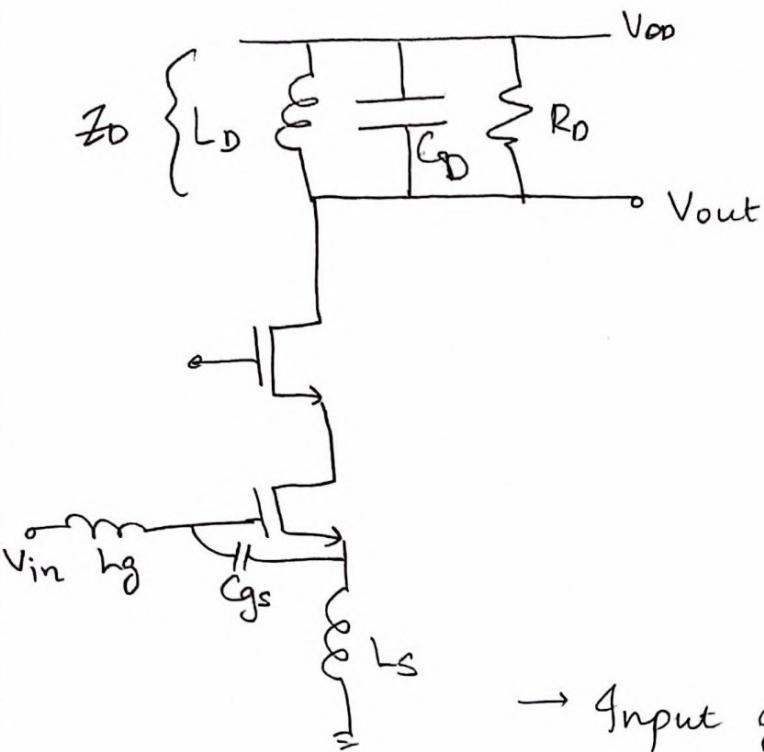→ Q_{op} is low so it is relatively wideband, ⇒ at the output we use a narrowband (signal is anyway narrowband) & use high Q_{op} .



Gain?

$$At \text{ resonance.}$$

$$V_{gs} = \frac{V_{in}}{2R_s} \left(\frac{1}{j\omega_0 C_s} \right) = \frac{Q_{in} V_{in}}{j}$$


$$i_D = g_m \left(\frac{Q_{in}}{j} \right) V_{in}$$

$$\text{Gain} = \frac{V_{out}}{V_{in}} = -g_m Z_0 \left(\frac{Q_{in}}{j} \right)$$

Controls both
Gain & BW.

- Input gives noise & power match.
- Z_0 gives Gain & BW.

Biassing.

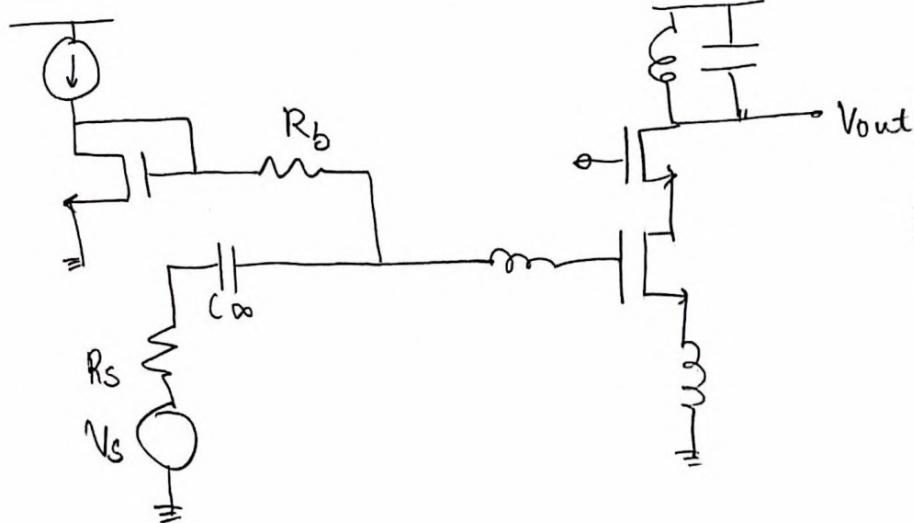


$$R_b \gg R_s \parallel R_s' = \frac{R_s}{2}$$

1) Effect of pads & wirebonds.

↳ parasitic cap

↳ parasitic inductance (poor tolerance)

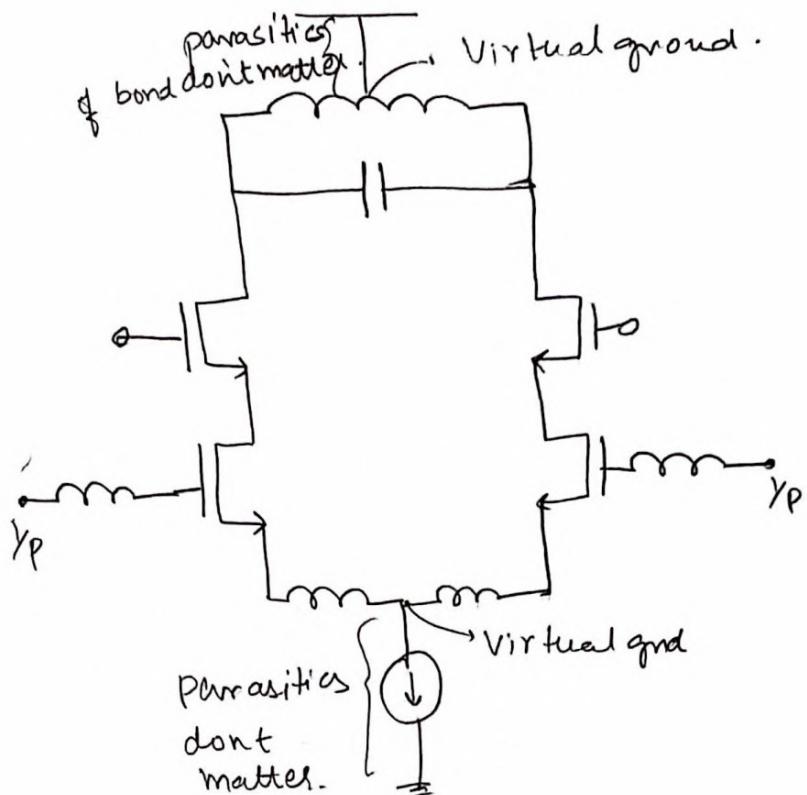- Could absorb into design at L_o & C_o .
- Or use differential LNA.



- A balun is implemented at Y_P to get rid of parasitics due to bondwire & pad that carry Y_P signal to chip!

CG LNA


$$NF = 1 + \frac{\gamma}{2}$$

Could improve to $NF = 1 + \gamma \cdot \frac{g_{do}}{g_{do} + g_m}$ (HW question)

Not so popular.

Broadband LNA

(I)

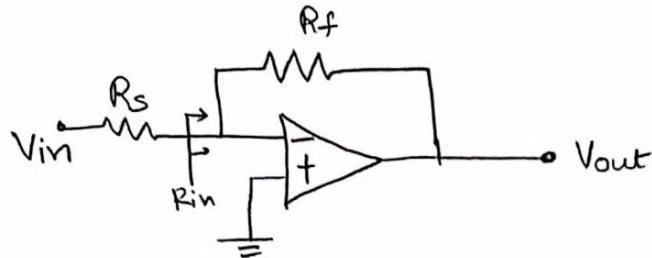

$$\overline{V_{nout}^2} = \left(-\frac{R_f}{R_s} \right)^2 \overline{V_n^2}_{R_s} + \overline{V_n R_f^2}$$




$$F = 1 + \left(\frac{R_s}{R_f} \right)^2 \cdot \frac{4kT R_f \Delta f}{4kT R_s \Delta f} = 1 + \frac{R_s}{R_f}$$

$$R_{in} = \frac{R_f}{1+A} \Rightarrow \text{matched} \Rightarrow \frac{R_f}{1+A} = R_s \Rightarrow R_f = (1+A)R_s$$


\Rightarrow

$$F = 1 + \frac{1}{1+A}$$

(II)

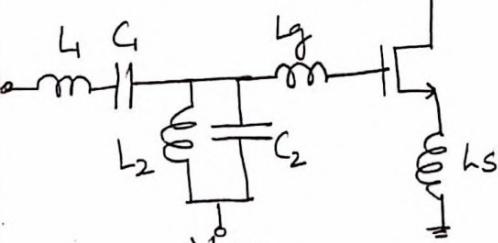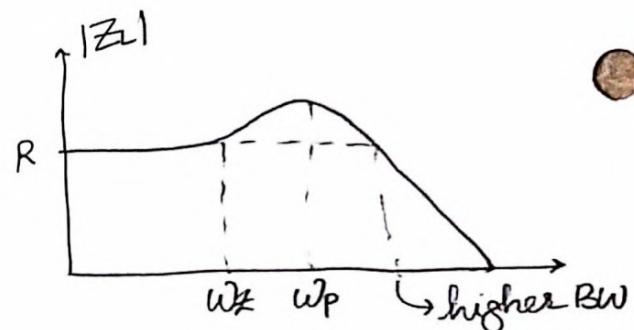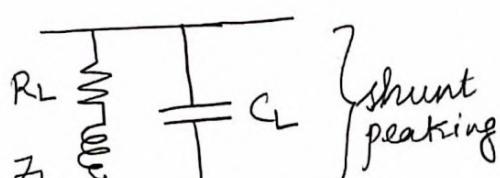

6th order matching network.

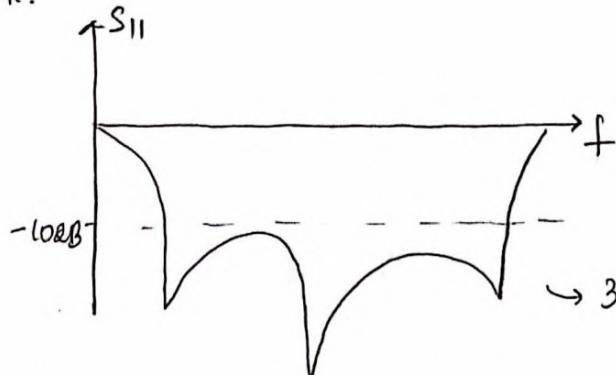

$$\omega_z = \frac{R_L}{L_L}$$

$$|Z_L(j\omega)| = R \sqrt{\frac{(\omega\tau)^2 + 1}{1 - \left(\frac{\omega\tau}{\omega_1}\right)^2 + \left(\frac{\omega}{\omega_1}\right)^2}}$$

$$\tau = \frac{L}{R} = \frac{1}{\omega_z}$$

$$\omega_1 = \frac{1}{RC} = -\omega_{-3dB} \text{ without } L.$$

$$m = \frac{RC}{\tau R} = \frac{1/\omega_1}{\tau} = \frac{1}{\tau\omega_1}$$

Shunt Peaking.

Maximum BW

$$M = \sqrt{2} \quad \text{or} \quad T = \frac{1}{\sqrt{2}\omega_1}$$

$$\Rightarrow BW = 1.85\omega_1, \quad \text{but } 20\% \text{ peaking}$$

⇒ Broadcast signal is distorted.

No peaking.


$$T = \frac{1}{(1+\sqrt{2})\omega_1} \Rightarrow BW = 1.72\omega_1$$

But phase response is not flat

Flat group delay


$$T = \frac{1}{3.1\omega_1} \Rightarrow BW = 1.6\omega_1$$

Common Gate LNA

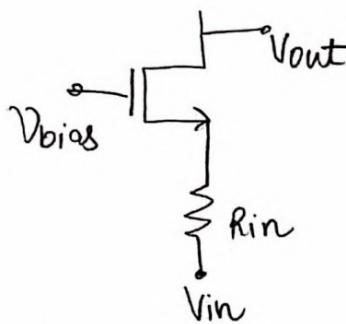


$$NF = 1 + \frac{\gamma}{\alpha}$$

Increase V_{GS} ⇒

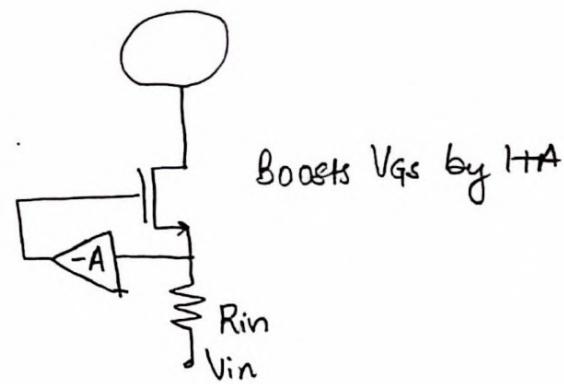
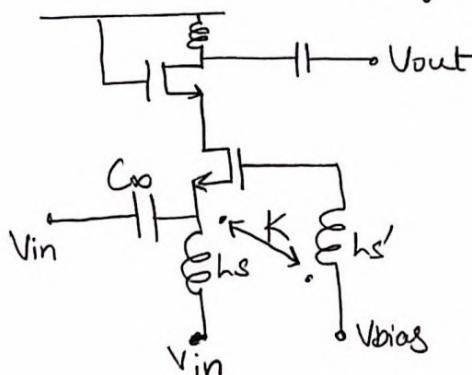
$$NF = 1 + \frac{\gamma}{\alpha} \cdot \frac{1}{1+A} \rightarrow \text{needs to be low noise and needs a voltage amplifier} \Rightarrow \text{Transformer.}$$




$$NF = 1 + \gamma \left(\frac{1}{1+nk} \right)$$


(Paper: Xiaoyong Li, ISSCC 2005)

> Reducing the effect of C_{gd}
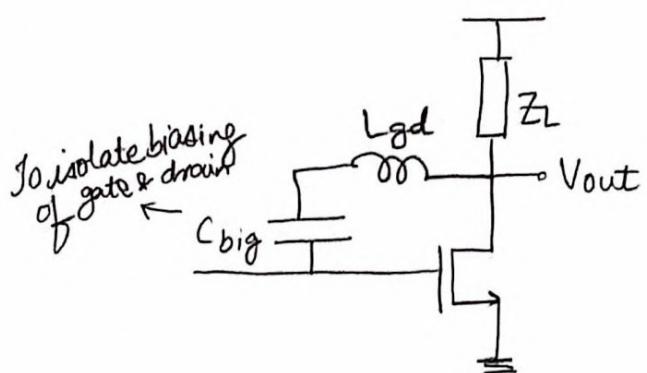
> Use L_{gd} to resonate with $C_{gd} \rightarrow$ However this is narrowband





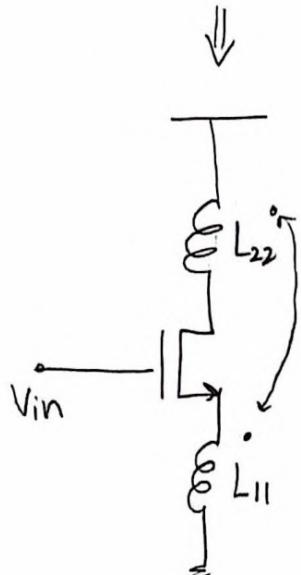But C_{gd} is small so L_{gd} needs to be large! \Rightarrow Bad.
Solution: Use a transformer.



$$\frac{n}{K} = \frac{C_{gs}}{C_{gd}} \Rightarrow \text{tunes out } C_{gd}!$$


MIXERS

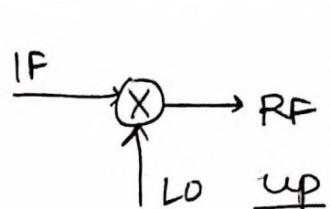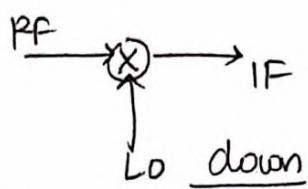


General Considerations.

- > NF (not as important as LNA)
- > Linearity (quite important)
- > Conversion gain (relaxes noise requirement down the chain)
- * > Isolation (B/W LO, RF & IF)
- > BW
- > Power.

Basic definitions

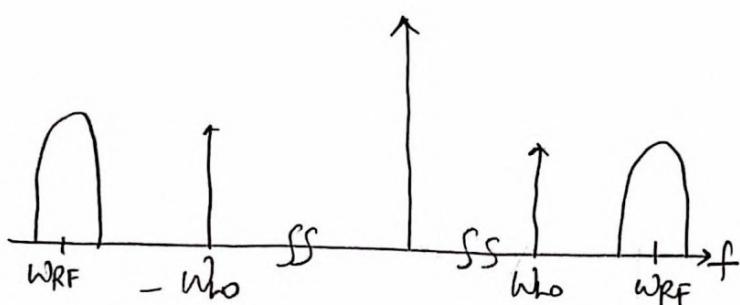

Down

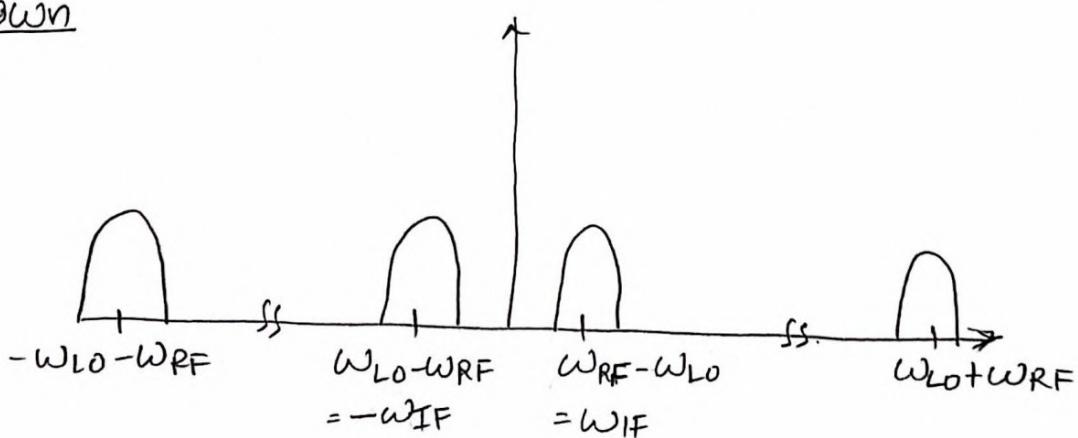

$w_{IF} = 0 \Rightarrow$ Homodyne, zero IF

$w_{IF} \neq 0 \Rightarrow$ Heterodyne, low IF

Up


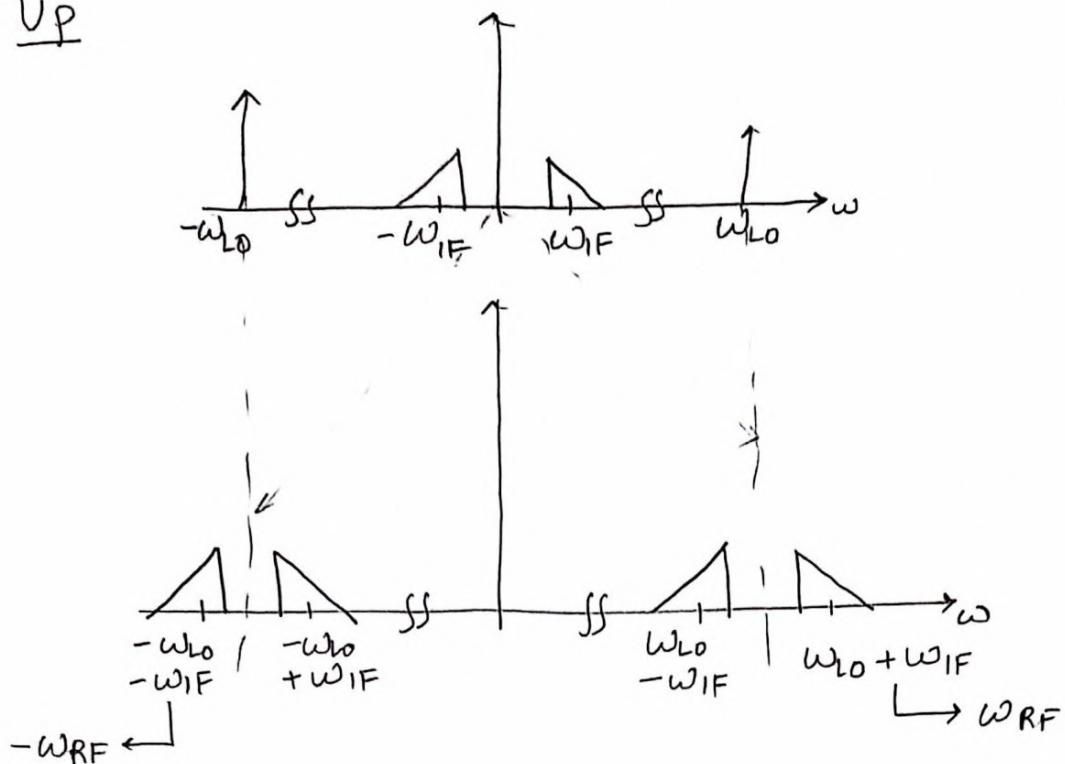



Image Aliasing

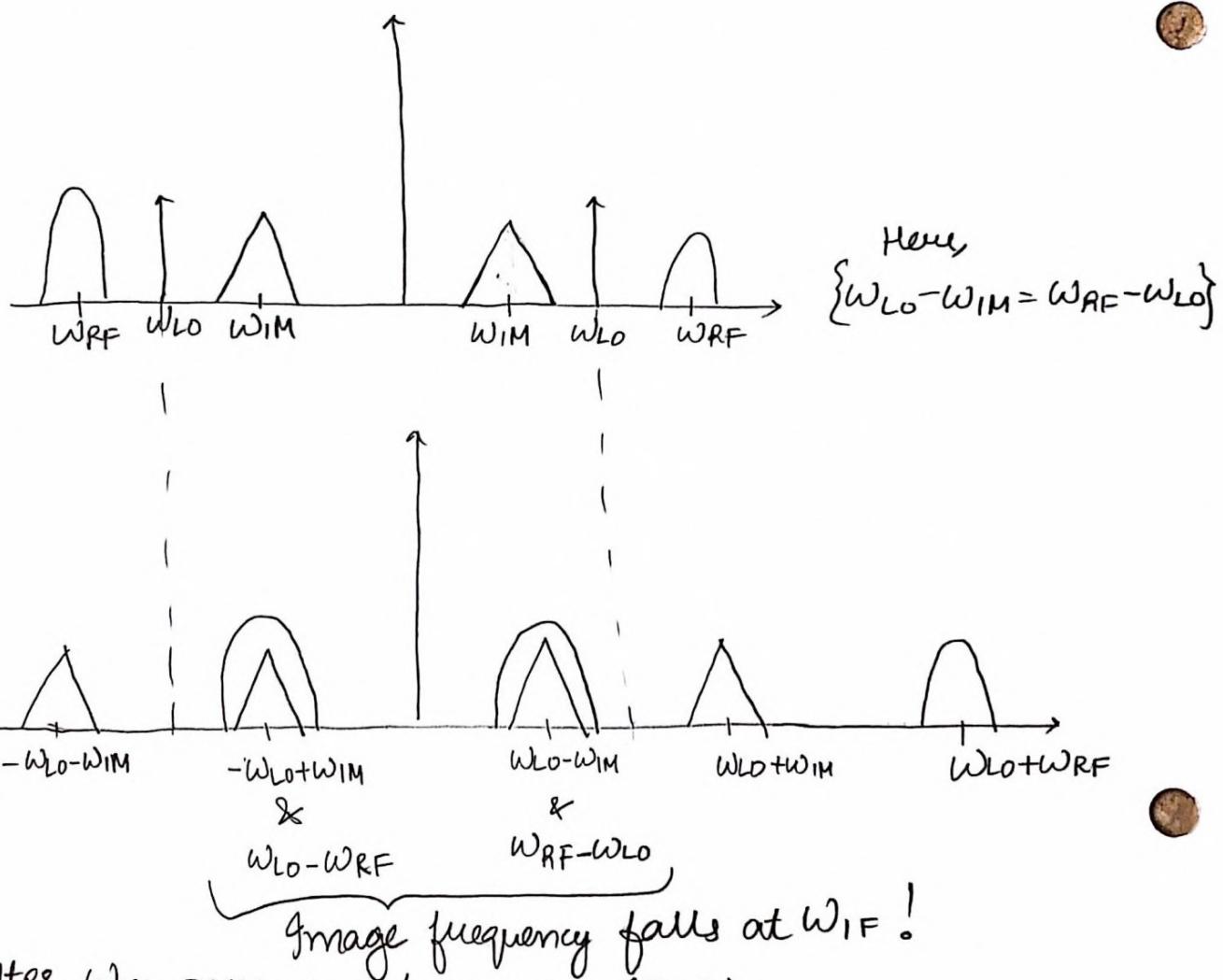

= Need to filter w_{IM} or use complex numbers (\Re, \Im)



LO Feedthrough

1) LO to IF feedthrough (Down)

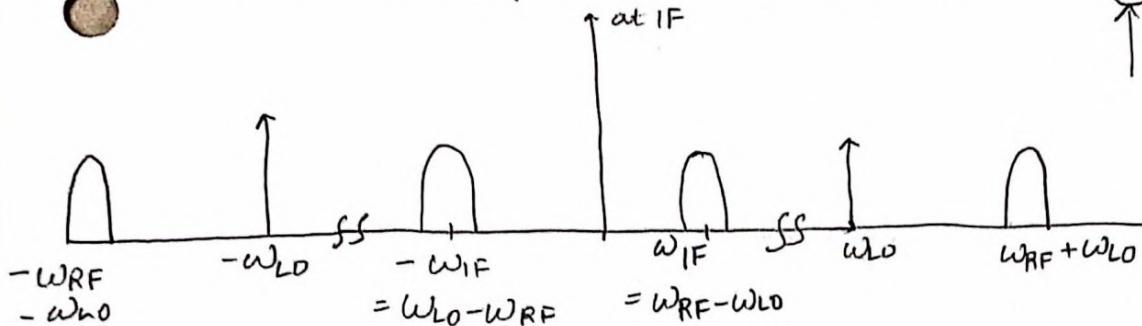

If w_{IF} is chosen low we can easily filter.

2) LO to RF feedthrough (Up)

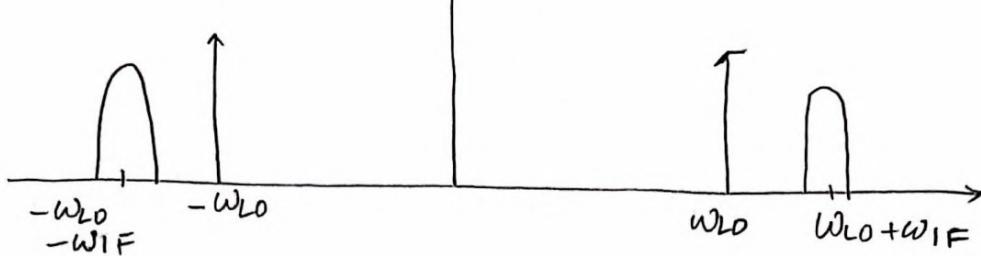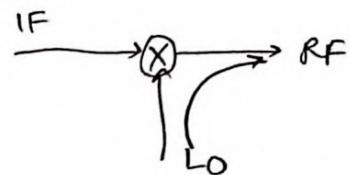

- > Regardless of w_{IF} it is problematic since we are radiating out of band signals.
- > More problematic in zero IF, w_{LO} is transmitted in band!
- > Could cause blocking for following stages (PA).


3) LO to RF reverse feedthrough (DOWN)



- > Could end up on antenna! Bad.
- > Self mixing \Rightarrow generates a dc signal \Rightarrow Bigger problem in zero IF \Rightarrow dc is in band
 - ↳ Could mess up biasing of next stage or saturate it.


- LO to IF reverse feedthrough in UP. could affect previous stages.
- RF to LO feedthrough should be low to prevent 'pulling'.

Mixer Noise Figure.

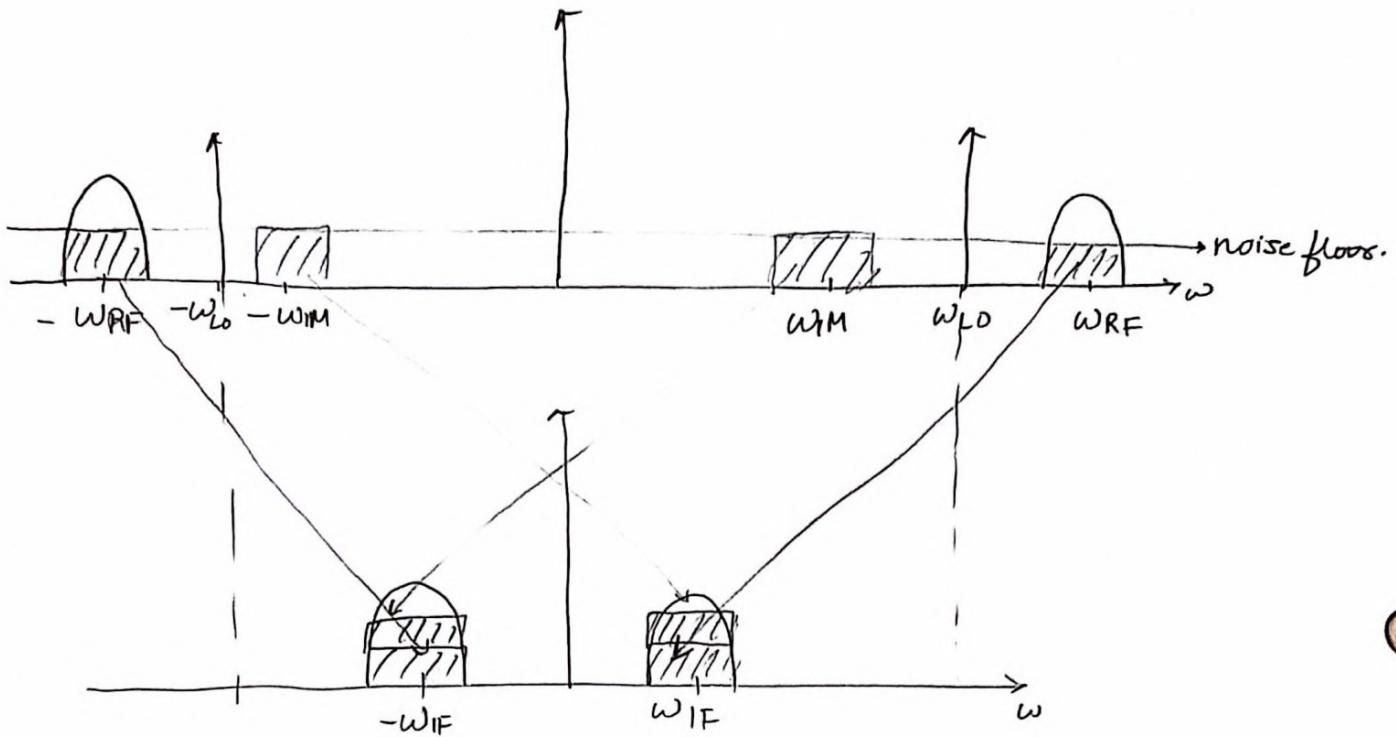

- Even an ideal mixer doubles the noise (at input).
 - Here since signal is only SSB, the NF is called SSB.
 - Double side band noise figure DSB is the NF when we assume the same signal also exists at ω_{IM} . (Leg in gen 1F).
- Therefore
$$\boxed{NF_{SSB} = NF_{DSB} + 3\text{dB}}$$

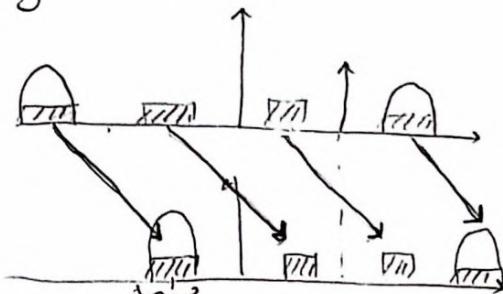
- Fix:
- 1) Filter noise at ω_{IM} . (Impractical)
 - 2) Use complex mixing. (Only ω_{LO} exists & no $-\omega_{LO}$ exists).



Balance of Mixer


→ Balanced $\Rightarrow 0 \text{ dc}$.

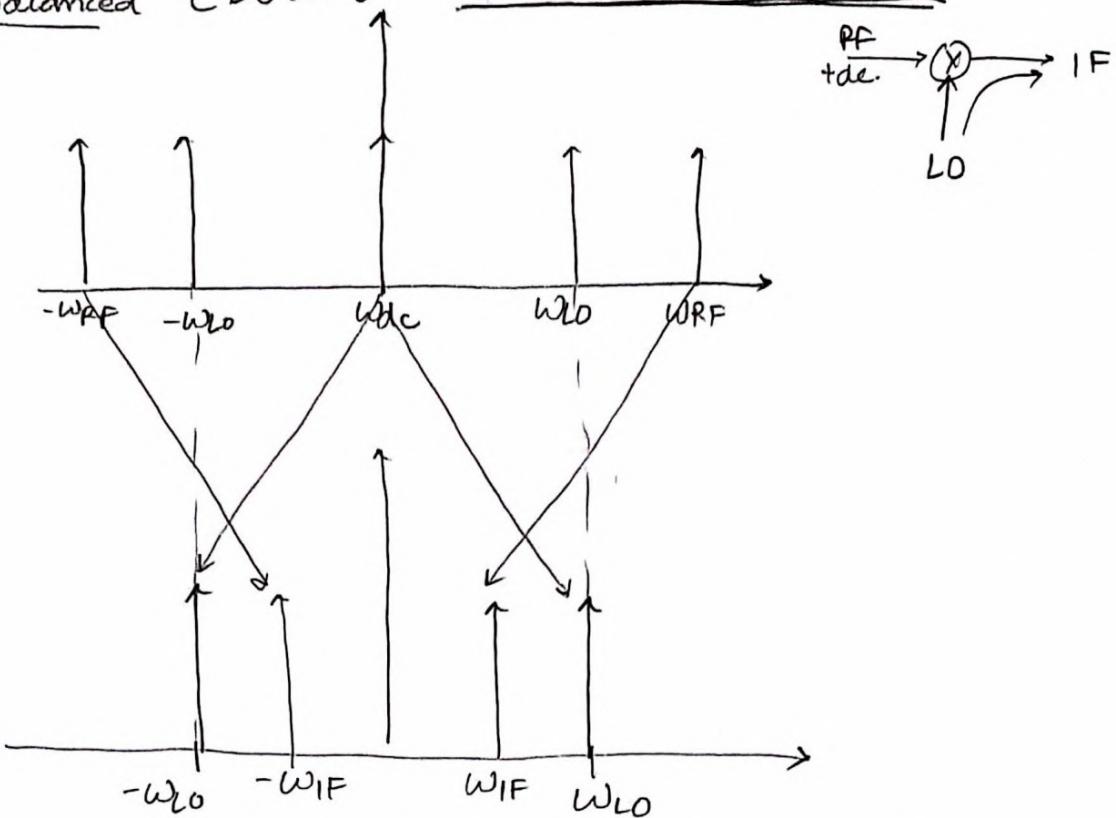① Eg: Unbalanced (Down) → Unbalanced at RF



→ Like LO feedthrough! \Rightarrow Problematic in upconversion mixers.

② Eg: Unbalanced at LO (DOWN)

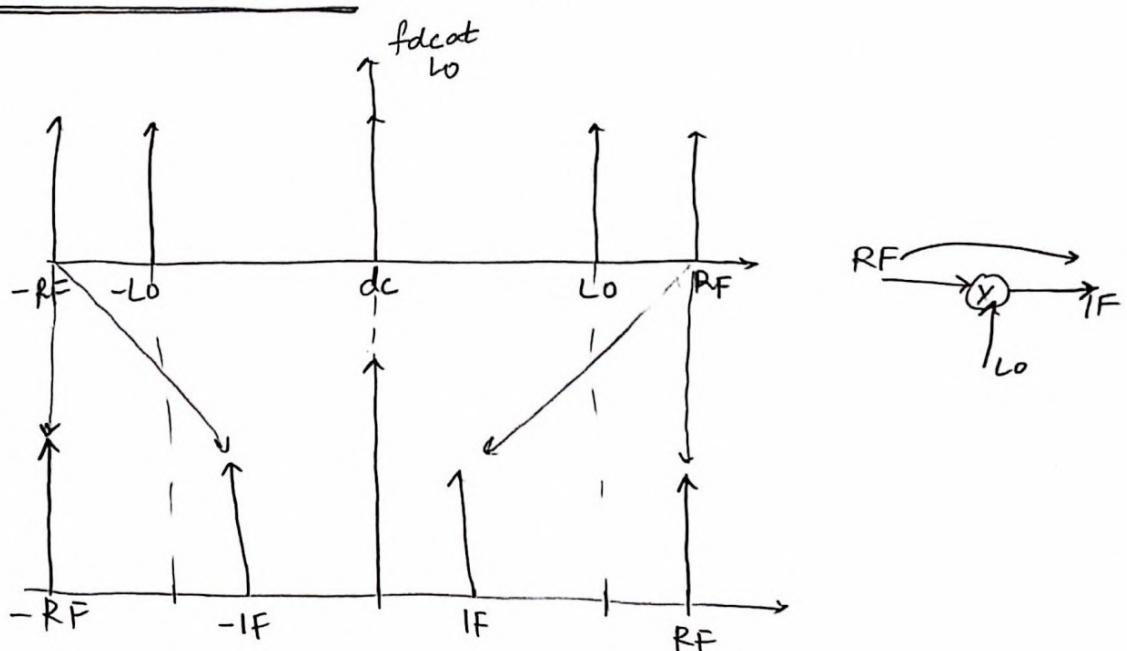


→ Like RF feedthrough

→ Double balanced \Rightarrow Balanced at RF and LO.

Implementation
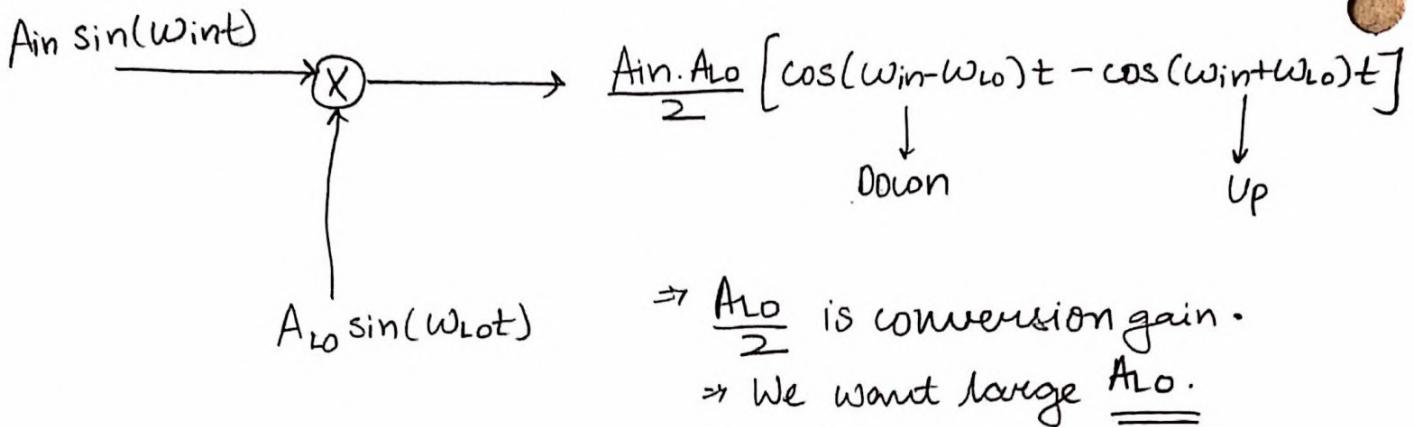
> Need nonlinear or time variant circuits.




$$\text{Conversion gain (power)} = \frac{\text{Power delivered to } R_L \text{ at IF}}{\text{Power available to } R_s \text{ at RF}}$$

(down)

$$\text{Conversion gain (power)} = \frac{\text{Power delivered to } R_L \text{ at RF}}{\text{Power available to } R_s \text{ at IF}}$$

(up)

Nonlinearity

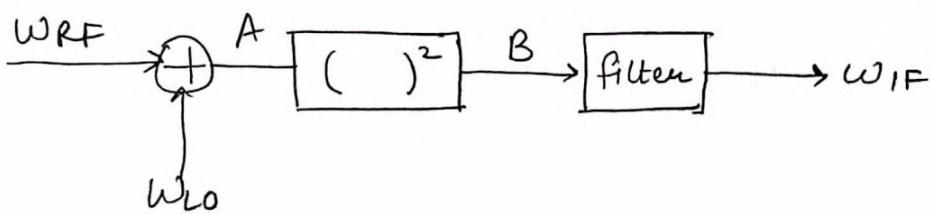

$$A: A_{RF} \sin(w_{RF} t) + A_{LO} \sin(w_{LO} t)$$

$$B: \underbrace{A_{RF}^2 \sin^2(w_{RF} t)}_{0, 2w_{RF}} + \underbrace{2A_{RF} A_{LO} \sin w_{RF} \sin w_{LO} t}_{w_{RF} \pm w_{LO}} + \underbrace{A_{LO}^2 \sin^2(w_{LO} t)}_{0, 2w_{LO}}$$

filter

Recall:




α_2 gives the $(\)^2$ function

Problems

- α_2 is small \Rightarrow low gain.
- α_3 can affect (we don't want)
- Cannot use differential.

Implementation (1)

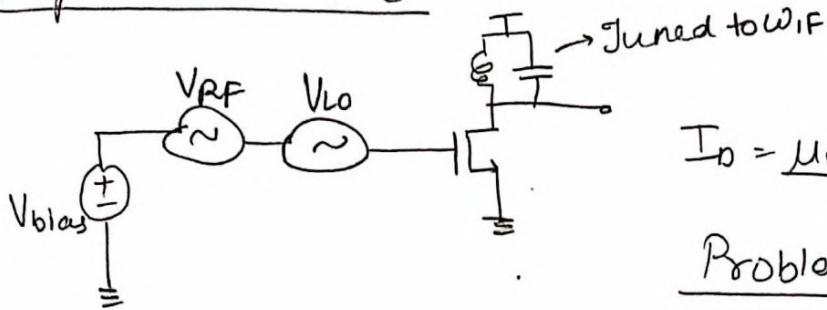


$$I_D = \frac{MnCox}{2} \frac{W}{L} [(V_{bias} + V_{RF} + V_{LO}) - V_{th}]^2$$

Problems

- Simple.
- Low gain
- xx No RF, LO isolation.

Implementation (2)

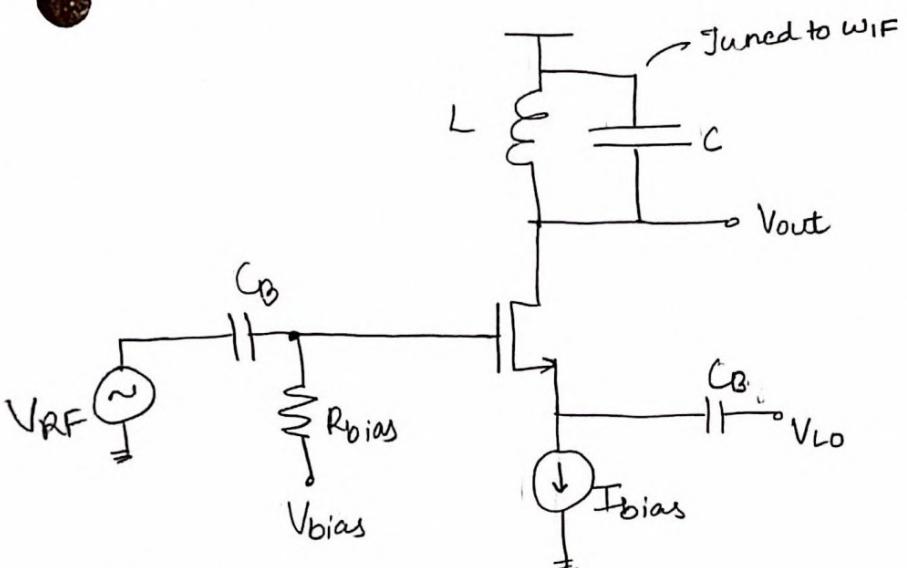

$$i_D = \frac{MnCox}{2} \frac{W}{L} (V_{gs} - V_{th})^2$$

$$i_D = \frac{MnCoxW}{2L} \{ (V_{RF} - V_{LO}) - V_{th} \}^2$$

$$= \frac{MnCoxW}{2L} \left\{ V_{RF}^2 + V_{LO}^2 + V_{th}^2 - 2 \cdot V_{th} (V_{RF} - V_{LO}) - 2 V_{RF} V_{LO} \right\}$$

Problems

- High gain
- Poor isolation


$$\Rightarrow \boxed{\text{Conversion gain} = \frac{MnCox}{2} \cdot \frac{W}{L} \cdot V_{LO}}$$

↳ does not depend on V_{bias} as long as device is in saturation.


V_{bias} must ensure $V_{RF} - V_{LO} > V_{th}$.

Switching Mixer

LTV

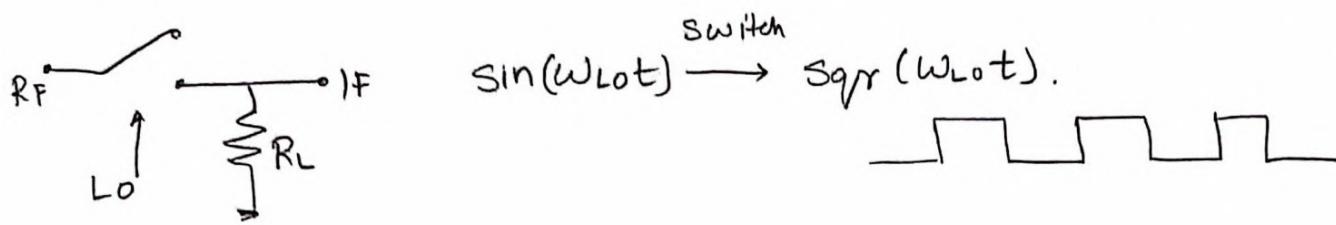

Derivation

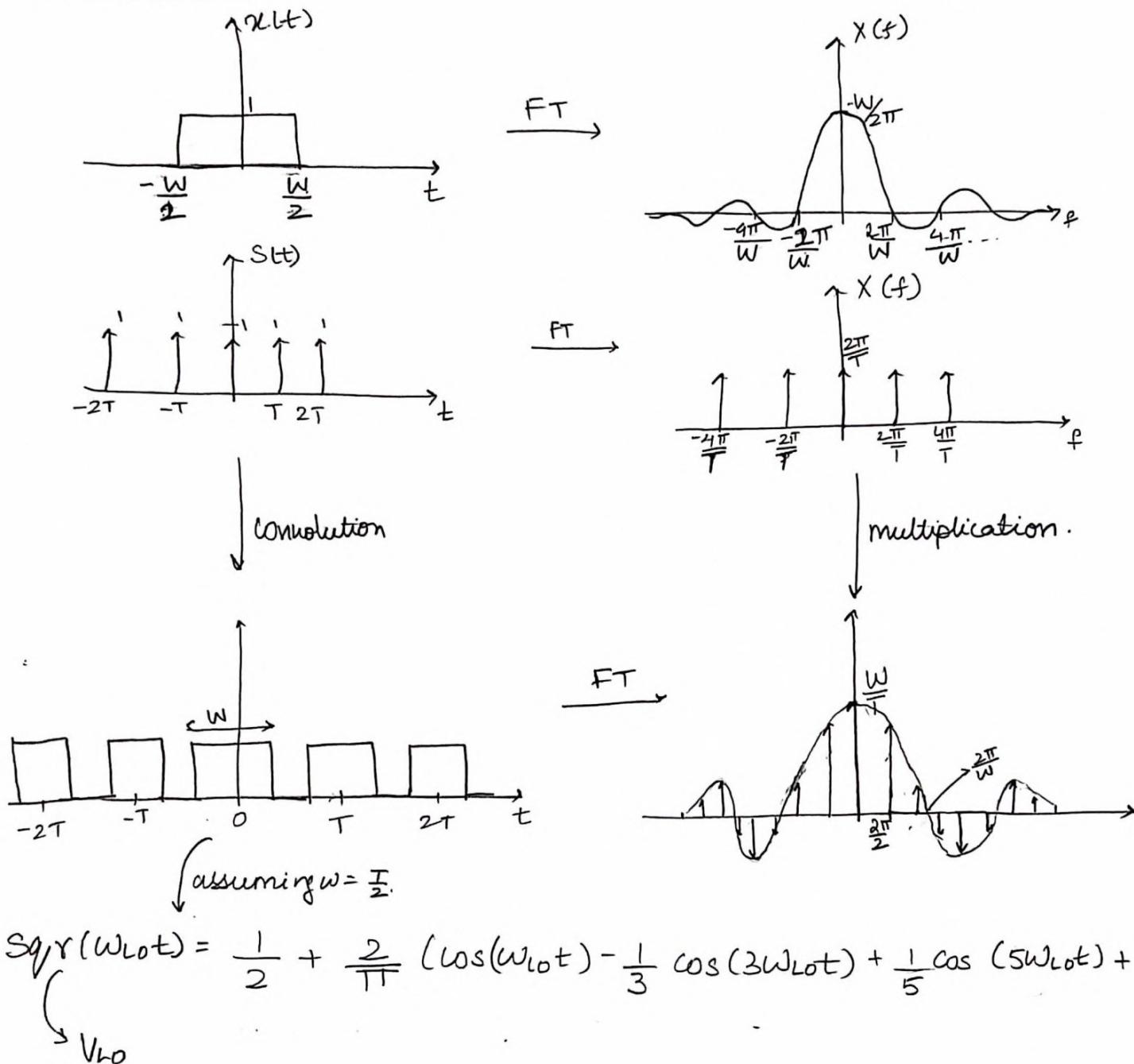

$$V_{IF}(t) = V_{RF}(t) \cdot V_{LO}(t)$$



$A_{RF} \cos(\omega_{RF} t)$

$$V_{IF}(t) = \frac{V_{RF}}{2} \cos(\omega_{RF} t) + \underbrace{\frac{2}{\pi} V_{RF} \cos(\omega_{LO} t) \cos(\omega_{RF} t)}_{\text{What we want.}}$$


$$\text{Voltage gain} = \frac{2}{\pi} \cdot \frac{1}{2} = \frac{1}{\pi} \rightarrow \text{how!}$$

Problems

- > h_{LO} is unbalanced (due to $\frac{1}{2}$)
- > gain is low (it is passive)



Implementation ② → (more widely used)

- > Use a switch & capacitor.

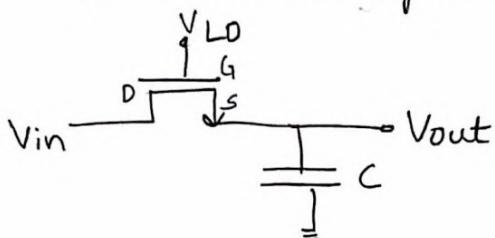

$$\left. \begin{array}{l} V_{LO} = 0 \Rightarrow \text{OFF} \\ V_{LO} = V_{dd} \Rightarrow \text{ON} \end{array} \right\} \text{For small } V_{in}. \quad R_{ON} = \frac{1}{\frac{L}{2} \cos \frac{W}{L} (V_{dd} - V_{out} - V_{th})}$$

When ON

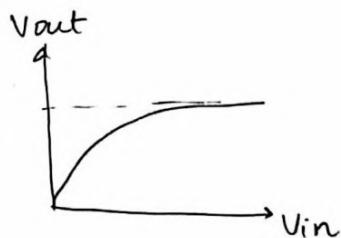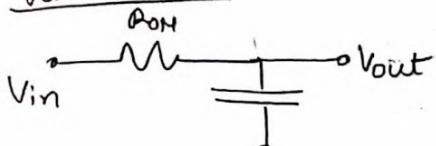

As $V_{out} \uparrow$, $R \uparrow$
⇒ slower

General rule
 $I \downarrow \Rightarrow R \uparrow$

Problems

- ∴ > slow

- ∴ > low pass → cutoff f > RF to work.

- > To make switch fast

$\left\{ \begin{array}{l} \text{Small } C \rightarrow \text{dominates (limited by parasitics)} \\ \text{Small } R_{ON} \Rightarrow \text{large } \frac{W}{L} \rightarrow \text{higher feedthrough} \end{array} \right.$


- > Tradeoff b/w ON & OFF states.

- ∴ > Can add gain during high ...




Fixing problem of variable R.


> Use a transmission gate.

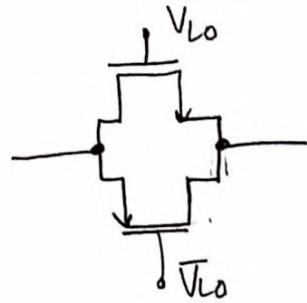

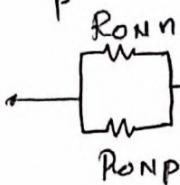$R_{ON} \parallel R_{OFF}$ \Rightarrow dependence on V_{DD} is cancelled
 when switch $V_{LO} = \text{high}$, V_{DD} .
 V_{DD} term is cancelled.




How to make a BJT switch faster.

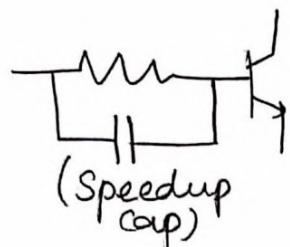

\Rightarrow To go from OFF to ON charges stored in cap are used to make the transition.


How to make it balanced?

=> Use LO signal with 0 dc.

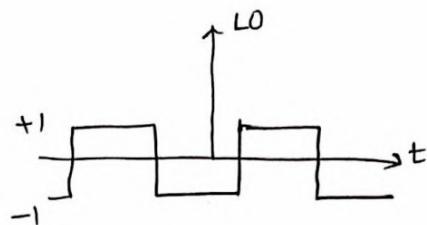

$$\Rightarrow V_{LO} = 0 + \frac{4}{\pi} \left(\cos \omega_{LO} t - \frac{1}{3} \cos (3 \omega_{LO} t) + \dots \right).$$

Double balanced.

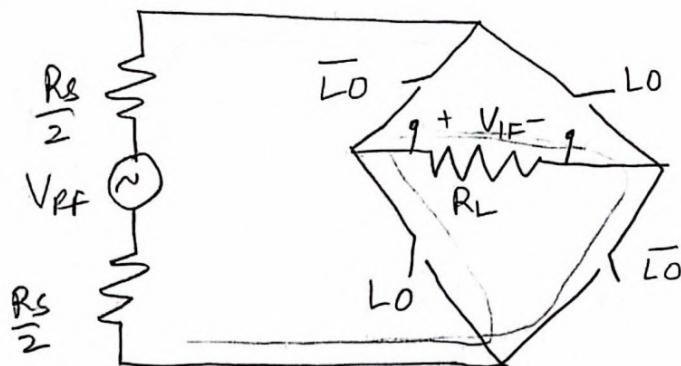


Problems

$\therefore 2$ switches \Rightarrow (R_{ON} & Parasitics)


Active Miracles

四

- Use a diff pair as a switch

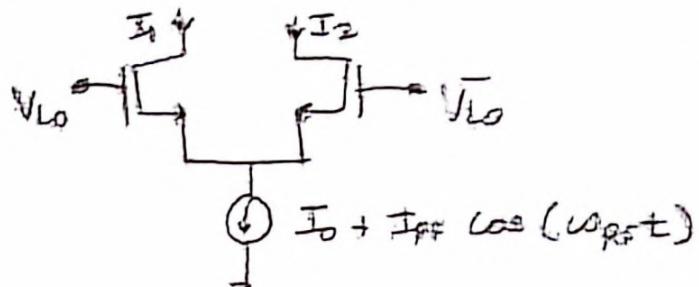


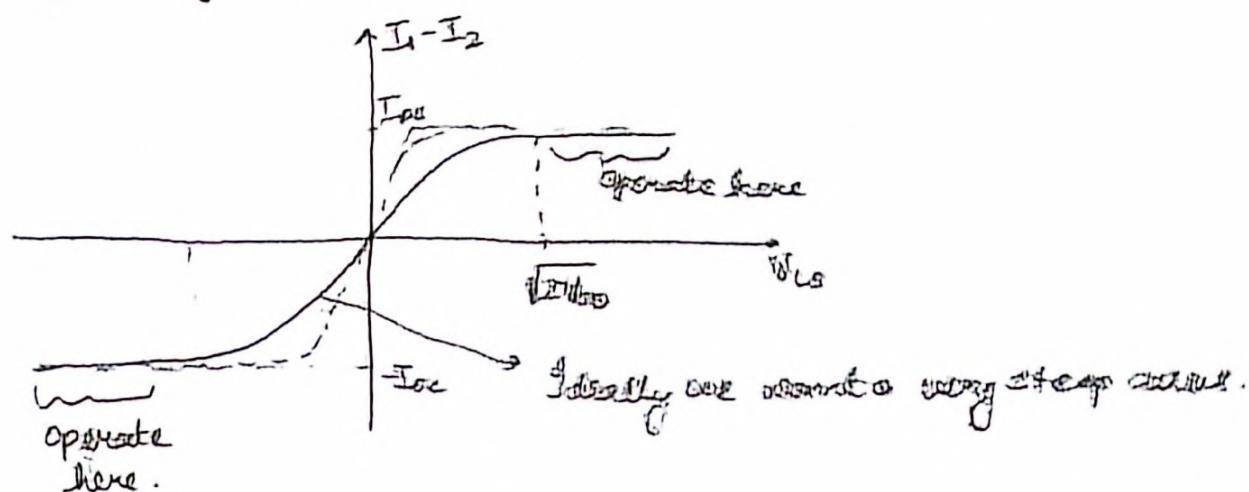- If V_{D2} is very large, current switches between I_1 and I_2



→ How to make it steeper → Also helps with FLICKER noise

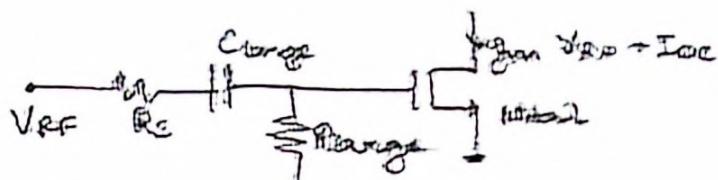
- Increase G_m (or $\frac{W}{L}$)
 - How? use a transistor



In saturation $G_m = g_m$.

♂ > large gm.

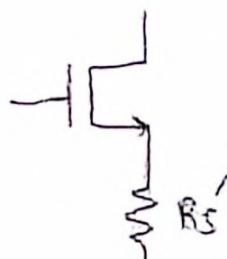
- > Nonlinear gm: G_m varies with V_{PF} → How to make it linear?
Source degeneration.



Problems : \rightarrow requires histogram

۷ نظر

>

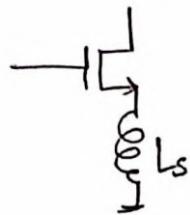

∴ > Linear gm

∴ > low noise (no noise if ideal)



∴ > No headroom issues

∴ > Could act as a filter for image frequency.
(We want to add filters wherever possible)


> Bias at velocity saturation to make gm (tail) more linear.

> However this is single balanced.


↳ unbalanced at RF.

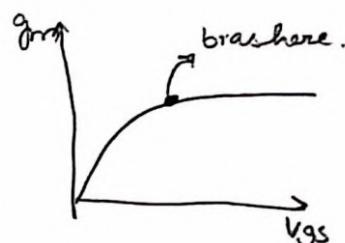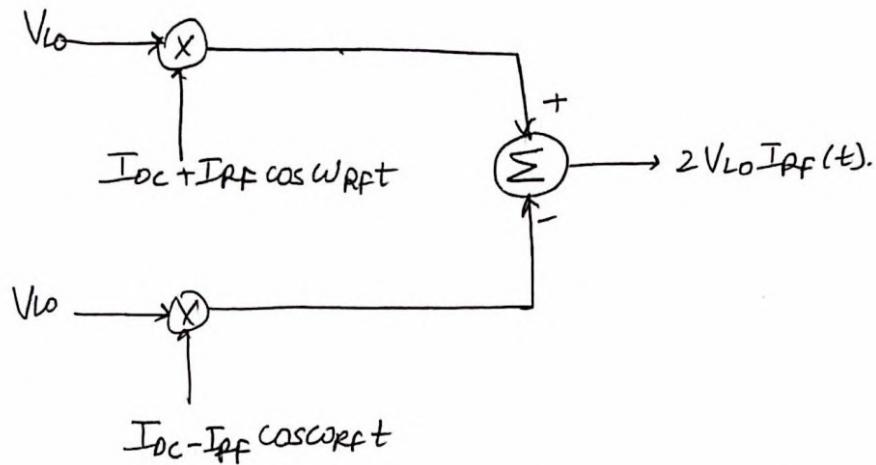Fix:

↓ Implementation


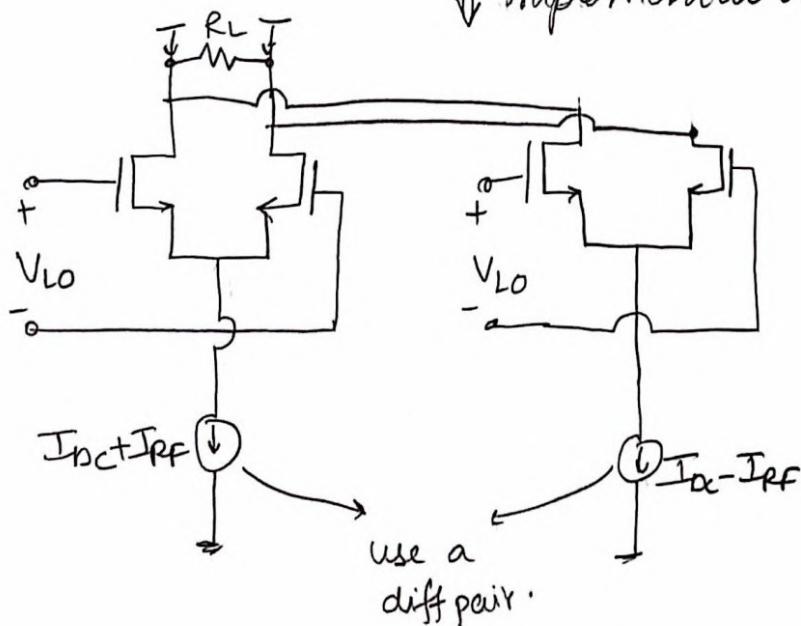


Gilbert Cell Mixer.

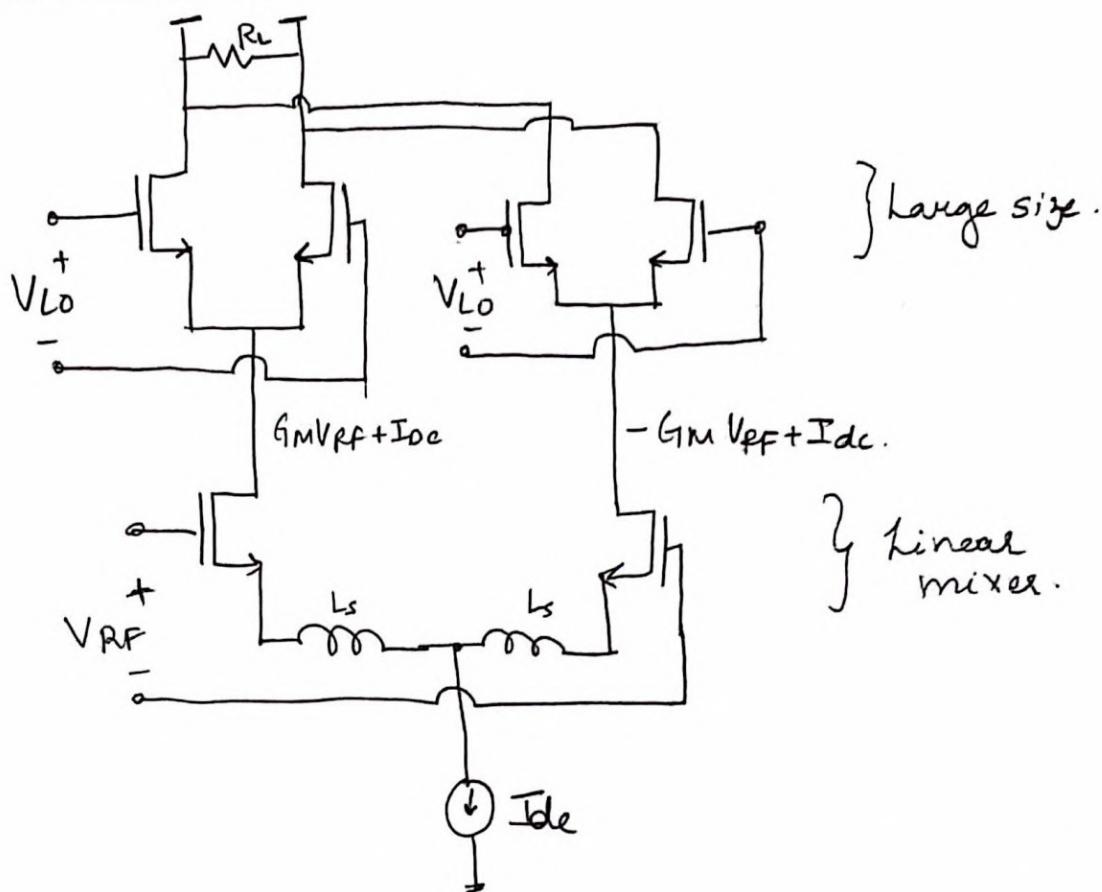


- > \approx High power.
- > Up conversion is same
- > For noise performance read H. Darabi, ISSCC 2005.

Current sharing between LNA and Mixer.

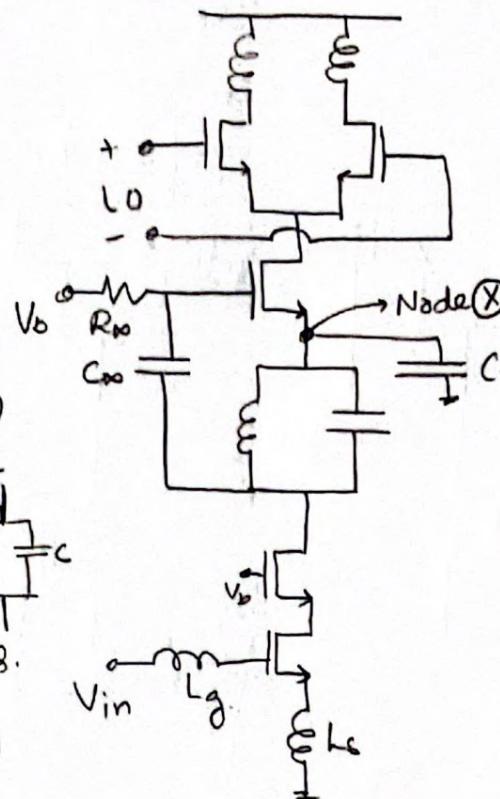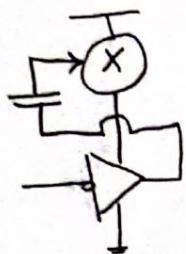

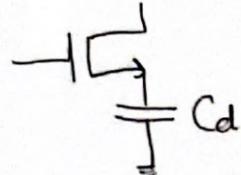- > Could play tricks at node(X)
 - place a resonant circuit to resonate at ω_{IM}
 - \Rightarrow open at ω_{IM} + mixer is degenerated heavily. High Q.
 - At $\omega_{IF} > \omega_{IM}$, it is a cap!



Gives negative real impedance at Z_{in} .


$$Z_{in} = Z_{gs} + Z_s + g_m Z_{gs} Z_s.$$

$$= \frac{1}{s Z_{gs}} + \frac{1}{s C} + \underbrace{\frac{g_m}{s^2 C_{gs} C}}_{\text{negative}}$$

\Rightarrow Gain is boosted at ω_{RF} or ω_{IF}


Paper : A. Zolfaghari, ISSC 2003 .

→ Could filter IM at LNA

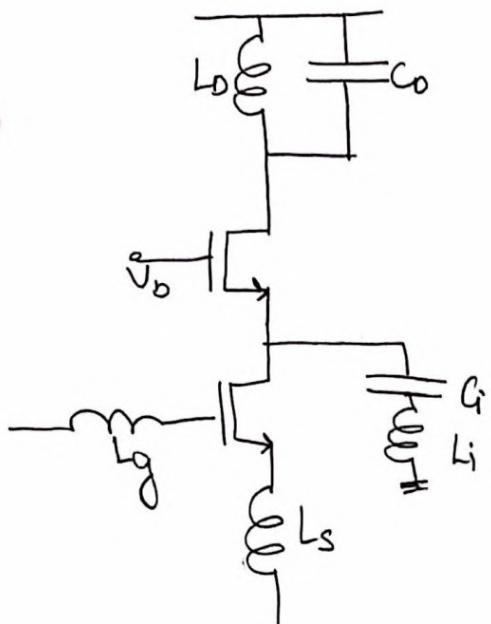

$L_0 \approx C_0$ resonate at $\omega_{IM} \Rightarrow$ short & gain = 0.
 $\omega_{RF} > \omega_{IM} \Rightarrow$ at ω_{RF}

In reality

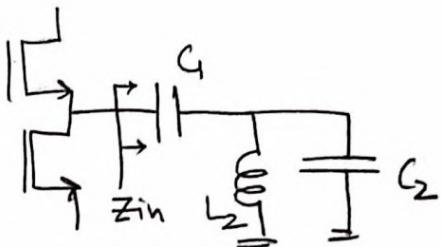


at ω_{IM} :- C_2 & L_2 are an inductor Leg.

L_{eq} & C_1 resonate at ω_{IM} .

at ω_{RF} C_2 & L_2 are an inductor. L_{eq}'
 $L_{eq}' < L_{eq} \Rightarrow L_{eq}' + C_1$ looks like an
inductor.

→ This way L_2 is small.


Paper : H. Samavati, ISSC.

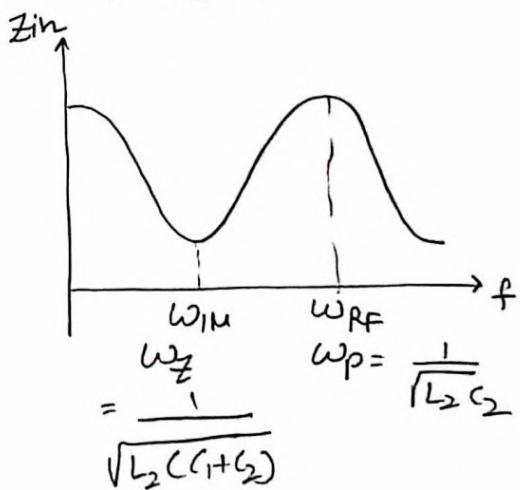

OSCILLATORS

- > Review feedback, root locus, Routh Hurwitz method to find gain at which poles cross the jω axis



Design

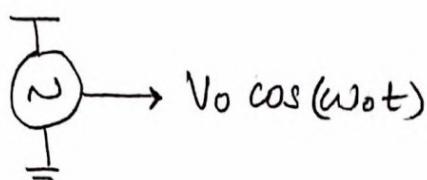

Requirements

- > Phase Noise (Gitter) ← related.
- > Power consumption (efficiency or % power)
- > Frequency
- > Tuning range of VCO ← tradeoff Phase noise.
- > Phase accuracy of multiphase oscillators.


(Trade off with phase noise)

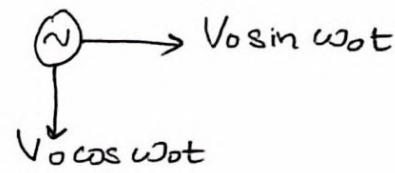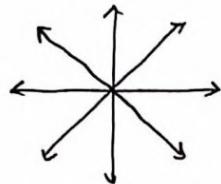

Types

- ① Resonance based:
 - good phase noise
 - good phase accuracy
 - High power
 - Large size.
 - ** Very high frequency.
- ② Ring oscillator:
 - Low power.
 - Small area.
 - High phase noise
 - Not as accurate.
- ③ Relaxation oscillators:
 - Very low power.


Basics

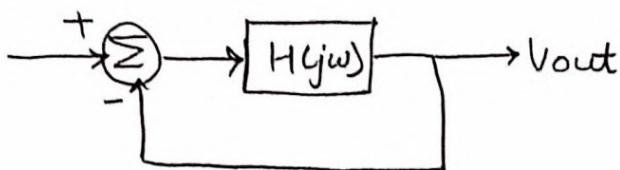



$$G = \frac{V_{out}}{V_{in}} = \frac{H}{1+H}$$

> Phase around loop should be 0° $\Rightarrow |H| = 1$ } Barkhausen
 $\Im H = (2n+1)\pi$ } Criteria.

Negative Resistance Viewpoint

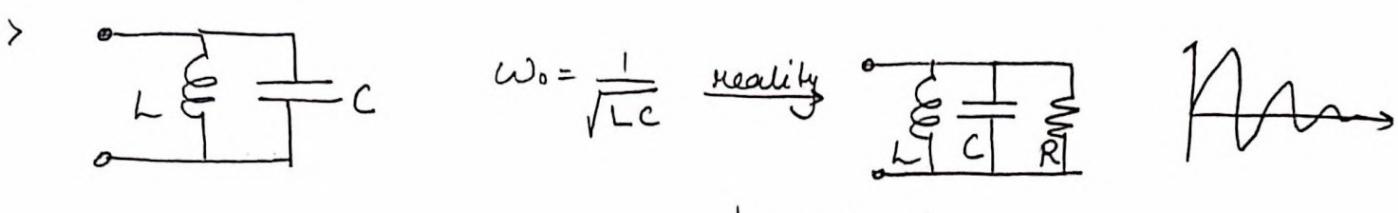

~~Ans~~

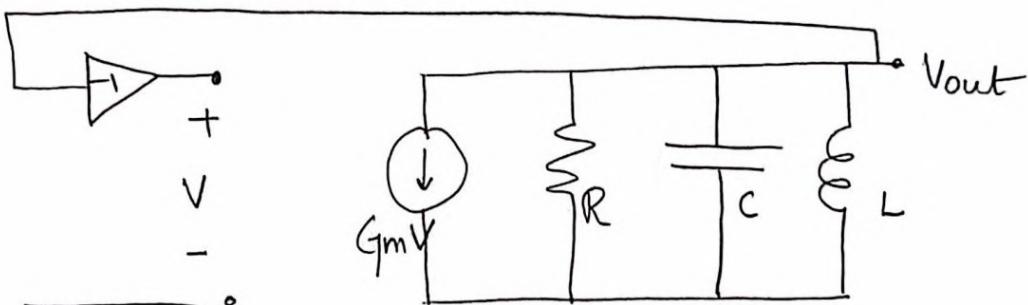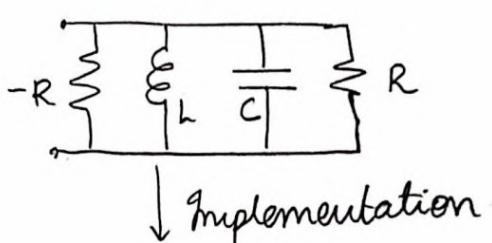


$$V = -V_{out} \Rightarrow G_m V = -G_m V_{out}$$

$\Rightarrow I = -G_m V_{out} \rightarrow$ Current source whose value \propto voltage across it \Rightarrow resistor.

$$\Rightarrow R = -\frac{1}{G_m}$$

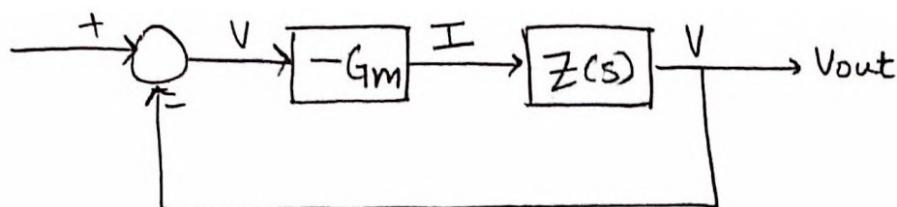$\Rightarrow -\frac{1}{G_m} = R$ gives oscillation!




$$Z(s) = \frac{Ls}{Lcs^2 + \frac{L}{R}s + 1}$$

$$\Rightarrow G_m \text{ desired} = \frac{1}{R}$$

At resonance $Z(s) = R$


$\Rightarrow |H| = G_m R = 1$ } Satisfies Barkhausen!
 $\angle H = 180^\circ$

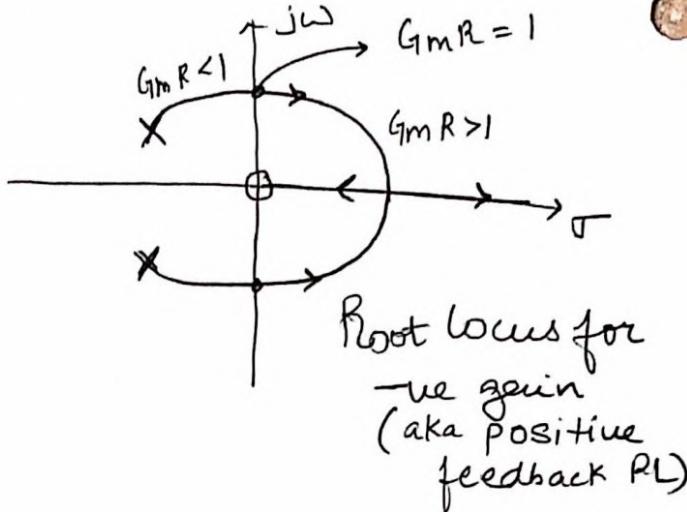





> How can we make $g_m = R$ exactly?

① Unpractical solution (Feedback)

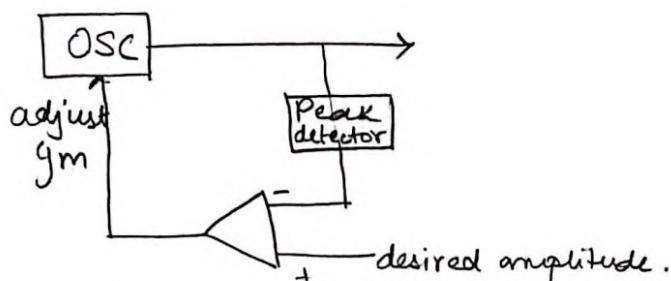
- ∴ Complex.
- ∴ Power \uparrow
- ∴ Noise \uparrow
- ∴ Stability
- ∴ Slow



② Nonlinearity.

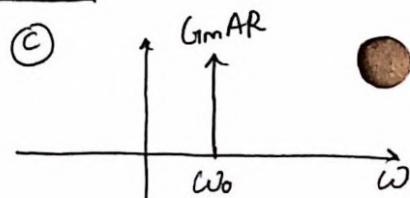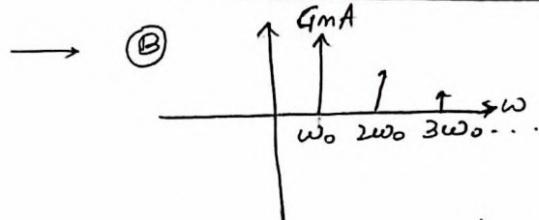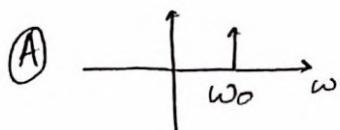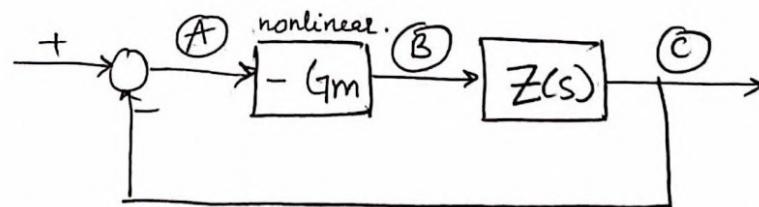

Assuming no filter harmonics

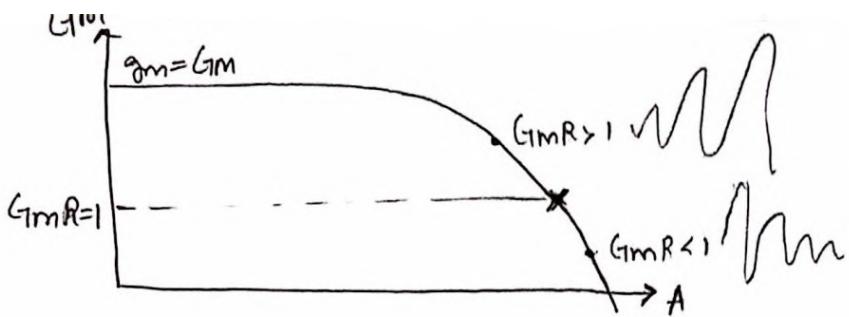

$G_m = \frac{\text{ratio of (fundamental) current}}{\text{voltage}}$

- > Startup condition : $G_m R > 1$ for small A .
- > Circuit stabilizes itself.

BJT example

$$i_C = I_s e^{\frac{V_{BE}}{V_T}}$$

$$V_{BE} = V_{DC} + V_1 \cos \omega t$$

$$\Rightarrow i_C = I_s \exp \left(\frac{V_{DC}}{V_T} + \frac{V_1 \cos \omega t}{V_T} \right)$$

$$= I_s \exp \left(\frac{V_{DC}}{V_T} \right) \left[I_0 + 2I_1 \cos \omega t + 2I_2 \cos 2\omega t + \dots \right]$$

Where,

$$I_0(x) = \frac{1}{2\pi} \int_{-\pi}^{\pi} e^{x \cos \theta} d\theta$$

$$I_n(x) = \frac{1}{2\pi} \int_{-\pi}^{\pi} e^{x \cos \theta} \cos n\theta d\theta$$

$$x = \frac{V_1}{V_T} \rightarrow \frac{kT}{q} = 25 \text{ mV}$$

$$\Rightarrow i_C = I_s e^{\frac{V_{DC}}{V_T}} \cdot I_0(x) \left[1 + 2 \sum_n \frac{I_n(x)}{I_0(x)} \cos n\omega t \right]$$

Average

$$\bar{i}_c = I_{Dc} = I_s e^{\frac{V_{Dc}}{V_T}} \cdot I_0(x) \quad \because \text{avg of cos} = 0$$

$$x=0 \Rightarrow \bar{i}_c = I_{Dc} = I_s e^{\frac{V_{Dc}}{V_T}}$$

x is small \Rightarrow

$$\begin{cases} I_0(x) = 1 \\ I_1(x) = \frac{x}{2} \end{cases} \Rightarrow i_c = I_{Dc} + \frac{2 \cdot \frac{x}{2} \cdot \cos \omega t}{1} + \dots$$

$$\Rightarrow i_c = I_{Dc} + x I_{Dc} \cos \omega t$$

$$= I_{Dc} + \frac{V_1}{V_T} I_{Dc} \cos \omega t$$

$$i_c = I_{Dc} + V_1 g_m \cos \omega t$$


\hookrightarrow Small signal g_m

x is large $\Rightarrow G_m = \frac{\text{find } \frac{dI}{V}}{V} = \frac{2 I_{Dc} I_1(x) \cos \omega t / I_0(x)}{V_1 \cos \omega t}$

$$= \frac{2 I_{Dc}}{V_1} \cdot \frac{I_1(x)}{I_0(x)}$$




$$= \frac{2}{x} \cdot \frac{I_{Dc}}{V_T} \cdot \frac{I_1(x)}{I_0(x)}$$
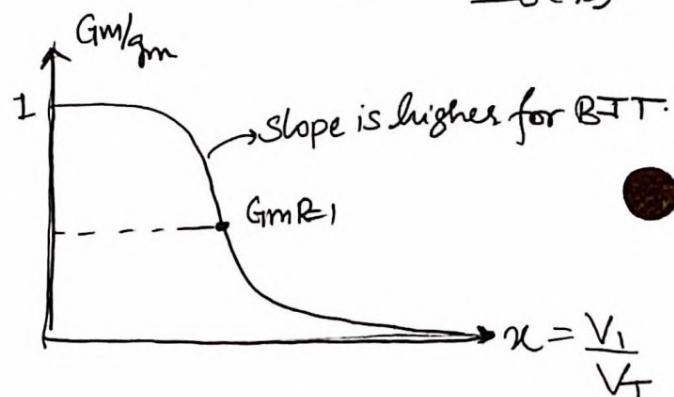
$$\boxed{\frac{G_m}{g_m} = \frac{2}{x} \cdot \frac{I_1(x)}{I_0(x)}}$$



Circuit

(I) Cross coupled oscillator

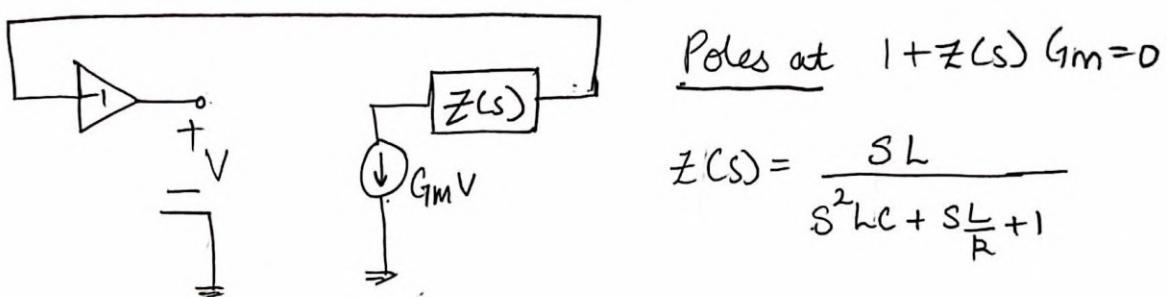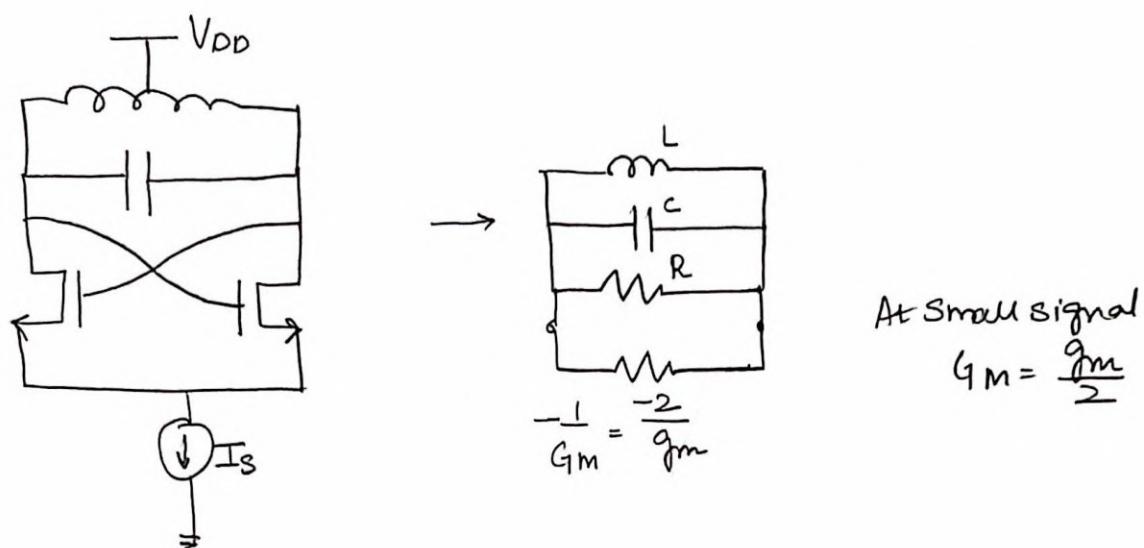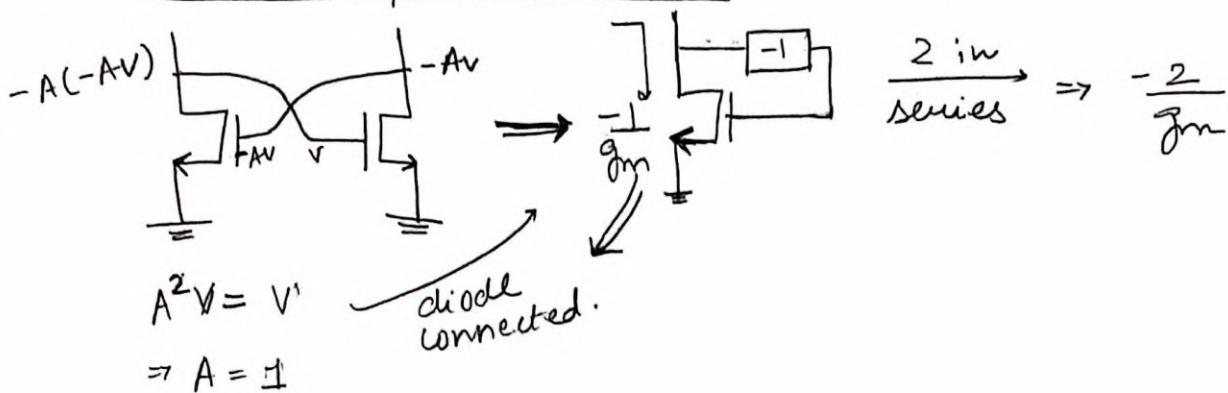

$$Z(s) = \frac{sL}{s^2 LC + s\frac{L}{R} + 1}$$

$$\Rightarrow 1 + \frac{sL}{s^2 LC + s\frac{L}{R} + 1} - \frac{g_m}{2} = 0 \xrightarrow[\text{Ch. eq.}]{=} (LC)s^2 + \left(\frac{1}{R} - \frac{g_m}{2}\right)LS + 1 = 0$$

Startup \Rightarrow the poles $\Rightarrow g_m > \frac{2}{R}$


$$g_m R > 2$$

$\left\{ R = R_p \text{ of tank at resonance.} \right.$

Amplitude of oscillations.




Assumptions

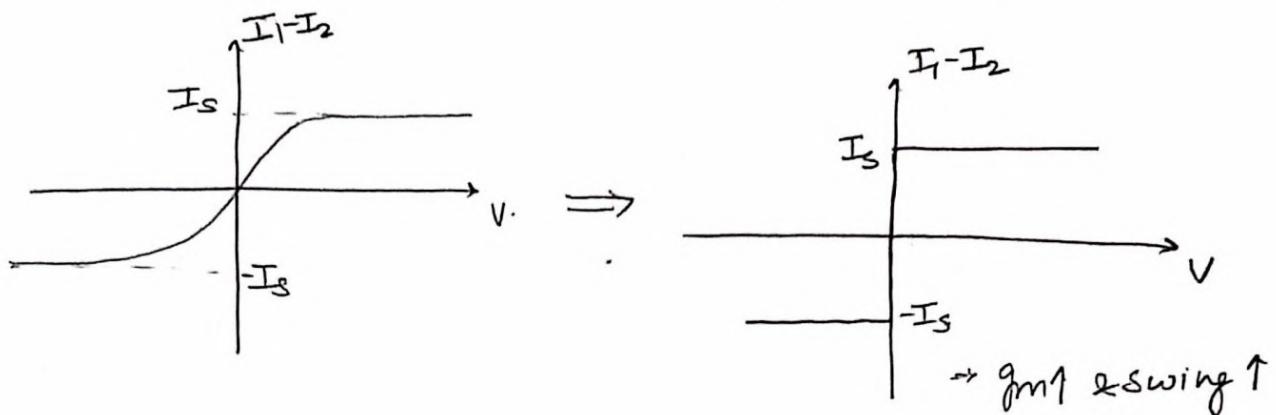- ① ω of LC tank is large enough to filter harmonics ($\omega \gg 2$)
- ② Assume the diff pair switches "ideally" \Rightarrow step function.



Derivation.

- ① Assume some oscillation at ω_p .

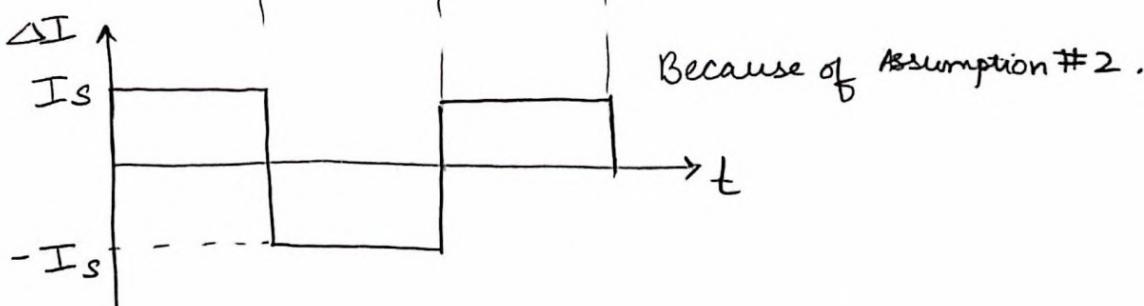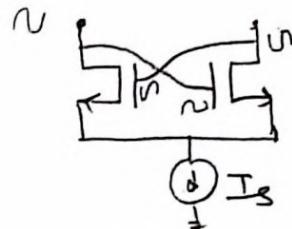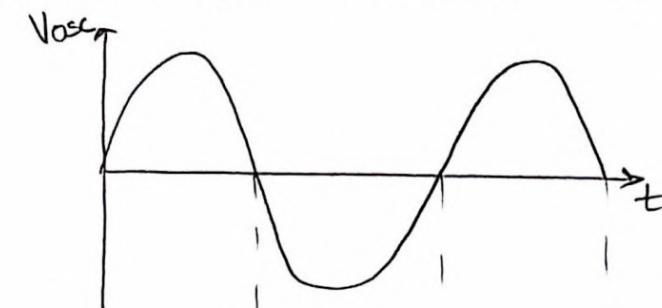


$$\Delta I = \frac{4}{\pi} I_s (\sin \omega_0 t + \frac{1}{3} \sin 3\omega_0 t + \frac{1}{5} \sin 5\omega_0 t \dots)$$

↪ Fourier series of square wave

> Assuming harmonics are filtered

$$V_o = \frac{4}{\pi} I_s R \Rightarrow G_m = \frac{4 I_s}{\pi V_o} \quad \rightarrow \text{Need to ensure } g_m R_p \gg 2$$

Oscillator derivation.

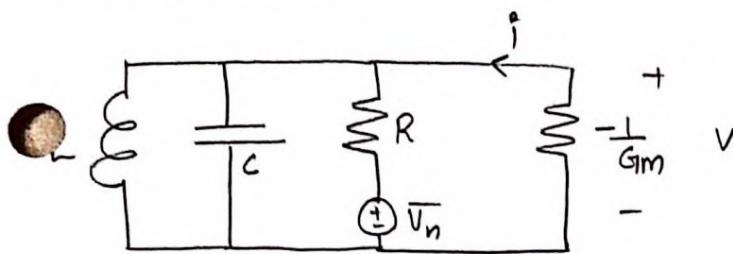

$$-\frac{V}{i} = -\frac{1}{G_m} \Rightarrow \frac{V}{i} = \frac{1}{G_m}$$

$$\text{KCL} \Rightarrow V_{Gm} = \frac{V}{sL} + V_{SC} + \frac{V - V_n}{R}$$

$$\Rightarrow V[G_m] = V \left[\frac{1}{sL} + SC + \frac{1}{R} \right] - \frac{V_n}{R}$$

$$\Rightarrow V[G_m - \frac{1}{Z(s)}] = - \frac{V_n}{R}$$

$$\Rightarrow \frac{V}{V_n} = \frac{-Z(s)/R}{G_m Z(s) - 1}$$

$$\Rightarrow \frac{V}{V_n} = \frac{Z(s)/R}{1 - G_m Z(s)}$$

Characteristic equation: $1 - G_m Z(s) = 0$

$$\Rightarrow 1 - G_m \left[\frac{sL}{s^2 LC + s \frac{L}{R} + 1} \right] = 0$$



$$\Rightarrow s^2 LC + s \left[\frac{L}{R} - G_m L \right] + 1 = 0$$

To get oscillations we need damping factor < 0


$$\Rightarrow \frac{L}{R} - G_m L < 0$$

$$\Rightarrow G_m > \frac{1}{R}$$



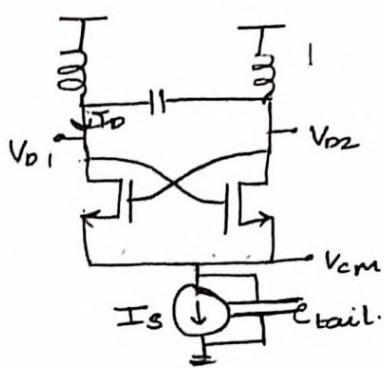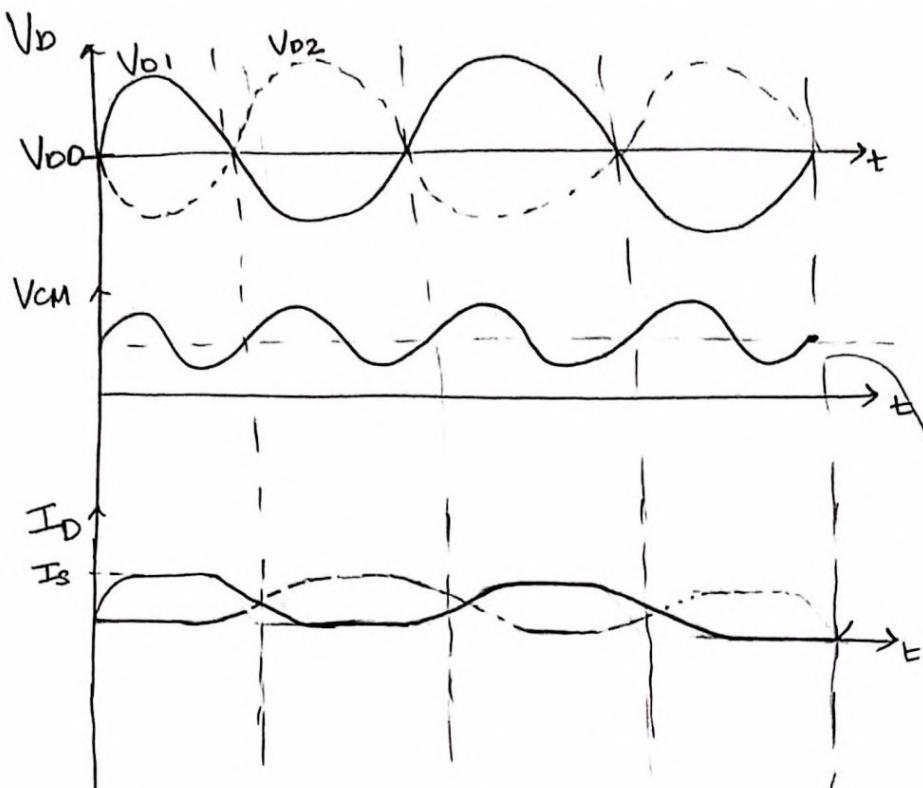


→ Twice the frequency.
Why?

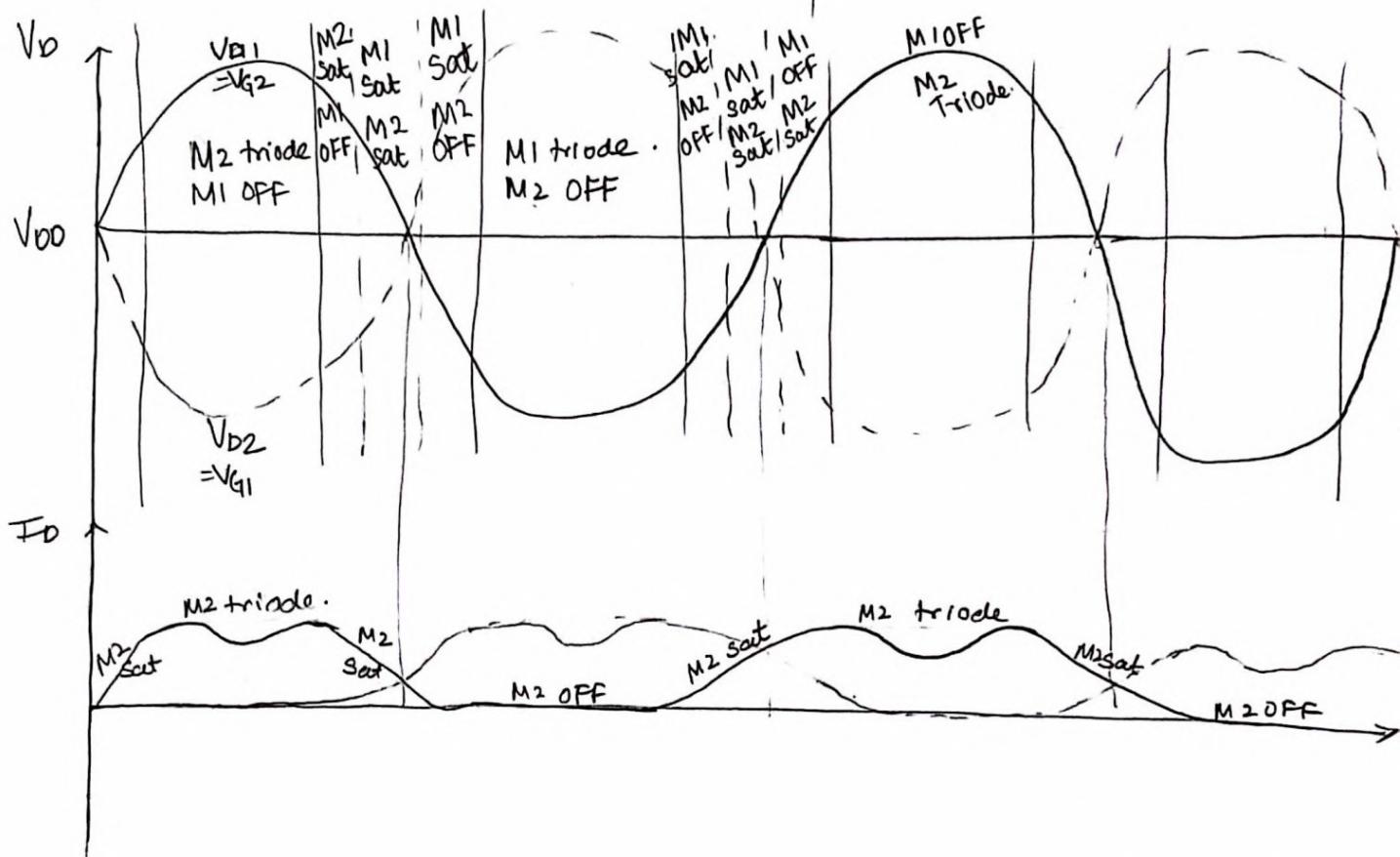


- V_{CM} is not constant since the current source is not an ideal AC open. The capacitance C_{tail} "steals" current every time M_1 or M_2 turns ON [since $I_{D1} + I_{D2}$ is not exactly I_s]. Therefore, its voltage goes up twice every cycle.

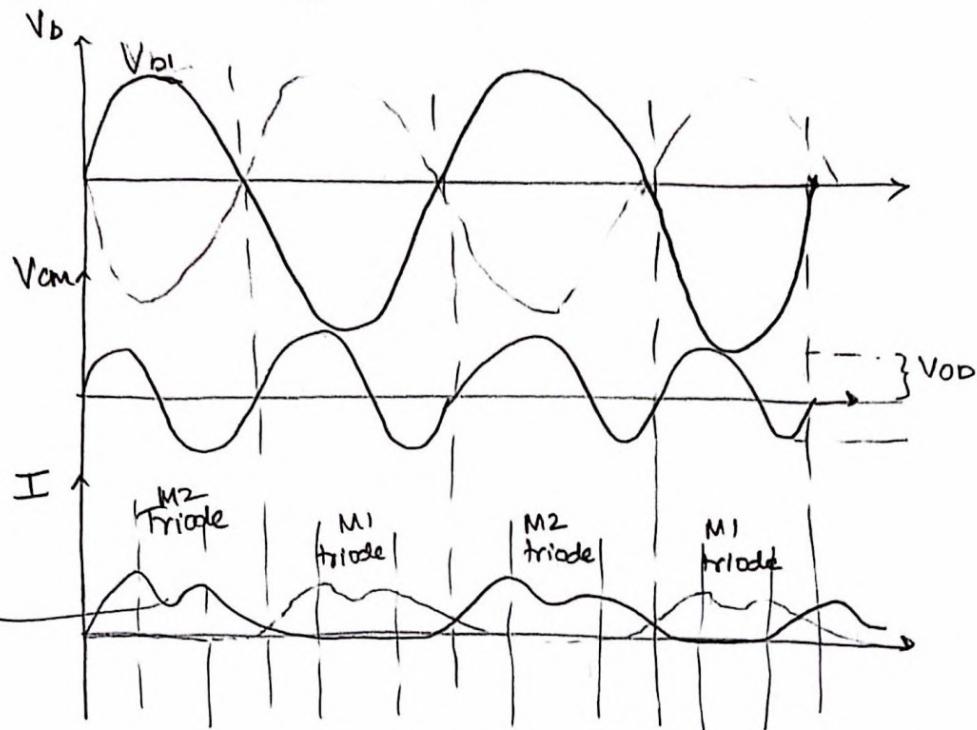- > Large swing $\Rightarrow I_s \uparrow \Rightarrow$ Current limited region.
- > Drain voltage swing \uparrow with I_s as long as it is above V_{cm} (by $1V_{ob}$).
- > V_{cm} should be large enough for I_{tail} to be in saturation.






$$\text{Max oscillation voltage} = \pm (V_{DD} - V_{cm}) \rightarrow (\text{ignoring triode})$$

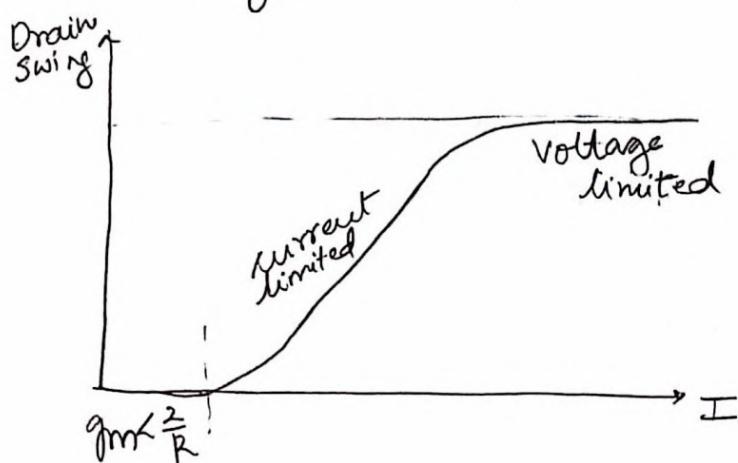
- > Voltage limited region: M_1 & M_2 go into triode during small period.
- > Current through branches would be \propto times larger.



Variations:

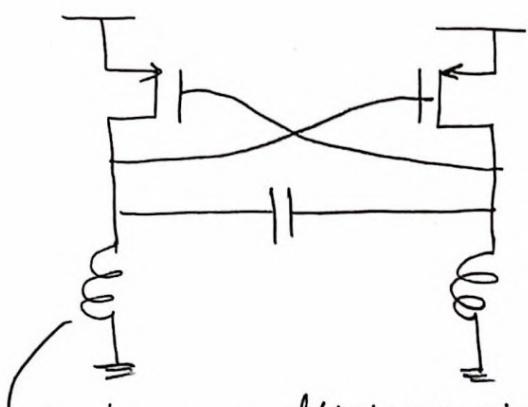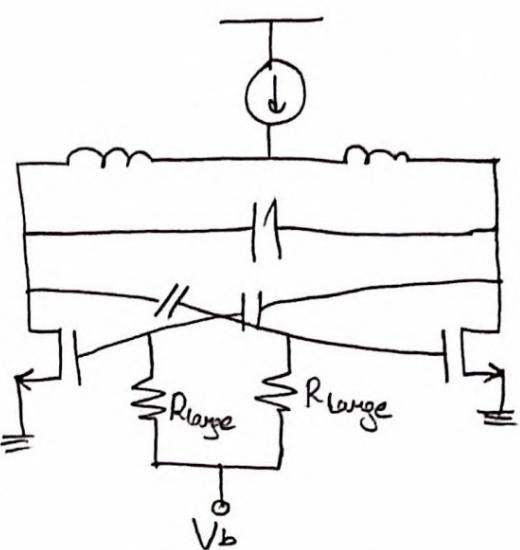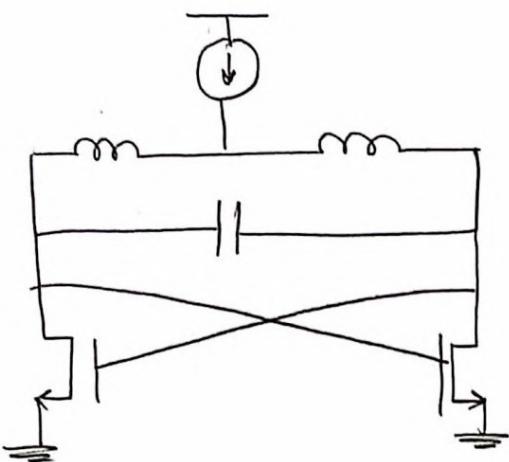


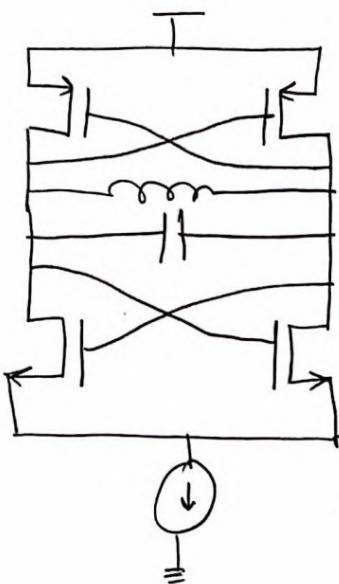→ lower flicker noise
of PMOS due to buried channel.



- Low phase noise since ISF is symmetric
- Higher g_m for same bias current
- Higher swing for same bias current
- Lower swing in voltage limited region.
- Difficult to bias & needs higher V_{DD} .

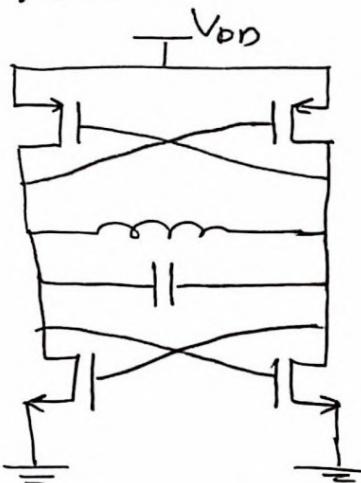
→ To remove tail noise and reduce V_{DD}
use voltage biased configuration




- Sizing needs to be right to limit current.

Three point oscillators




Colpitts

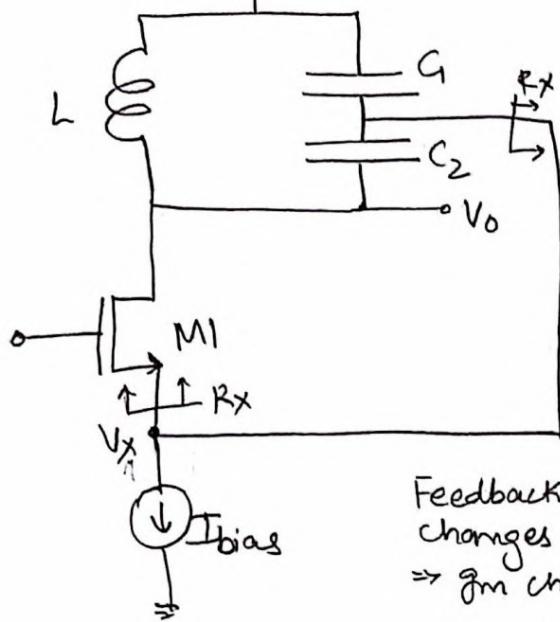


Hartley

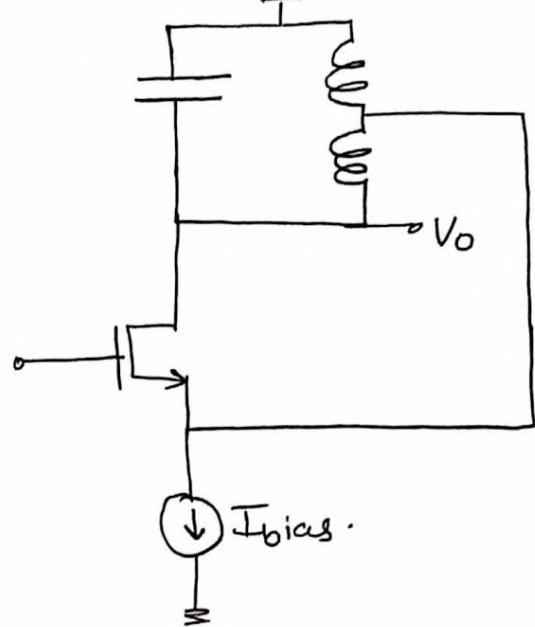

Analysis

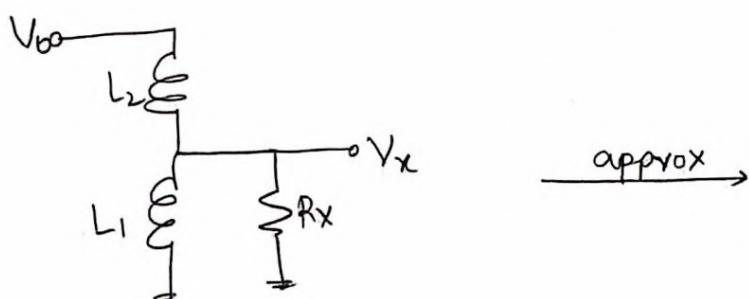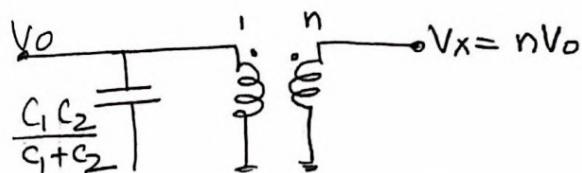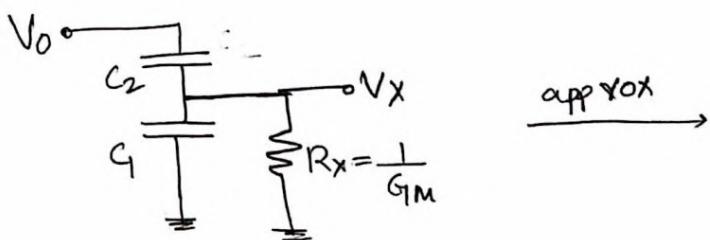

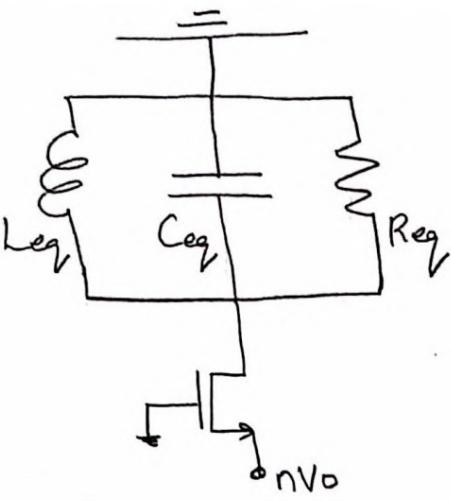

Colpitts

$$L_{eq} = L$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$n = \frac{C_2}{C_1 + C_2}$$


Hartley

$$L_{eq} = L_1 + L_2$$


$$C_{eq} = C$$

$$n = \frac{L_1}{L_1 + L_2}$$
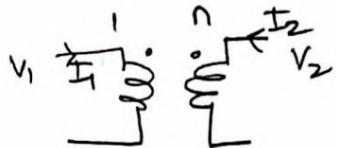
$$R_{eq} = \frac{R_x}{n^2} \quad \text{since} \quad \frac{V_1}{I_1} = \frac{R_x}{n^2}$$


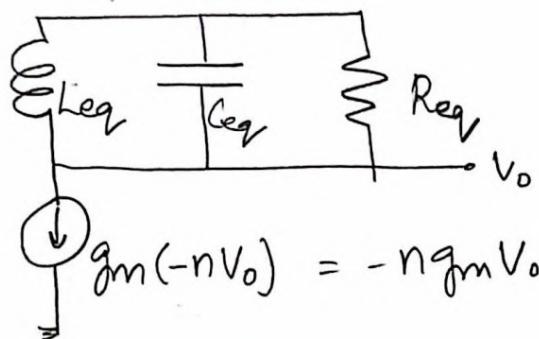
$$\begin{aligned} R_{eq} &= \frac{\text{small signal}}{g_m} \frac{1}{h^2} \\ &= \frac{1}{n g_m} \end{aligned}$$



$$\Rightarrow R = \frac{-1}{n g_m}$$


$$\omega_{osc} = \frac{1}{\sqrt{L_{eq} C_{eq}}}$$

$$\text{Startup} \quad -n g_m + \frac{1}{R_{eq}} < 0 \Rightarrow$$

$$g_m > \frac{1}{n R_{eq}}$$

Easier derivation:

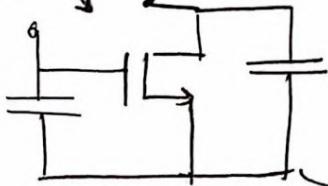
$$Z_{in} = \frac{1}{sC_1} + \frac{1}{sC_2} + \frac{g_m}{s^2 G C_2} \quad \rightarrow \text{negative resistance.}$$




$$\Rightarrow \frac{G C_2}{G + C_2} \frac{1}{s^2 G C_2} - \frac{g_m}{s^2 G C_2}$$

Three point oscillator.


Ground the gate

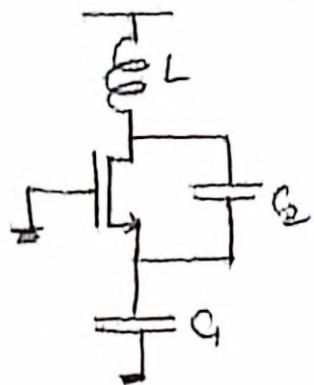

Ground the drain


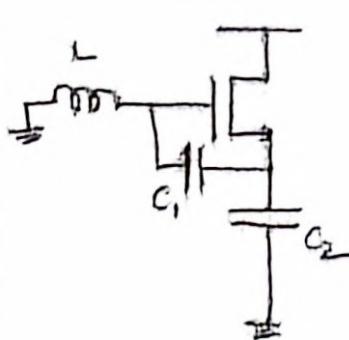


Ground the source

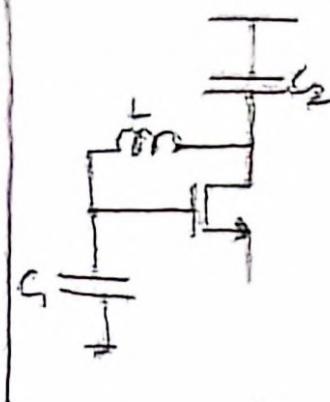

> Noise performance differs but W_{osc} is same!

Analysis

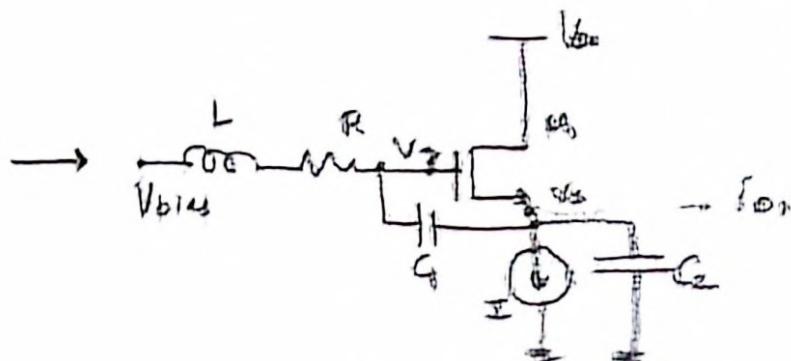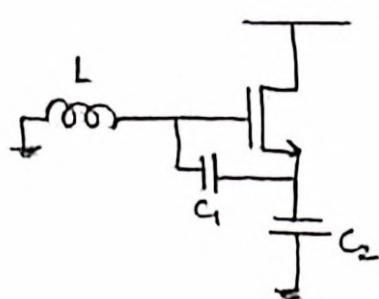

Find voltages and current waveforms


> Assume high ω_s , \Rightarrow voltages are single tone

$$\omega_o = \frac{1}{\sqrt{L \cdot \frac{C_1 C_2}{C_1 + C_2}}}$$

$$V_g = V_{bias} + V_o \sin \omega_o t$$

$$V_S = V_{bias} + \frac{C_1}{C_1 + C_2} V_o \sin \omega_o t$$
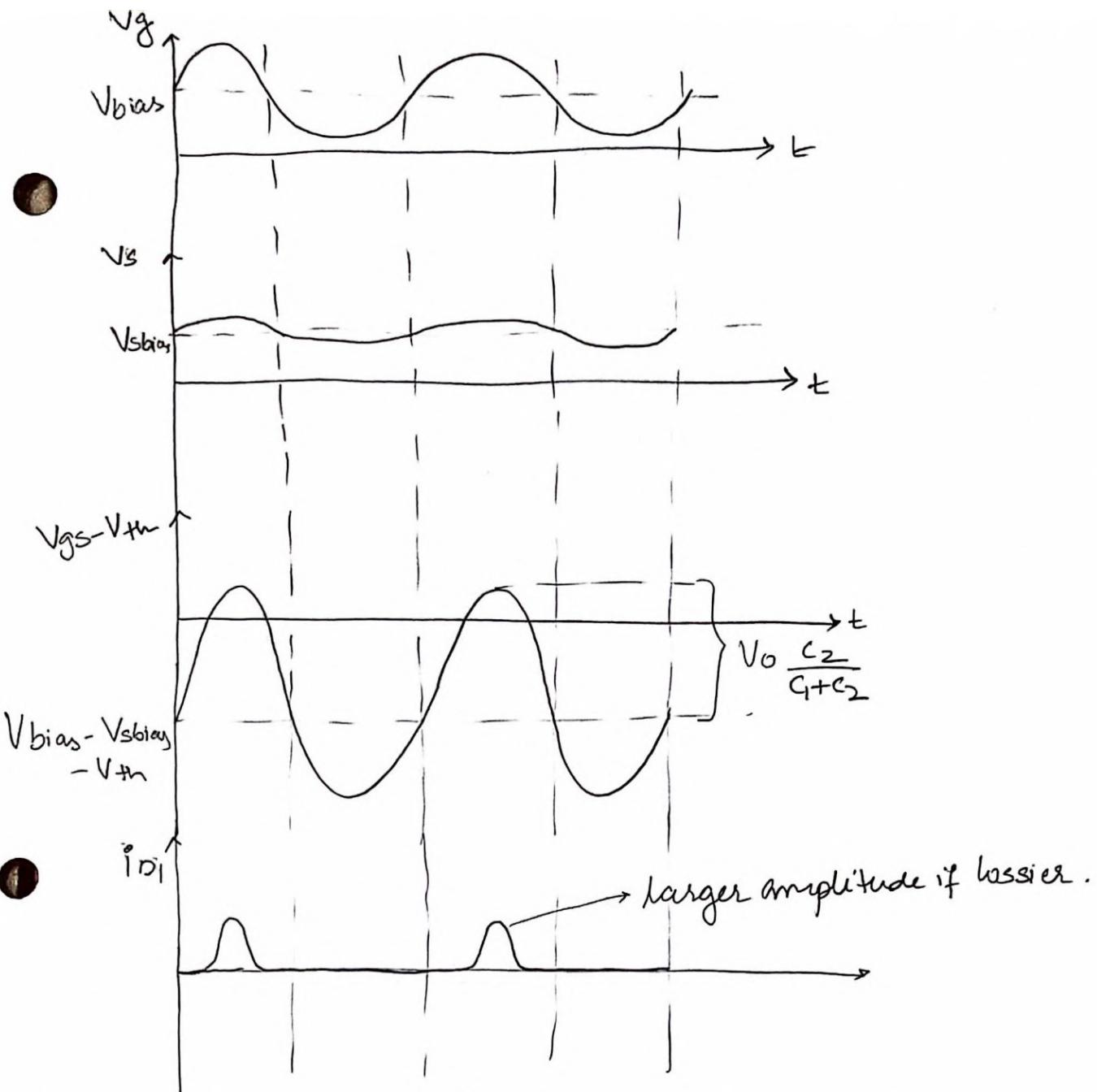
$$V_{gs} = V_{bias} - V_{bias} + \frac{C_2}{C_1 + C_2} V_o \sin \omega_o t$$



Energy is pumped into tank in short impulses.

$$\text{Avg } \langle i_{D_1} \rangle = I_{\text{bias}}$$

$$i_{D_1}(t) = I_0 + \sum_{n=1}^{\infty} a_n \cos(n\omega_0 t) + \sum_{n=1}^{\infty} b_n \sin(n\omega_0 t)$$

We care about fundamental. for amplitude of voltage.

$$\Rightarrow a_n = \frac{2}{T} \int_0^T i_b(t) \cos(n\omega_0 t) = 0 \rightarrow \text{assuming single tone sinusoid.}$$


$$b_1 = \frac{2}{T} \int_0^T i_b(t) \sin(\omega_0 t) \simeq \frac{2}{T} \int_0^T i_{D_1}(t) \sin(\omega_0 t)$$

→ When we have current flowing the sine is close to the peak

$$\Rightarrow b_1 = 2 I_{bias}$$


Oscillation amplitude

Use small signal.

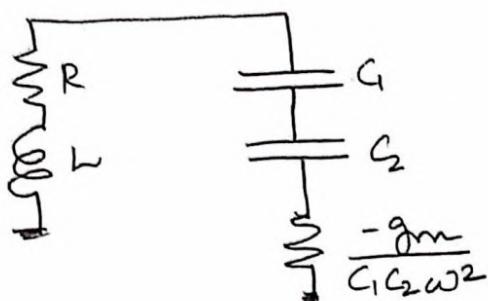


$$\text{Startup} \Rightarrow g_m > C_1 C_2 \omega^2 R$$

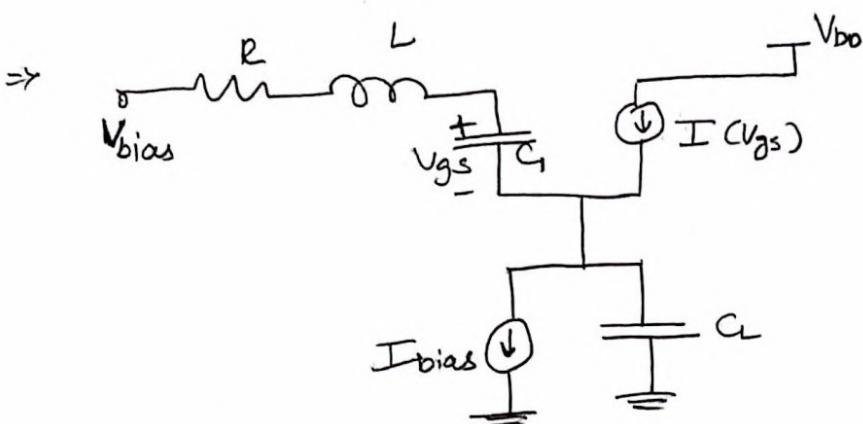In steady state, small signal model cannot be used.



At fundamental:

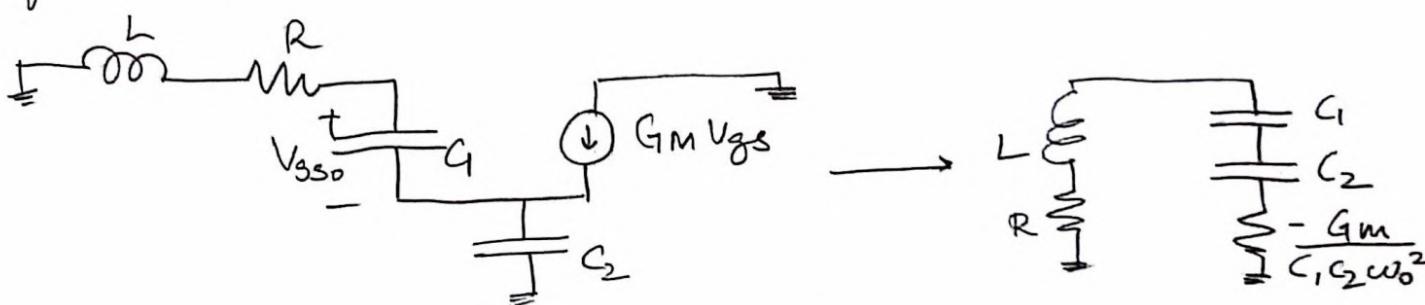

$$\text{At steady state: } R - \frac{G_m}{C_1 C_2 \omega_0^2} = 0$$

$$\begin{aligned} \Rightarrow G_m &= C_1 C_2 \omega_0^2 R \\ &= \frac{R(C_1 + C_2)}{L} \end{aligned}$$

$$\text{But, } G_m = \frac{I_{fund}}{V_{gs0}}$$

$$\Rightarrow G_M = \frac{2 I_{bias}}{V_{gso}} = \frac{G + C_2}{L} \cdot R$$

$$\Rightarrow V_{gso} = \frac{L}{C_1 + C_2} \cdot \frac{1}{R} \cdot 2 I_{bias}$$


$$V_{gso} = \frac{C_2}{G + C_2} V_0 \rightarrow \text{Voltage swing at fundamental}$$

$$\Rightarrow V_0 = \frac{L}{C_2} \cdot \frac{1}{R} \cdot 2 I_{bias}$$


Current limited region.

\rightarrow Independent of transistor.
 ↓
 just acts as
 a switch to
 "pump" energy



KING OSCILLATOR

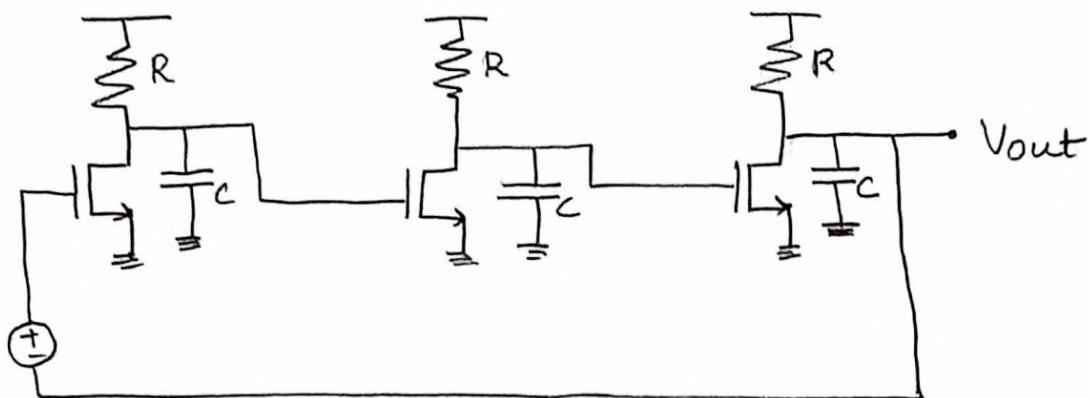

Model

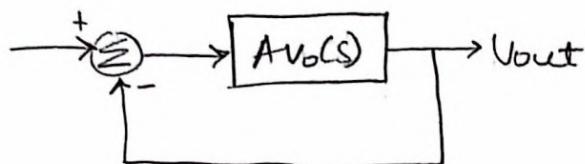
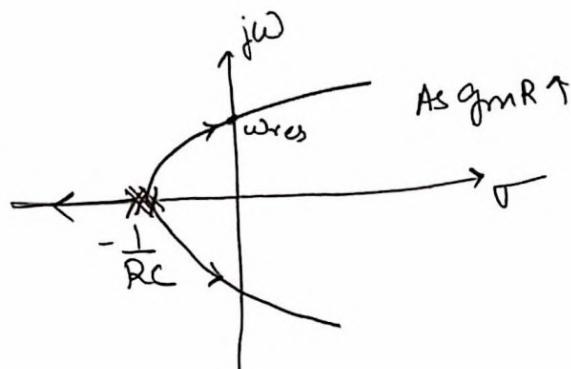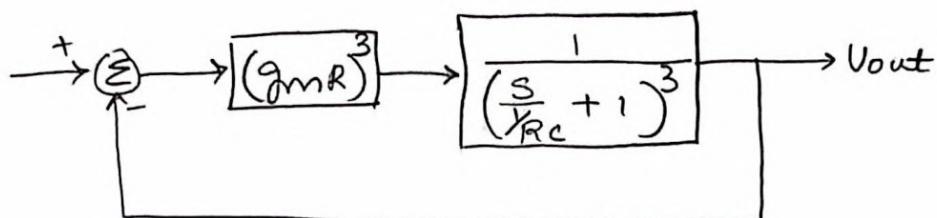
$$Av_o(s) = \left(\frac{g_m R}{Rcs + 1} \right)^3 \text{ ignoring 2nd order parasitics.}$$



$$\frac{(2n+1)180^\circ}{3} \rightarrow 60^\circ, 180^\circ, 300^\circ$$

$$\omega_a = -\frac{1}{RC}$$

$$\omega_0 \approx \frac{1}{RC} \cdot \tan 60^\circ$$

$$\omega_0 = \frac{\sqrt{3}}{RC}$$

Using RH table to find $g_m R$.

$$(Rcs + 1)^3 + (g_m R)^3 = 0$$

$$\Rightarrow (RC)^3 s^3 + 3(RC)^2 s^2 + 3RCs + 1 + (g_m R)^3 = 0$$

$$\begin{array}{c|cc}
 s^3 & (RC)^3 & 3RC \\
 s^2 & 3(RC)^2 & 1 + (g_m R)^3 \\
 s^1 & \frac{3(RC)^2 \cdot 3RC - (RC)^3 [1 + (g_m R)^3]}{3(RC)^2} & 0 \\
 s^0 & 1 + (g_m R)^3 & 0
 \end{array}$$


$$\Rightarrow 9(RC)^3 - (RC)^3 [1 + (g_m R)^3] < 0$$

$$\Rightarrow \boxed{g_m R > 2} \rightarrow \text{why } 2?$$


T.F of each stage is $\frac{g_m R}{Rcs + 1}$ \rightarrow We need $|TF| = 1$
 ~~$\times TF = 120^\circ$~~

$$\Rightarrow s = \frac{\sqrt{3}}{RC}. \text{ Solving, we get } g_m R = 2.$$

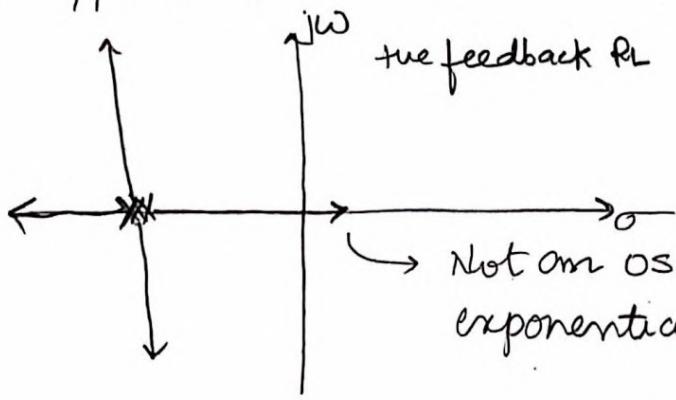
- Wres could be much lower. Why?
- Inputs to transistors are large \Rightarrow The capacitor could be charging. \Rightarrow Slew rate limited \Rightarrow Dont use large current sources.
- What happens if we use 4 stages.



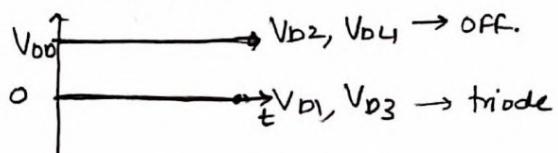Not an oscillator, amplitude grows exponentially and 'latches'.



> However if we had -ve feedback.

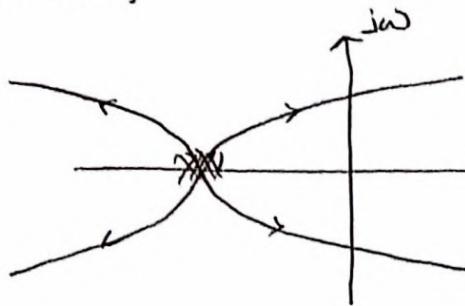

$$\Omega_a = -\frac{1}{RC}$$

$$\omega_0 = \frac{1}{RC} \tan 45^\circ$$

$\therefore \omega_0 = \frac{1}{RC} \rightarrow \text{lower.}$

$\therefore \text{More phases.}$

$$1 + Av(s) = 0$$



$$\left(\frac{g_m R}{RCS + 1} \right)^4 + 1 = 0$$

$$(RCS)^4 s^4 + 4(RC)^3 s^3 + 6(RC)^2 s^2 + 4RCS + 1 + g_m R = 0$$

s^4	$(RC)^4$	$6(RC)^2$	$1 + (g_m R)^4$
s^3	$4(RC)^3$	$4RC$	0
s^2	$5(RC)^2$	$1 + (g_m R)^4$	0
s^1	$\frac{20(RC)^3 - 4(RC)^3(1 + (g_m R)^4)}{5(RC)^2}$	0	0
s^0	$1 + (g_m R)^4$	0	0

> $g_m R > \sqrt{2}$

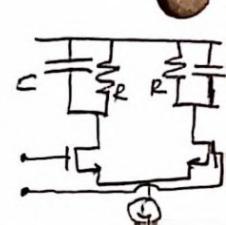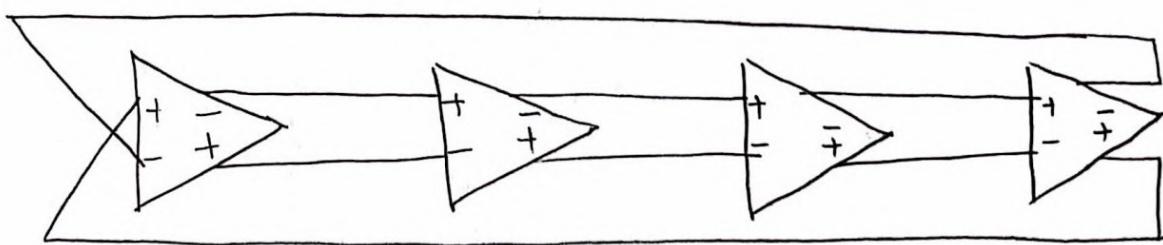=> Each stage must have 90° of phase. However for an RC stage $\omega \rightarrow \infty$ for 90° of phase. Fix? Differential.




∴ > Tolerance of gm & R is poor $\Rightarrow w_{res}$ is not well defined.

∴ low power.

∴ Small

∴ Multiphase

→ Resonance based Ring oscillator.

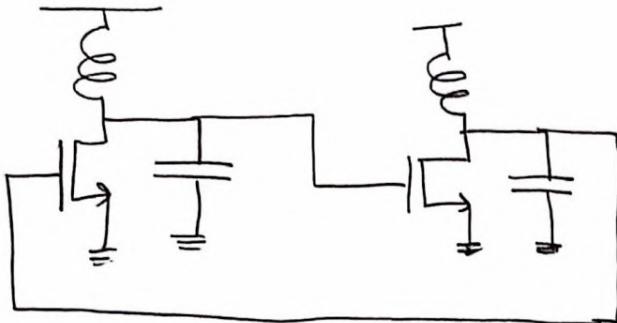

→ Cross coupled!

→ Only C cannot give 180° of phase for each stage since that happens at $\omega=0$

→ R, L, C can give $-90 \rightarrow -270^\circ$ of phase per stage.

→ ω is set when each cell has gain = 1 \Rightarrow phase = 180° .

→ Read paper by Afshari & Momeni on designing oscillators close to f_{max}

→ Phase Noise: [Hajimiri Lee paper.]

Lesson: $Z\{\Delta f\} = 10 \log \left\{ \frac{2KFT}{P_{sig}} \left[1 + \left(\frac{1}{2\pi} \frac{f_0}{\Delta f} \right)^2 \right] \left[\frac{1 + \Delta f_F^3}{10f_1} \right] \right\}$

F → Correcting coefficient

> Phase noise $\propto \frac{1}{P_{sig}} \propto \frac{1}{\Omega}$


> Active boosting of Ω doesn't work since F changes.

Phase noise basics


$$L\{\Delta\omega\} = 10 \log \frac{\text{Power in } 1\text{ Hz BW } \Delta\omega \text{ away from } \omega_0}{\text{Total carrier power.}}$$

dBc
Hz

$$A(t) \cos(\omega_0 t + \phi(t))$$

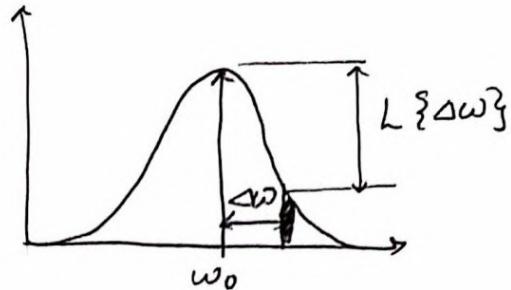

Phase noise model

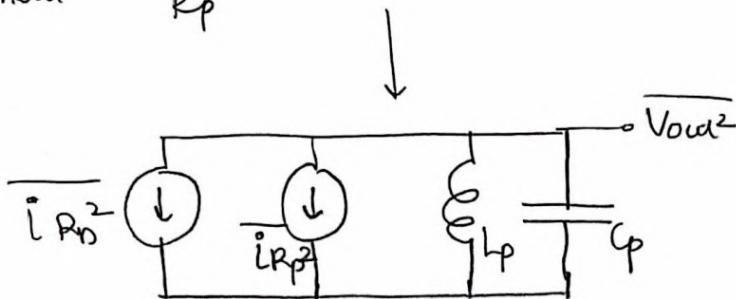

$$Z_{\text{tank}}(\omega) = \frac{1}{j C_p \omega} || j L_p \omega = \frac{j L_p \omega}{1 - \omega^2 L_p C_p}$$

$\hookrightarrow \omega = \omega_0$
 $\Rightarrow Z_{\text{tank}} = \infty$
 $\Rightarrow \text{amplifies current to } \infty.$

$$Z_{\text{tank}}(\omega_0 + \Delta\omega) = \frac{j L_p (\omega_0 + \Delta\omega)}{1 - (\omega_0 + \Delta\omega)^2 L_p C_p}$$

$$\begin{aligned}
 &= \frac{j L_p \omega_0}{(1 - L_p C_p \omega_0^2) - 2 \omega_0 \Delta\omega L_p C_p} \underset{n}{\sim} \frac{-j}{2} \frac{1}{\omega_0 C_p} \frac{\omega_0}{\Delta\omega}
 \end{aligned}$$

Even when $\Delta\omega \neq 0$, Z_{tank} is high and it amplifies the noise. (89)

$$Z_{\text{tank}}(\omega_0 + \Delta\omega) = -j \cdot \frac{R_p}{2} \cdot \frac{\omega_0}{\Delta\omega}$$

$$\frac{\overline{V_{\text{out}}^2}}{\Delta f} = \left(\frac{\overline{i^2 R_p^2}}{\Delta f} + \frac{\overline{i^2 R_n^2}}{\Delta f} \right) |Z_{\text{tank}}(f)|^2$$

$$= \left(\frac{4kT}{R_p} + \frac{4kT}{R_n} \right) \left(\frac{R_p}{2Q} \left(\frac{f_0}{\Delta f} \right) \right)^2$$

From Equipartition theorem, half of noise power goes to amplitude and half to phase.

$$\frac{\overline{V_{\text{out}}^2}}{\Delta f} = \left(\frac{2kT}{R_p} + \frac{2kT}{R_n} \right) \left(\frac{R_p}{2Q} \cdot \frac{f_0}{\Delta f} \right)^2$$

$$L\{\Delta f\} = 10 \log \frac{S_{\text{noise}}}{P_{\text{signal}}}$$

Assume $R_p = R_n$


$$L\{\Delta f\} = 10 \log \left\{ \frac{4kT}{P_{\text{sig}}} \left(\frac{1}{2Q} \cdot \frac{f_0}{2\Delta f} \right)^2 \right\}$$

Check derivation!
Doesn't seem right

Define a parameter $F = \frac{\text{total noise in tank @ } \Delta f}{\text{noise in tank due to tank loss @ } \Delta f}$

$$= 1 + \frac{\overline{i^2 R_n / \Delta f}}{\overline{i^2 R_p / \Delta f}}$$

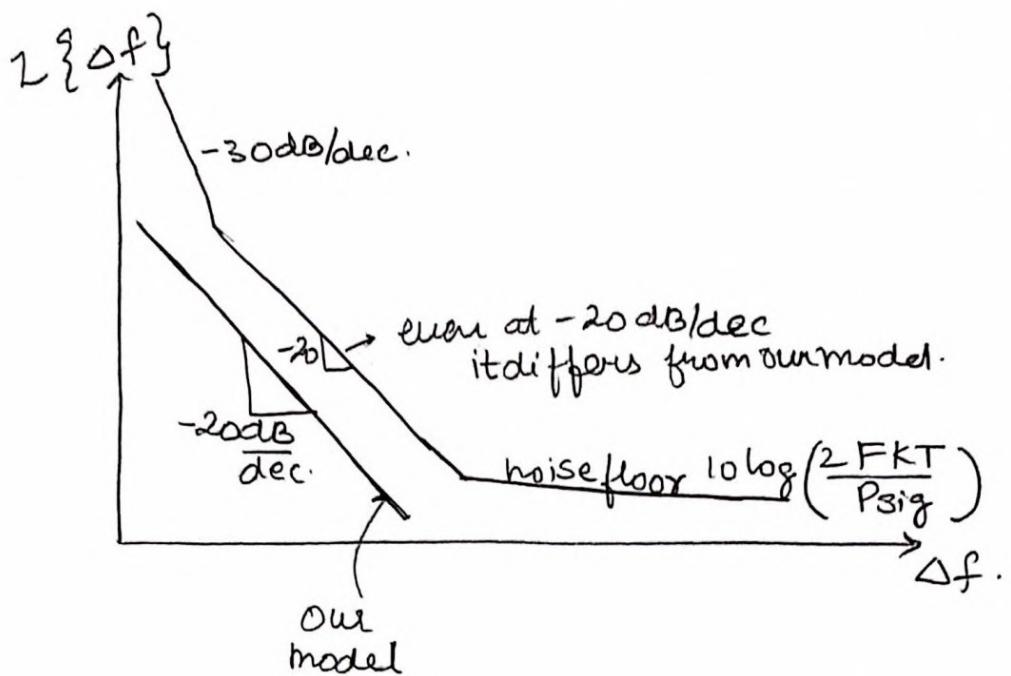If we include flicker noise, we would see the -30dB/dec. don't



- Noise floor could be from measurement setup or output buffer or from more complex models of L & C for high frequency.
- Improved model → Leeson model.
- More improved → ISF model
- Most recent / accurate (used in Cadence) → Demir model.

Transceiver Considerations


(I) Receivers

General Considerations

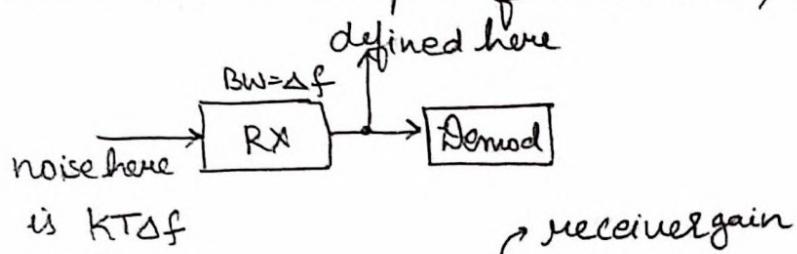- 1) Frequency
- 2) Dynamic Range
- 3) Gain
- 4) Pde
- 5) Image rejection.

Noise Floor

Noise power at the output of receiver, before the demodulator




$$\Rightarrow \text{Noise floor} = K T \Delta f \cdot G \cdot F \quad \rightarrow \text{noise of receiver.}$$

Sensitivity: Function of noise floor and SNR required.

"Min. signal that can be detected".


$$S = K T \Delta f \cdot F \rightarrow \text{Assuming demodulator only needs an SNR of 1.}$$
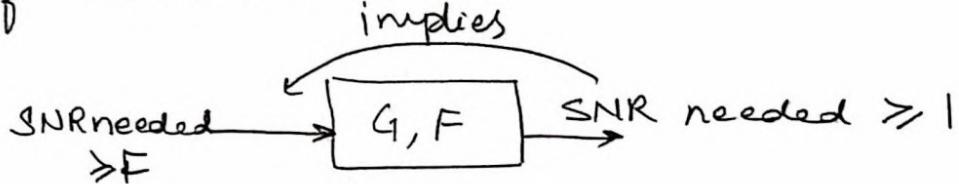
> In reality demodulator needs an SNR that depends on type of modulation.



> Higher order modulation \Rightarrow SNR needed is higher
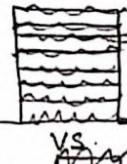
$$S = K T \Delta f \cdot F \cdot \text{SNR}_{\text{Rx}} \rightarrow \text{depends on modulation and } R = R$$



> SNR_{Rx} would be less than 1, but BW required would be high.

$$\rightarrow S(\text{dBm}) = -174 \text{ dBm} + 10 \log \frac{\Delta f}{1 \text{ Hz}} + \text{NF (dB)} + \text{SNR (dB)}$$

$\nearrow \text{KT at } 300K$

Eg: BPSK \rightarrow BER is $10^{-6} \Rightarrow \text{SNR required} = 12.5 \text{ dB}$

BAM is $10^{-6} \Rightarrow \text{SNR required} = 27 \text{ dB}$

to retrieve information.

Eg: $\text{BER} = 10^{-6} \Rightarrow \text{SNR} = 14 \text{ dB}$ QPSK.

$\Delta f = 1 \text{ GHz}$ assuming NF = 9 dB.

$$\Rightarrow S = -174 + 10 \log \frac{1 \text{ GHz}}{1 \text{ Hz}} + 9 + 14$$

$S = -61 \text{ dBm}$

$\Rightarrow \text{In Watt}$

Eg: 5 GHz LAN $\Rightarrow \Delta f = 20 \text{ MHz}$, SNR = 14 dB, NF = 6 dB,

$$S = -174 + 10 \log \frac{20 \text{ MHz}}{1 \text{ Hz}} + 6 + 14$$

$S = -81 \text{ dBm}$


Phase Noise

$L \{ \Delta f_{\text{in}} \} = \max \text{ PN that you can tolerate}$

$$= P - C - I - 10 \log \frac{\Delta f_{\text{in}}}{\text{channel BW}}$$

↓ ↓ ↓ ↓
 channel BW desired signal level adjacent channel rejection Interference power level

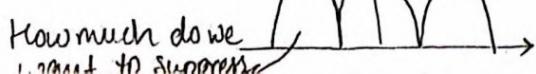Approximating that interference is constant in each band.



Eg:

> 60 GHz signal

> P = -60 dBm

> C = 14 dB

I = -38 dBm

$\Delta f = 1.8 \text{ GHz} \rightarrow \text{Huge offset}$

$$L\{1.8 \text{ GHz}\} = -60 - 14 + 38 - 92.55$$

$$= -128.55 \text{ dBc/GHz at } 1.8 \text{ GHz offset.}$$

Transmitter Specifications

> freq. of operation

> Pout \rightarrow Based on standard. [Japan 60 GHz \rightarrow 10 dBm
USA 60 GHz \rightarrow 27 dBm.

> EVM \rightarrow Error vector magnitude.

> Noise  jitter is more important.

> Rough estimate: $t_{rms} \approx \frac{1}{f_0} \sqrt{2 \cdot L \cdot \Delta f}$

Link budget analysis

$$P_{Rx}(d) = \underbrace{P_{Tx} \cdot G_{Tx}}_{\substack{\text{EIRP} \\ \downarrow \\ \text{Antenna gain}}} \cdot G_{Rx} \cdot \left(\frac{\lambda}{4\pi d} \right)^2$$

prop. loss in free space

G = directivity

Efficiency

Like an omnidirectional transmitter.



EIRP: Power $\cdot G_{Tx}$

$$P_{Rx}(d) > S$$

Link works.

Usually $P_{Rx}(d) > S$ by 10 dB.

$$\text{Eg: } f = 60 \text{ GHz.}$$

$$d = 2 \text{ m}$$

$$P_{\text{Tx}} = 0 \text{ dBm}$$

QPSK modulation: $\text{BER} = 10^{-6} \Rightarrow \frac{\text{SNR}_{\text{Rx}}}{\text{BER}} = 14 \text{ dB.}$

$\Delta f = \text{BW} = 2 \text{ GHz.} \Rightarrow R_b = 4 \text{ Gbps from Nyquist.}$

$$N F_{\text{Rx}} = 7 \text{ dB}$$

$$G_{\text{Rx}} = G_{\text{Tx}} = 25 \text{ dB} \rightarrow \text{very good.}$$

$$P_{\text{Rx}} = P_{\text{Tx}} + G_{\text{Tx}} + G_{\text{Rx}} + 20 \log \left(\frac{\lambda}{4\pi d} \right) \xrightarrow[2 \text{ m}]{5 \text{ mm}}$$

$$= 0 + 25 + 25 - 174 = -24 \text{ dBm}$$

$$S = -174 \text{ dBm} + 10 \log \underbrace{(2 \times 10^9)}_{\Delta f} + 7 \text{ dB} + 14 \text{ dB}$$

$$\boxed{S = -60 \text{ dBm.}} \Rightarrow \text{Link works.}$$

Modulations

ASK

$$s(t) = m(t) \cos(\omega_0 t) \quad m = 0, 1.$$

$$\begin{array}{l} \text{Prob of error} \\ \text{erfc} \end{array} \quad P_e = \frac{1}{2} \operatorname{erfc} \sqrt{\frac{E_b}{4n_0}} \quad E_{b.} = \int_0^T s^2(t) dt$$

Bit energy in one period


$$n_0 = \text{noise level [W/Hz]}$$


$$S = \text{Signal power} = E_b \times R_b$$



bit rate [bits per second]

$$N = \text{noise power} = n_0 \cdot \Delta f$$

$$\frac{E_b}{n_0} = \text{SNR} \cdot \frac{\Delta f}{R_b}$$

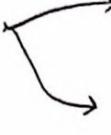➤ BER  ratio definition : no. of error bits per no. of bits.

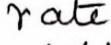 rate definition : no. of errors in one time period.

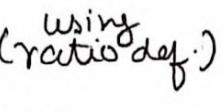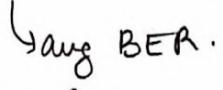Prob. of error $P_e = \overline{\text{BER}}$ 
 using BER.

Usually $P_e \leftrightarrow \text{BER}$ are considered same.

FSK Easy to design PA since amplitude is constant.

$$s(t) = \cos [(\omega_2 + m(t) \Delta\omega) t]$$


$$\begin{aligned}\Delta\omega &= \omega_1 - \omega_2 \\ &= 2\pi(f_1 - f_2)\end{aligned}$$

$$\text{BW} = 2 (\Delta f + \frac{2}{T}) \xrightarrow{\text{depends on demodulation.}}$$


 period of the signal / binary data rate. or $m(t)$.

Demodulation

Coherent / synchronous

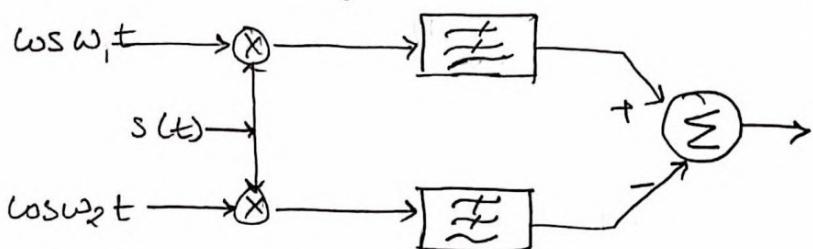

Asynchronous

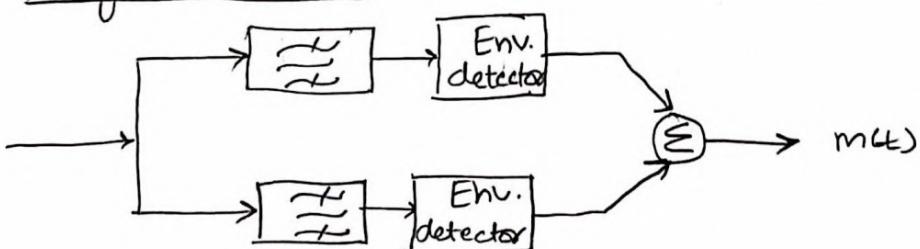

$$P_e = \frac{1}{2} \operatorname{erfc} \sqrt{\frac{E_b}{2n_0}} \rightarrow \text{Better?}$$

If we normalize to power (in E_b) it is not.

PSK

$$s(t) = m(t) \cdot \cos(\omega_0 t)$$

$\hookrightarrow m(t) = +1, -1$ polar NRZ

$$P_e = \frac{1}{2} \operatorname{erfc} \sqrt{\frac{E_b}{N_0}} \rightarrow \text{After normalizing it is same.}$$

MPSK

$$s_i(t) = A \cos(\omega_0 t + \phi_i)$$

$$\phi_i = 2\pi \cdot \frac{i}{M} \quad M = 2^n; i = 0, \dots, M-1, \circ n = \text{no. of bits per symbol}$$

BPSK $\rightarrow m=2$; QPSK $\rightarrow m=4$.

> Could use I & Q to represent M phase states.

QAM


$$s_k(t) = a_k \cos(\omega_0 t) + b_k \sin(\omega_0 t).$$

For BER = 10^{-6}


<u>modulation</u>	<u>BW efficiency η</u>	<u>SNR required (dB)</u>
BPSK	1	12.5
4FSK	2 (bits per symbol)	17
QPSK	2	14
8PSK	3	19
16QAM	4	21
64QAM	6	27

Receiver Architectures

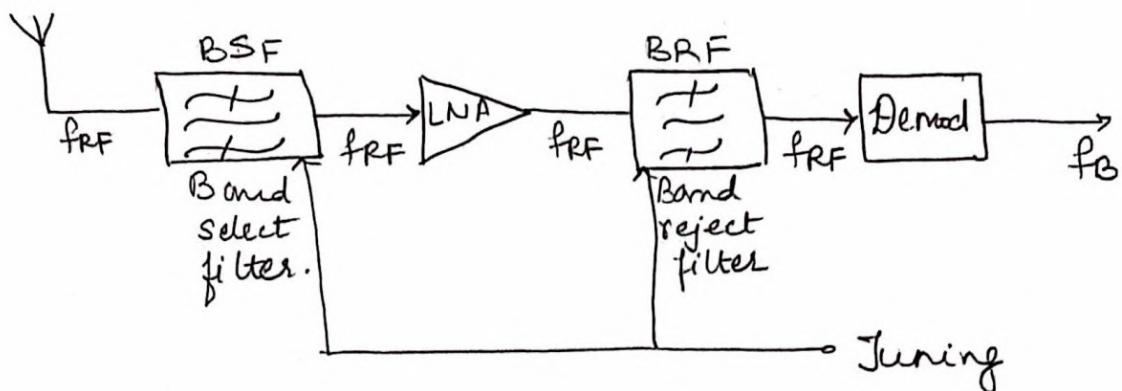1) Tuned radio receiver. (aka tuned homodyne)



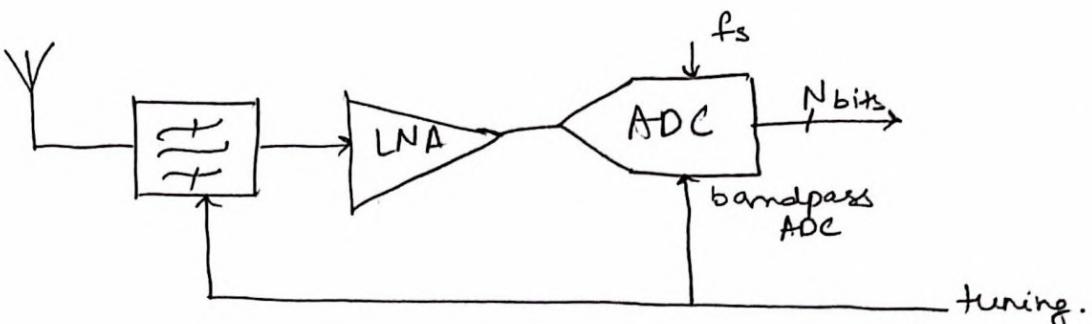Square law detector. Only detects amplitude \Rightarrow AM, ASK.



✓ Poor sensitivity \Rightarrow LNA & filter need large gain

$$s(t) = \text{RF input} = \underbrace{A(t)}_{\text{slow changing & contains information.}} \cos(\omega_{RF}t)$$

$$\text{Output} = [A_v s(t)]^2$$

\hookrightarrow gain of receiver.


$$\text{Output} = \frac{A_v^2 A(t)^2}{2} [1 + \cos(2\omega_{RF}t)]$$

$$\text{Output}_{LPF} = \frac{A_v A(t)}{\sqrt{2}}$$

$\&$ sq.root

Used in AM radio, automatic volume control.

2) Heterodyne or Superheterodyne (1906)

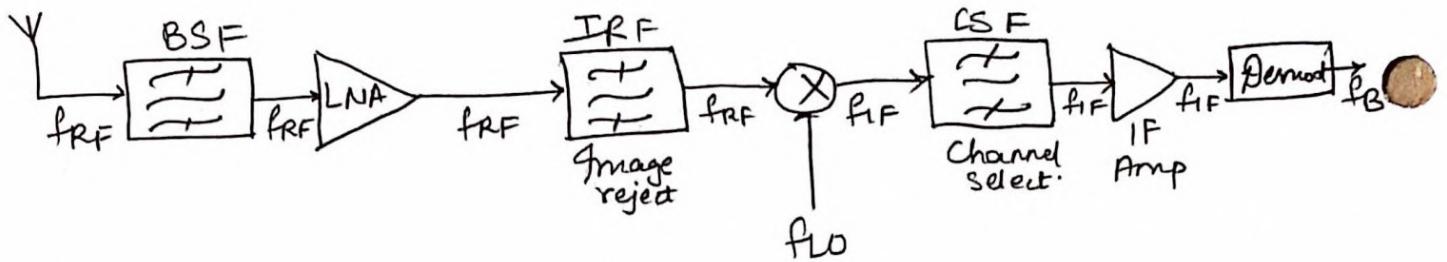

$$f_{RF} = f_{LO} \pm f_{IF}$$

Choosing f_{IF}


High f_{IF} \rightarrow Relaxes IRF design.
 High f_{IF} \rightarrow CSF & IF amp are at high freq.

$$S(t) = A(t) \cos [\omega_{RF}t + \alpha(t)] \cos (\omega_{LO}t)$$


After IRF $\rightarrow \frac{A(t)}{2} \cos [\omega_{IF}t - \alpha(t)]$
 Both amp & phase information.

- Problem is the image rejection filter.
- To eliminate IRF use Hartley and Weaver topologies.

Hartley

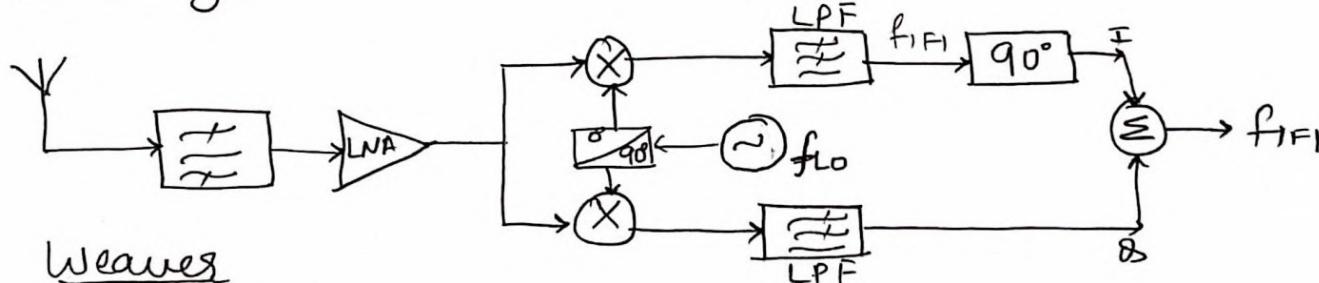

Weaver

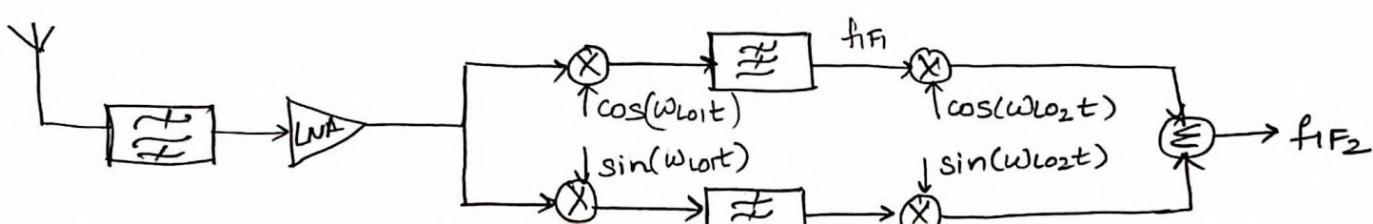

Hartley

$$S_{RF}(t) = A_{RF} \cos(\omega_{RF} t + \alpha_{RF})$$

$$S_{IM}(t) = A_{IM} \cos(\omega_{IM} t + \alpha_{IM})$$

$$f_{RF} = f_{LO} - f_{IF} \quad ; \quad f_{IM} = f_{LO} + f_{IF}$$

Ipath

$$S_I(t) = A_{RF} \cos(\omega_{RF} t + \alpha_{RF}) \cos(\omega_{LO} t) + A_{IM} \cos(\omega_{IM} t + \alpha_{IM}) \cos(\omega_{LO} t)$$

$$\xrightarrow{LPF} S_I(t) = \frac{A_{RF}}{2} \cos(\omega_{IF} t - \alpha_{RF}) + \frac{A_{IM}}{2} \cos(\omega_{IF} t + \alpha_{IM})$$

$$\xrightarrow{90^\circ} S_I(t) = \frac{A_{RF}}{2} \sin(\omega_{IF} t - \alpha_{RF}) + \frac{A_{IM}}{2} \sin(\omega_{IF} t + \alpha_{IM}) \quad \text{①}$$

$$S_O(t) = \frac{A_{RF}}{2} \sin(\omega_{IF} t - \alpha_{RF}) - \frac{A_{IM}}{2} \sin(\omega_{IF} t + \alpha_{IM}) \quad \text{②}$$

$$\text{①} + \text{②} \Rightarrow S_{IF}(t) = A_{RF} \sin(\omega_{IF} t - \alpha_{RF})$$

→ Having 90° phase shift over wideband is difficult.
→ use Weaver

Weaver

$$S_{I1}(t) = \frac{A_{RF}}{2} \cos(\omega_{IF1} t - \alpha_{RF}) + \frac{A_{IM}}{2} \cos(\omega_{IF1} t + \alpha_{IM})$$


$$S_{O1}(t) = \frac{A_{RF}}{2} \sin(\omega_{IF1} t - \alpha_{RF}) - \frac{A_{IM}}{2} \sin(\omega_{IF1} t + \alpha_{IM})$$

→ $\times \cos(\omega_{LO2} t)$
→ $\times \sin(\omega_{LO2} t)$ & add them.

$$\Rightarrow S_{IF2}(t) = \frac{A_{RF}}{2} \cos(\omega_{IF} t - \alpha_{RF}) - \frac{A_{IM}}{2} \cos[(\underbrace{\omega_{IF1} + \omega_{LO2}}_{\text{Image pushed to high frequency.}}) t - \alpha_{IM}]$$

Both amp & phase info.

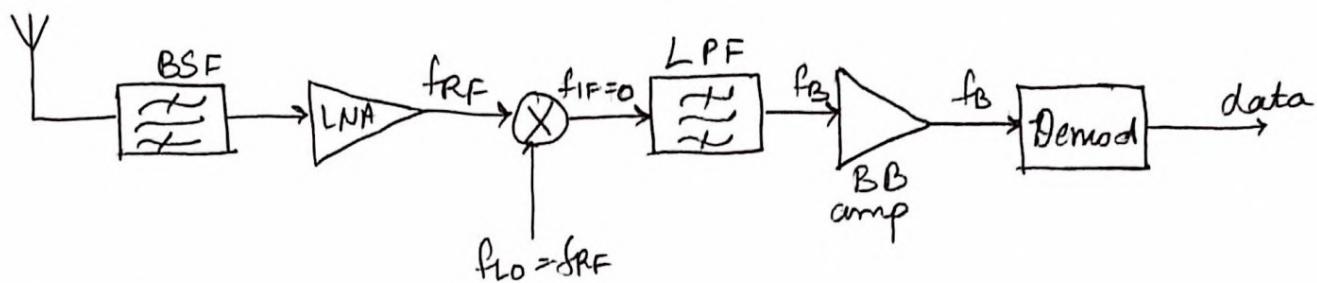⇒ Direct conversion receivers → (Zero IF, Homodyne)
 1924



- ∴ No image.
- ∴ CSF is just a LPF
- ∴ Need to track fRF to adjust fLO
- ∴ fRF 'pulls' fLO.

Heterodyne: $S_{IF}(t) = \frac{A(t)}{2} \cos(\omega_{IF}t - \alpha(t))$

Homodyne: $S_{IF}(t) = \frac{A(t)}{2} \cos(\alpha(t))$

↳ ideal for amplitude modulation
since $\cos \alpha(t)$ is constant

> To get FSK & PSK need I & Q.

∴ DC offset.

∴ Flicker noise of mixer is in band.